


# AC-circuits

## Maximum Power Transfer Theorem

1
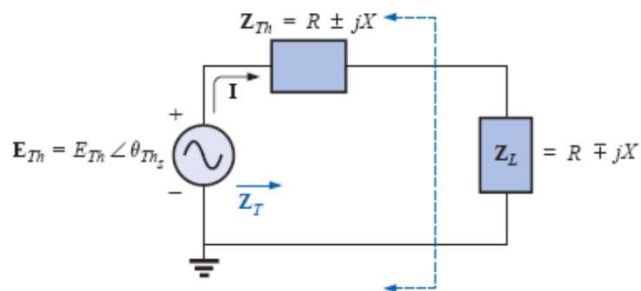
### Maximum Power Transfer Theorem

*Maximum power will be delivered to a load when the load impedance is the complex conjugate of the Thévenin impedance across its terminals.*



$$R_L = R_{Th} \quad \text{and} \quad \pm j X_{load} = \mp j X_{Th}$$

2

The total impedance of the circuit is **purely resistive for Maximum power** to be transferred to the load.

$$Z_T = (R \pm jX) + (R \mp jX)$$

$$F_p = 1$$

(maximum power transfer)

$$Z_T = 2R$$

The magnitude of the current  $I$


$$I = \frac{E_{Th}}{Z_T} = \frac{E_{Th}}{2R}$$

The maximum power to the load is

$$P_{\max} = I^2 R = \left( \frac{E_{Th}}{2R} \right)^2 R$$


and

$$P_{\max} = \frac{E_{Th}^2}{4R}$$

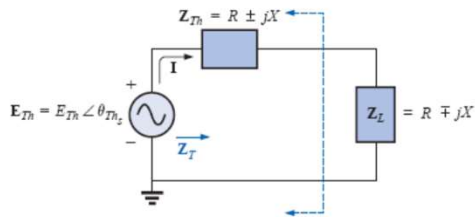

3

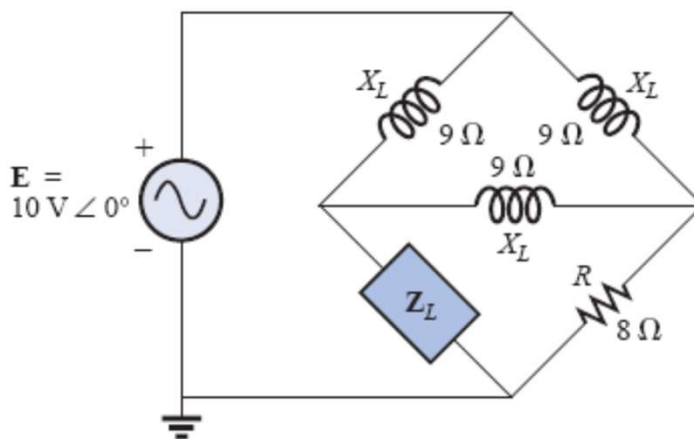**Find the load impedance** in Fig. for maximum power to the load and **find the maximum power** delivered to it.



4

## Star-Delta/ Y- $\Delta$ transformation

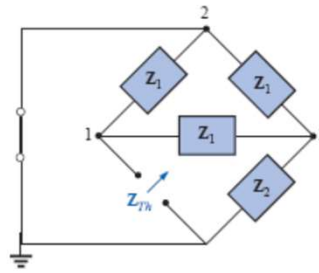


FIG. 18.84

Defining the subscripted impedances for the network of Fig. 18.83.

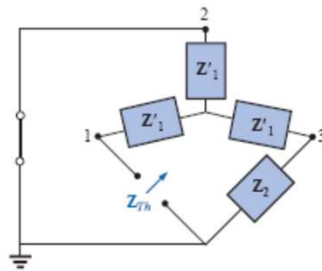


FIG. 18.85

Substituting the Y equivalent for the upper  $\Delta$  configuration of Fig. 18.84.

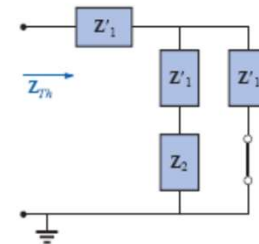


FIG. 18.86

Determining  $Z_{Th}$  for the network of Fig. 18.83.

5

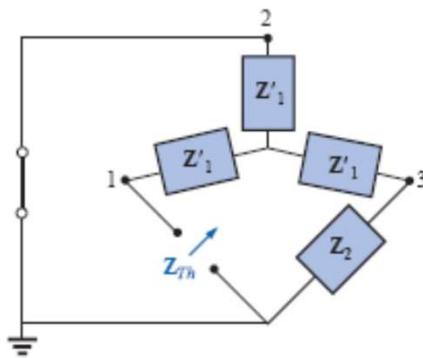


FIG. 18.85

Substituting the Y equivalent for the upper  $\Delta$  configuration of Fig. 18.84.

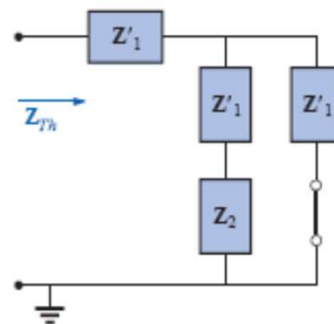


FIG. 18.86

Determining  $Z_{Th}$  for the network of Fig. 18.83.

6

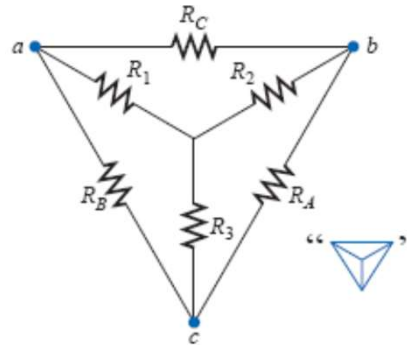


FIG. 8.73

Introducing the concept of  $\Delta$ -Y or Y- $\Delta$  conversions.

7

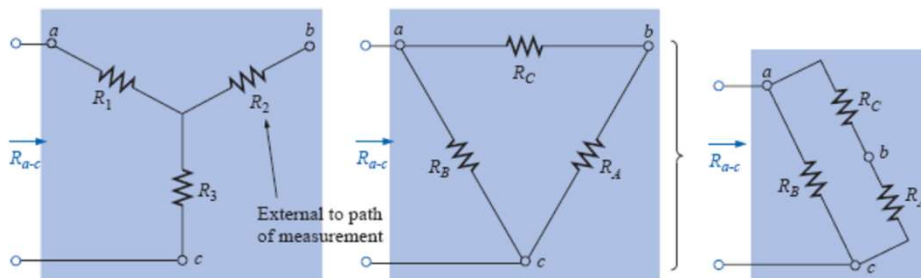


FIG. 8.74

the resistance  $R_{a-c}$  for the Y and  $\Delta$  configurations.

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$


$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

8

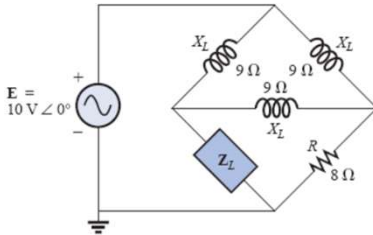Find the load impedance ( $Z_L$ ) in Fig. for maximum power to the load and find the maximum power delivered to it.



$$\begin{aligned}
 Z_{Th} &= Z'_1 + \frac{Z'_1(Z'_1 + Z_2)}{Z'_1 + (Z'_1 + Z_2)} \\
 &= j 3 \Omega + \frac{3 \Omega \angle 90^\circ (j 3 \Omega + 8 \Omega)}{j 6 \Omega + 8 \Omega} \\
 &= j 3 + \frac{(3 \angle 90^\circ)(8.54 \angle 20.56^\circ)}{10 \angle 36.87^\circ} \\
 &= j 3 + \frac{25.62 \angle 110.56^\circ}{10 \angle 36.87^\circ} = j 3 + 2.56 \angle 73.69^\circ \\
 &= j 3 + 0.72 + j 2.46 \\
 Z_{Th} &= 0.72 \Omega + j 5.46 \Omega \\
 Z_L = Z_{Th}^* &\Rightarrow Z_L = 0.72 \Omega - j 5.46 \Omega
 \end{aligned}$$

9

Thanks

10