
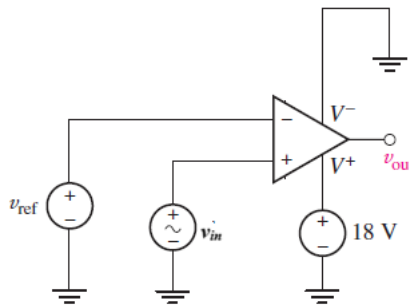


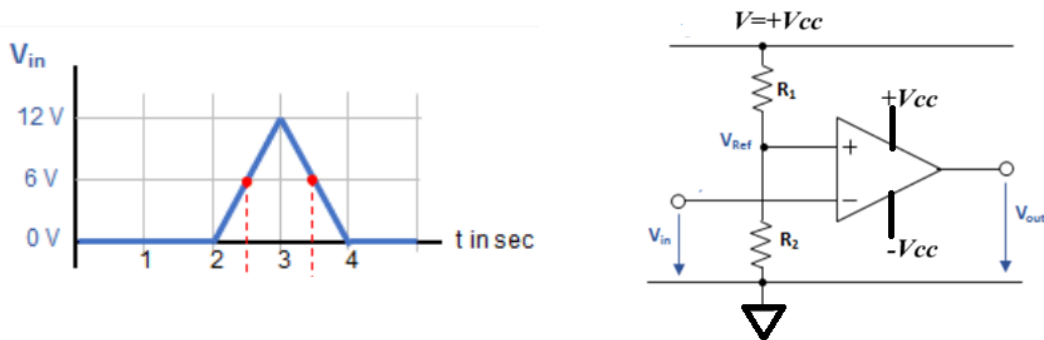
1. For the circuit depicted in below Fig. the input signal v_{in} signal varies continuously between -5 V to $+5\text{ V}$. Sketch the expected output voltage v_{out} as a function of v_{in} for $-5\text{ V} \leq v_{in} \leq +5\text{ V}$, if v_{ref} is equal to (a) -3 V ; (b) $+3\text{ V}$. Assume positive saturation voltage level equal to $+V_{cc}$ and negative saturation voltage level equal to ground ($-V_{cc}$).



2. Draw the out-put voltage wave form in response to the given input wave. Given $+V_{cc}=12\text{ V}$, $-V_{cc}=0\text{ V}$ and $R_1=R_2$.



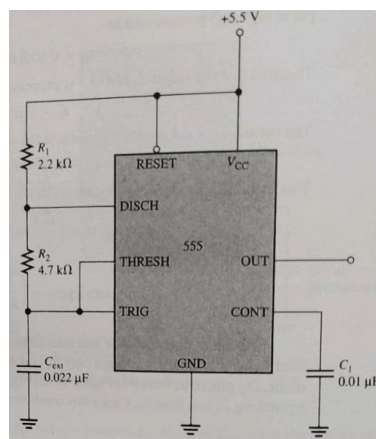3. A 555 timer configured to run in the astable mode is shown in Figure below. Determine the frequency of the output and the duty cycle $=T_{ON}/(T_{ON}+T_{OFF})$. Also draw the output voltage waveform and C_{ext} voltage waveform. Next, a dc supply of 2.8 V is applied to control pin (PIN-5), now recalculate the output waveform frequency and duty cycle.



4. A 555 IC is connected as Monostable multivibrator (one shot) with $C_{ext}=0.1\text{ μF}$ and $R_{ext}=10\text{ k-ohm}$.

What is the pulse width of the output?