
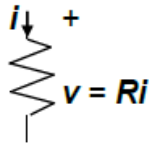


ECE101: Basic Electrical and Electronic Circuits


To be discussed during Feb 10-14

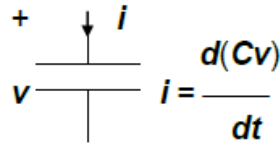

Linear Resistor



Linear Capacitor

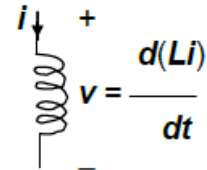



Linear Inductor

For linear time-invariant capacitors and inductors, $i = C(dv/dt)$ and $v = L(di/dt)$ respectively.

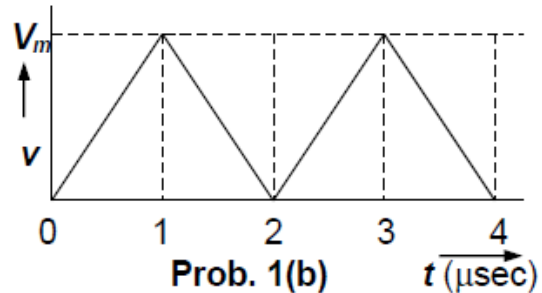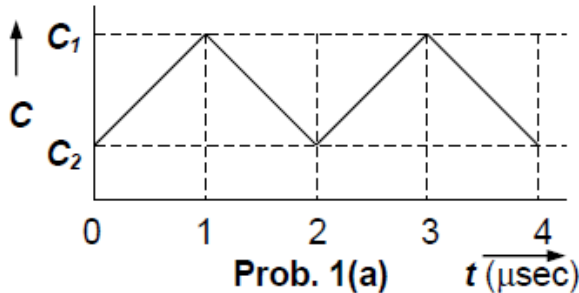Q.1.



Sketch the waveform of the current flowing through a linear capacitor for $0 < t < 4\mu\text{sec}$ if

- a constant voltage $v = 10$ volts is applied to the capacitor and the capacitance C varies with time as shown below, where $C_1 = 2000\text{pF}$ and $C_2 = 1000\text{pF}$.
- the capacitor has a constant capacitance $C = 1000\text{pF}$ and the applied voltage v varies with time as shown below, where $V_m = 10$ volts.




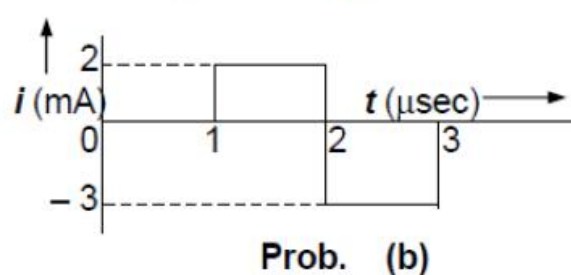
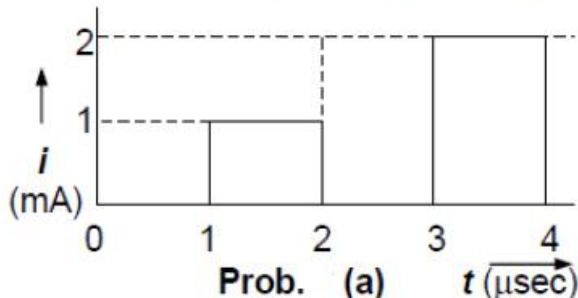
Q.2.

Calculate and sketch the waveform of the voltage v across a linear capacitor having a constant capacitance $C = 0.01\mu\text{F}$ if the capacitor is initially uncharged and the waveform of the current i flowing through the capacitor for a period of $4\mu\text{sec}$ is as given below.



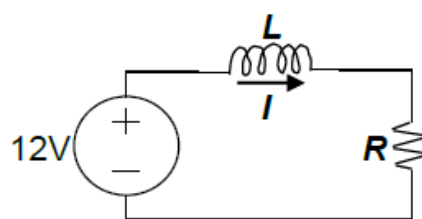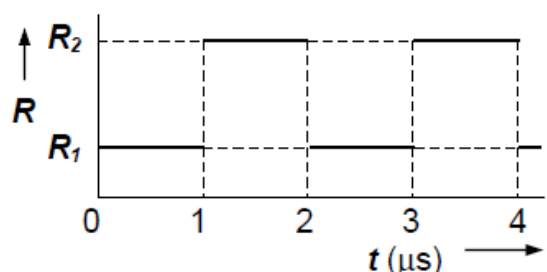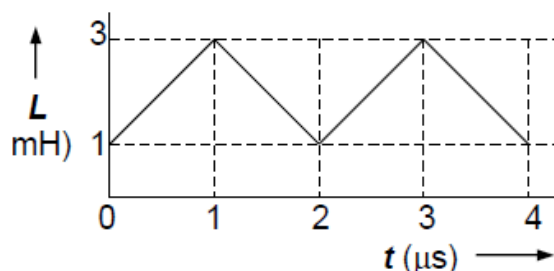Q.3.



A linear time-varying inductor having inductance L and a linear time-varying resistor having resistance R are connected in series with a 12V d-c voltage source. Variations in L and R with time are as shown in the graphs given below, and the resulting current through the series combination is $I = 3\text{mA}$ (d-c). Find the values of R_1 and R_2 .



- Write KVL equations for the two time intervals $0 < t < 1$ (μs) and $1 < t < 2$ (μs) in terms of R_1 and R_2 .
- Hence determine the values of R_1 and R_2 .

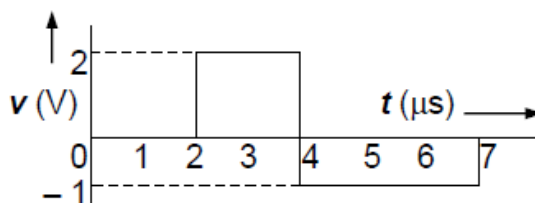
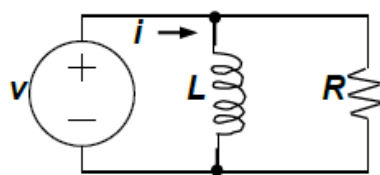
Q.4.

A voltage v having the waveform given below is applied to the parallel combination of a linear time-invariant inductor having inductance $L = 2\text{mH}$ and a linear time-varying resistor having resistance $R = 2\text{k}\Omega$ for $0\mu\text{s} < t \leq 4\mu\text{s}$ and $R = 1\text{k}\Omega$ for $4\mu\text{s} < t \leq 7\mu\text{s}$. Calculate the current i in the given circuit at instants of time $t = 3\mu\text{s}$ and $6\mu\text{s}$ if the inductor current at time $t = 0$ is zero.



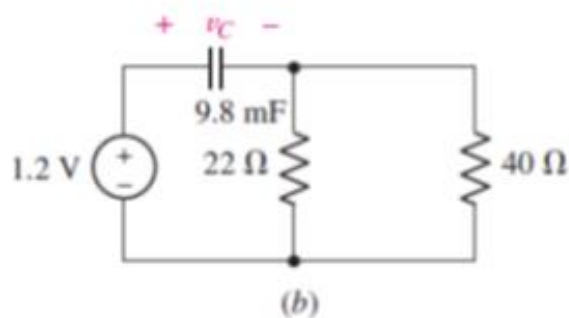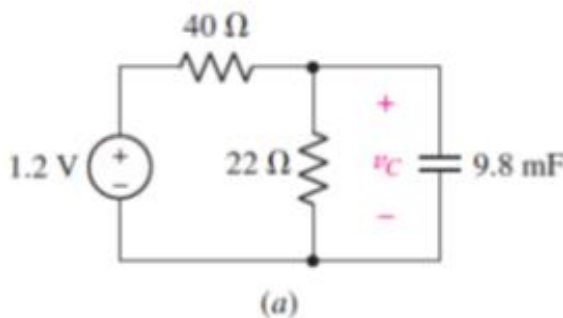
Q.5.

Calculate the power dissipated in the 40Ω resistor and the voltage labelled v_C in each of the circuits depicted in Fig. (a) and (b).



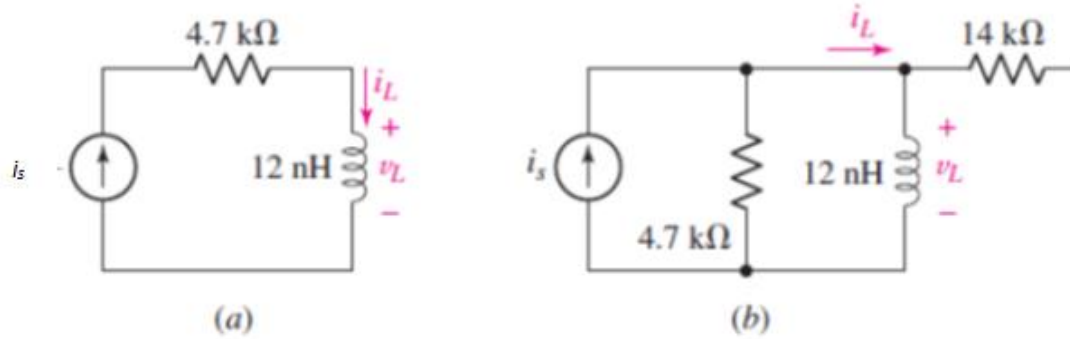Q.6.

Calculate v_L and i_L for each of the circuits depicted in Fig. if $i_s = 1$ mA



Q.7. Find current i and voltage v in the given circuit:

