

Basics of Electrical and Electronic Circuits

Experiment 04

Spring 2025

Thevenin's and Maximum Power Transfer Theorems

Thevenin's and Norton's theorems enable us to construct very simple models to represent a linear time-invariant circuit including independent voltage/current sources, as "seen" by a load connected between any pair of terminals of the circuit. The general structures of Thevenin and Norton equivalents are shown in **Fig.1**. v_{OC} (**Open-Circuit Voltage**) denotes the voltage v_o measured between the terminals when the load is an open-circuit ($i_o = 0$), and i_{SC} (**Short-Circuit Current**) denotes the current i_o flowing into the load when the load is a short-circuit ($v_o = 0$). R_o denotes the **Output Resistance** of the circuit, defined to be the resistance measured between the two terminals of the circuit with the load disconnected and all **independent** sources "removed" (replaced with internal resistance) from /within the circuit. It can be proved that R_o is given by the ratio of the open-circuit voltage v_{OC} and the i_{SC} : $R_o = v_{OC} / i_{SC} = R_{th}$. Thus the Thevenin and Norton equivalents for any given circuit can be obtained if the values of v_{OC} and i_{SC} are measured. But exact open-circuit ($i_o = 0$) and short-circuit ($v_o = 0$) conditions are difficult to achieve in practice, and hence one measures v_o and i_o for several values of R_L and determines v_{OC} and i_{SC} by extrapolation.

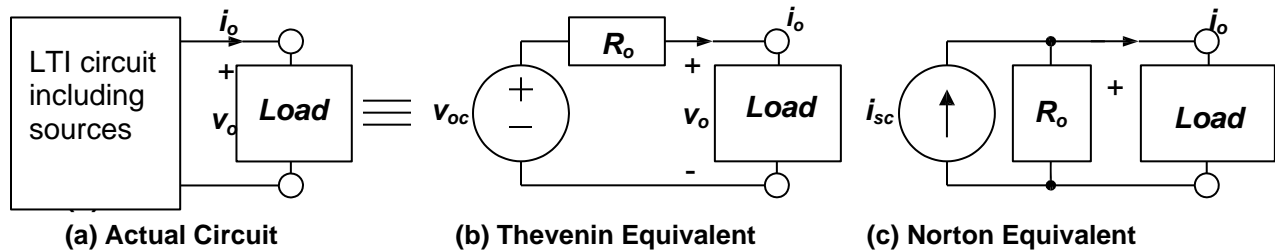


Fig. 1 Equivalent circuits based on Thevenin's and Norton's theorems

The Thevenin resistance, Thevenin voltage and Norton current are related by

$$R_{th} = V_{th} / I_N$$

A. Thevenin and Norton equivalents for resistive load

1. Assemble the resistive circuit shown in **Fig. 2(a)**, where R_L denotes the load resistance and v_s is the WAVEGEN output. Set the WAVEGEN for a **1kHz** sinusoidal output having $V_{pp} = 4V$ and offset = 2V, so that we can expect the voltage v_s to have a minimum level = **0V** and a maximum level = **4V**. However, as WAVEGEN output levels are not very precise, set the Y1 and Y2 cursors precisely at the levels 0V and 4V, and adjust the settings of V_{pp} and offset of the WAVEGEN repetitively to obtain the **minimum** and **maximum** levels of v_s at 0V and 4V **exactly**, as desired.

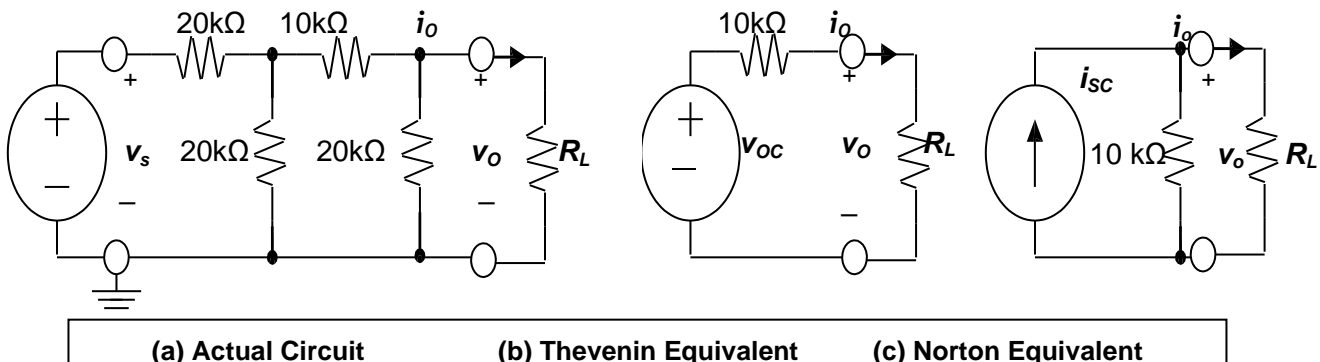


Fig. 2 Resistive circuit with Resistive Load

Basics of Electrical and Electronic Circuits

- Verify that the circuit of **Fig. 2(a)** gets reduced by repeated source transformations to the two equivalents given in **Fig. 2(b)** and **Fig. 2(c)**, where Thevenin's voltage $V_{th} = v_{OC} = v_s / 4$ and Norton's current $I_N = i_{SC} = v_s / (40k\Omega)$.
- Measure the **minimum** and **maximum** levels of the output voltage v_o in the circuit of **Fig.2(a)** with the DSO for the following 7 values of the load resistance R_L : 1.00, 2.20, 4.70, 10.0, 22.0, 47.0 and 100 (all in $k\Omega$). Verify that the minimum level is close to zero in all cases and plot the **peak-to-peak /rms** value of v_o against the **peak-to-peak/rms** value of i_o on a linear graph paper and draw the best approximation of a straight line passing through the points corresponding to different values of R_L .

Table-1: Measurement Table for given circuit (Fig. 2a)

Load Resistance (R_L)	v_o (min)	v_o (max)	$v_o(rms)$	$i_o(rms) = v_o(rms)/R_L$	Power ($v_{rms} * i_{rms}$)

Also save /draw input and output waveforms.

- Determine the **peak-to-peak** values of the **Open-Circuit Voltage** v_{OC} and the **Short-Circuit Current** i_{SC} from the intercepts of the straight line on the two axes and hence calculate the value of the **Output Resistance** $R_o = R_{th} v_{OC} / i_{SC}$. Verify/compare that, this value is the same as the value R_{th} and R_N indicated in the equivalent circuits of **Fig. 2(b)** and **Fig. 2(c)** respectively.

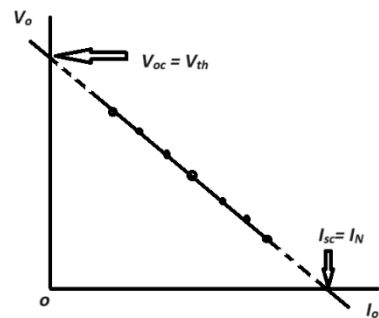


Fig.3. v_o and i_o plot to extract V_{th} and I_N

- Connect a **0.01 μF capacitor** as the **Load** instead of the resistance R_L in the circuit of **Fig.2(a)**. Sketch the input and output waveforms and measure the **minimum** and **maximum** levels of the output voltage v_o .
- Connect the given **diode** as the **Load** instead of the resistance R_L in the circuit of **Fig.2(a)**. Choose the polarity of the diode so as to ensure the flow of current through the diode. Sketch the input and output waveforms and measure the **minimum** and **maximum** levels of the output voltage v_o .

Table-2: Measurement Table for given circuit (Fig. 2a)

Load	v_o (min)	v_o (max)	$v_o(rms)$	$i_o(rms) = v_o(rms)/R_L$	Power ($v_{rms} * i_{rms}$)
Capacitor(0.01 μF)					
Diode					

B. Thevenin equivalent with Resistive, Capacitive and Nonlinear Loads

- Now set up the Thevenin equivalent circuit given in **Fig. 2(b)**, with a Load Resistance $R_L = 10k\Omega$, and adjust the **maximum** level of the WAVEGEN output to **1V**, keeping the **minimum** level at **0V**, so that the input voltage is the same as expected value of $v_{OC} (= v_s / 4)$. Measure the **minimum** and **maximum** levels of the output voltage v_o and

Basics of Electrical and Electronic Circuits

compare these values with the values measured in step **A.3** for the same Load Resistance ($R_L = 10\text{k}\Omega$).

2. Now connect the same **0.01 μF capacitor** as used in step **A.5** as the Load instead of the $10\text{k}\Omega$ resistor in the circuit of **Fig. 2(b)**. Sketch the input and output waveforms and measure the **minimum** and **maximum** levels of the output voltage v_o . Compare these measured values with those obtained in step **A.5**.
4. Now connect the same **diode** as used in step **A.6** as the Load instead of the $10\text{k}\Omega$ resistor in the circuit of **Fig. 2(b)**. Sketch the input and output waveforms and measure the **minimum** and **maximum** levels of the output voltage v_o . Compare these measured values with those obtained in step **A.6**.

Table-3: Measurement Table for given circuit (Fig. 2b)

Load	v_o (min)	v_o (max)	$V_{o(rms)}$	$i_{o(rms)} = V_{o(rms)}/R_L$	Power ($V_{rms} * i_{rms}$)
$R_L = 10\text{k}\Omega$					
Capacitor(0.01 μF)					
Diode					

- C. Verification of Maximum Power Transfer Theorem:** Plot Power (P) with respect to R_L values obtained in Table-1. Identify the maximum power transfer condition (i.e. the value of load resistor R_L and its relationship with R_{th} at which P_{max} occurs) and find the P_{max} value.

Results:

Conclusion: It must be in your words and be based on your understanding/ learning in the experiment.