

## Basics of Electrical and Electronic Circuits

### Experiment 6

### Series and Parallel Resonance

Spring 2025

Resonance is a property that enables one to select a particular frequency out of a signal containing many frequencies. This frequency-selective behaviour is essentially that of a band-pass circuit having a very sharp peak in its frequency response. In this experiment, we will study two RLC circuits which exhibit this kind of frequency response. One of them is called a series resonant circuit, and the other, a parallel resonant circuit. The circuit configurations for these two are given in **Fig.1** and **Fig. 2**. Both circuits consist of the three basic elements – a capacitance **C**, an inductance **L** and a resistance **R**, but they are interconnected differently resulting in different electrical property. At the resonant frequency, a series resonant circuit gives the **minimum impedance** while a parallel resonant circuit gives the **maximum impedance**. Most practical capacitors used in such circuits can be represented by a pure capacitance. Most practical inductors, on the other hand, are coils with a ferromagnetic core, which do not behave like a pure inductance, but have to be represented by a series combination of an inductance **L** and a resistance **r<sub>L</sub>**. This resistance **r<sub>L</sub>** is not just the resistance of the wire constituting the coil; it also includes a resistance which represents the power losses in the coil due to hysteresis and eddy current. Hence the resistance **r<sub>L</sub>** is always higher than the resistance of the coil as measured by a multimeter. Moreover, the nonlinear magnetization characteristics of the ferrite core makes the coil behave in a slightly nonlinear fashion that may lead to some distortions in the waveforms.

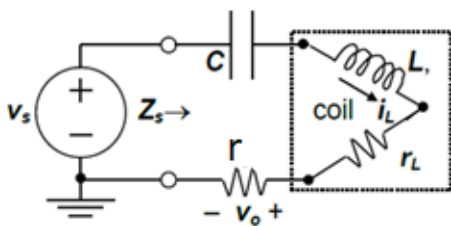


Fig. 1 Series Resonant LRC circuit

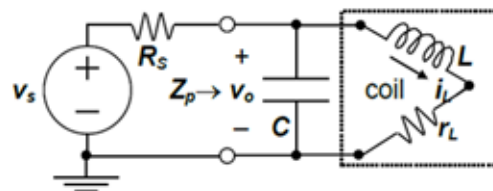


Fig. 2 Parallel Resonant LRC circuit

#### Part A. Series Resonance

As this circuit gives a low impedance **Z<sub>s</sub>** which is **minimum** at the resonant frequency, it is preferable to measure the current **i<sub>L</sub>** and note how it goes through a **maximum** as frequency is varied. But the DSO— our primary test equipment – can only enable us to observe voltages, we have to add an external resistance **r** as shown, and then observe the waveform of the voltage **v<sub>o</sub> = i<sub>L</sub>r** across the resistance **r**. The total Impedance **Z<sub>s</sub>** of the series LRC circuit shown in **Fig. 1** is therefore given by

$$\mathbf{Z_s = R + j(X_L - X_C) = R + j(\omega L - 1/\omega C)}, \text{ where } \mathbf{R = r_L + r} \text{ is the total resistance in the circuit.}$$

The magnitude of impedance **Z<sub>s</sub>** will be **minimum** and hence the amplitude of **i<sub>L</sub>** will be **maximum** for a given amplitude of the applied voltage **v<sub>s</sub>** at the **series resonant frequency**

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

At this frequency, the waveforms of **v<sub>o</sub>** and **v<sub>s</sub>** will be **in phase** because **Z<sub>s</sub>** is real (**=R**), and **v<sub>o</sub> / v<sub>s</sub> = r / (r + r<sub>L</sub>)**. This property will be made use of to determine the values of **f<sub>s</sub>** and **r<sub>L</sub>** in this experiment.

1. Check the values of the given capacitor and resistors by noting their printed value and colour codes respectively. Set up the circuit shown in **Fig. 1**, with **C = 0.1μF**, **r = 100 Ohm** and the given inductor **1 mH**. Apply the input voltage **v<sub>s</sub> = 2V** (peak to peak), a sinusoidal waveform having frequency **50kHz** from the WAVEGEN.
2. Observe the waveforms of the voltages **v<sub>s</sub>** and **v<sub>o</sub>** on DSO Channels 1 and 2 and verify that they are both sinusoidal. This ensures that the circuit is indeed Linear and Time-invariant, in spite of the unavoidable non-linearity in the inductor.
3. Change the DSO display mode to the **x-y** mode, and note the elliptical display, indicating a phase difference between **v<sub>s</sub>** and **v<sub>o</sub>**. Vary (Increase/ decrease) the frequency gradually until the display becomes a straight line with 45°. At this point, **v<sub>s</sub>** and **v<sub>o</sub>** are in phase, implying that the voltages across the capacitance and the inductance cancel each other, resulting in the condition **v<sub>o</sub> / v<sub>s</sub> = r / (r + r<sub>L</sub>)**. Note the value of this frequency (**= f<sub>s</sub>**) and the slope of the straight line (**= r / (r + r<sub>L</sub>)**). Determine the values of **r<sub>L</sub>** from these measured values, using the known values of **C** and **r** and the given theoretical expressions for **f<sub>s</sub>** and the slope of the graph. You will later learn how to prove these expressions.
4. Measure the resistance of the coil with a multimeter and compare this value with the value of **r<sub>L</sub>** just obtained by the measurement at resonance. Comment on the difference between the two values.

#### Observation Table-1

Experimental $r_L$	Measured from multimeter $r_L$

5. Change the mode of the DSO to **y-t** and determine the frequencies  $f_1$  and  $f_2$  at which the ratio of the AMPLITUDES of  $v_o$  and  $v_s$  becomes the value measured in step 3 divided by  $\sqrt{2}$ .  
 Note that near the resonant frequency, the impedance of the series resonant circuit is quite low, and its magnitude changes quite sharply as the frequency is varied. This results in continuous variation in the amplitude of  $v_s$  due to the current drawn by the resonant circuit from the WAVEGEN (“loading”), though the WAVEGEN setting still continues to indicate the same value. An intelligent way to determine  $f_1$  and  $f_2$  is to set the **scale factors** of the DSO channels so that  $v_s$  and  $v_o$  will **appear** to have equal amplitudes on the screen when their ratio has the desired value.

Observation Table-2

Series Resonance	Resonance Freq ( $f_s$ )	Current $I_{(max)}$ at $f_s$ for Minimum Impedance of value $(r+r_L)=\dots\dots\Omega$	Lower cut-off Frequency ( $f_L<f_s$ ) at which $I= 0.707*I_{max}$	Upper (or higher) cut-off Frequency ( $f_u$ or $f_H> f_s$ ) at which $I= 0.707*I_{max}$
R=....., L=....., C=.....				

6. Find the value of the bandwidth ( $f_2 - f_1$ ) and hence the value of the Quality Factor  $Q = f_s / (f_2 - f_1)$ . Compare this value with the theoretically expected  $Q = \sqrt{(L / C) / R}$ .

Observation Table-3

Experimental resonance frequency $f_s$	Experimental bandwidth ( $f_2 - f_1$ )	Experimental Quality factor $Q$	Theoretical value of resonance freq $f_s$	Theoretical value of bandwidth ( $f_2 - f_1$ )	Theoretical value of Quality factor $Q$

**Part B. Parallel Resonance**

In a parallel resonant circuit, the capacitor and the inductor are placed in parallel, resulting in a high impedance which becomes **maximum** at the resonant frequency. To observe this variation in impedance as frequency is varied, an additional resistor is placed in series with the applied voltage source (WAVEGEN), as shown in **Fig. 2**, and the voltages  $v_s$  and  $v_o$  are connected to two channels of the DSO . At the resonant frequency, the waveforms of  $v_o$  and  $v_s$  will be **in phase** because  $Z_p$  becomes real ( $=R_p$ ), and so the **x-y** plot will give a straight line with slope  $R_p/(R_s+ R_p)$ . This property will be made use of to determine the values of  $f_p$  and  $R_p$  in this experiment.

1. Remove the 100 Ohm resistor and insert  $R_s = 10k\text{-Ohm}$  to set up the Parallel Resonant circuit given in **Fig.2** and obtain a display of  $v_o$  against  $v_s$  with the DSO in the **x-y** mode. **Decrease** the frequency gradually until the display becomes a straight line again. Measure the slope of this straight line and this frequency  $f_p$ , which is the resonant frequency of the inductance  $L$  and the capacitance  $C$ :

**At parallel: frequency  $f_p$ ,  $v_o / v_s = R_p/(R_s+ R_p)$  and  $f_p = 1/2\pi\sqrt{(LC_{eq})}$ , where  $C_{eq} = C$**

2. Now determine the cut-off frequencies (lower and upper) by decreasing and increasing the frequency from  $f_p$  .

Observation Table-4

Parallel Resonance	Resonance Freq ( $f_p$ )	Current $I_{(min)}$ at $f_s$ for Maximum Impedance of value $(R_s+R_p)=\dots\Omega$	Lower cut-off Frequency ( $f_L<f_p$ ) [at which $I= 1.414*I_{min}$ ]	Upper (or higher) cut-off Frequency ( $f_u$ or $f_H> f_p$ ) [at which $I= 1.414*I_{min}$ .]
R=....., L=..... C=.....				

**Note: Qualitatively draw current Vs frequency plot for both series and parallel resonance circuits indicating the useful data obtained from experimental observations.**

**Results:**

**Conclusion:** It must be in your words and be based on your understanding/ learning in the experiment.