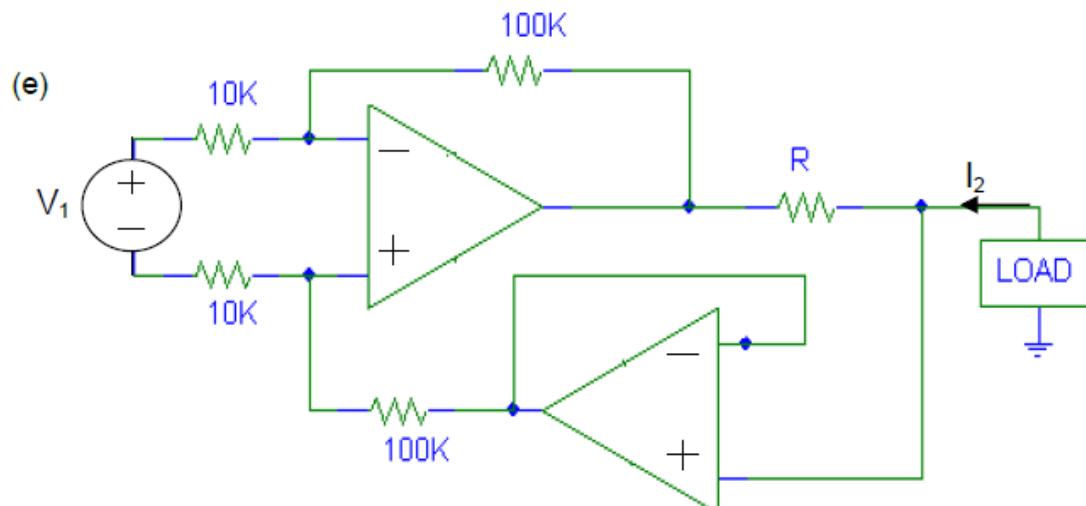
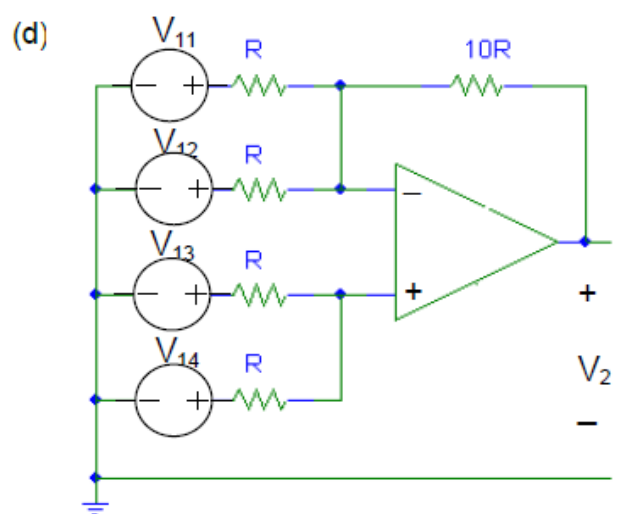
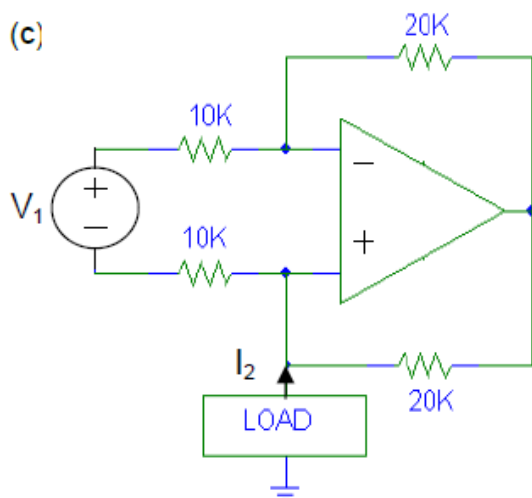
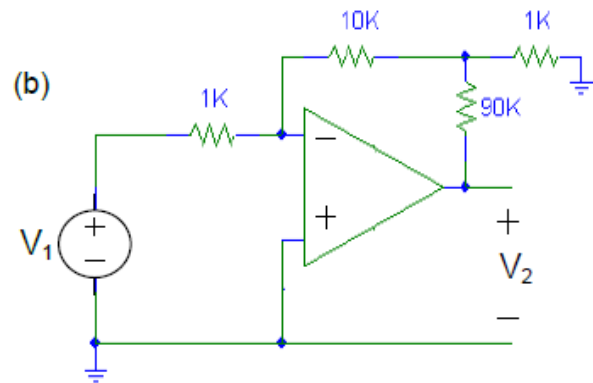
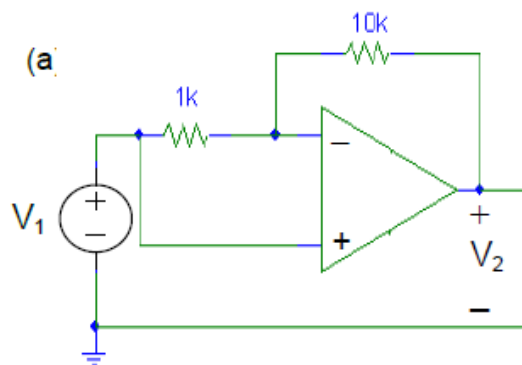


1. The Thevenin equivalent of a microphone for a particular sound level consists of a voltage source $V_s = 20\text{mV}$ peak-to-peak in series with a resistance $R_s = 100\text{k}\Omega$.
 - (a) Find the power delivered to a loudspeaker having resistance $R_L = 8\Omega$ if it is directly connected across the output terminals of the microphone.
 - (b) If an amplifier having input resistance $R_i = 100\text{k}\Omega$ is used to amplify the signal from the microphone, find the required Voltage Gain of the amplifier so that the power delivered by the amplifier to the same loudspeaker is 4W .
 - (c) How would the required Voltage Gain change if (i) $R_i = 10\text{k}\Omega$ and (ii) $R_i = 1\text{M}\Omega$?
 - (d) Calculate the values of the Power Gain of the amplifier in the three cases.
 - (e) Comment on how the Voltage and Power gains change as R_i changes.
2. Assuming the opamp(s) to be ideal, obtain the input-output relationships of the given circuits.



3.

Three pressure-sensitive sensors are used to double-check the weight readings obtained from the suspension systems of a long-range jet airplane. Each sensor is calibrated such that $10\ \mu\text{V}$ corresponds to $1\ \text{kg}$.

(a) Design a circuit which adds the three voltage signals to produce an output voltage calibrated such that $10\ \text{V}$ corresponds to $400,000\ \text{kg}$, the maximum take-off weight of the aircraft.

(b) Verify your design by analyzing the final circuit.