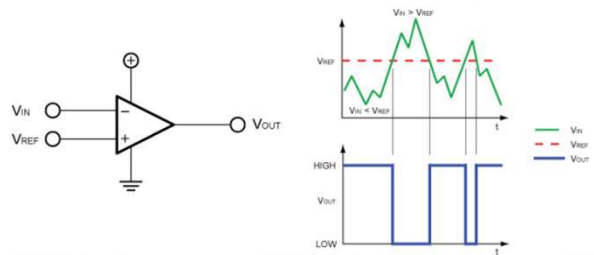


- Inverting Operation: When V_{IN} exceeds V_{REF} , the output V_{OUT} goes from HIGH to LOW.



The inverting operation can be represented in another graphical form:




Inverting Comparator Operation

OPAMP in Open Loop as a Comparator

- Non-inverting Operation: When V_{IN} exceeds V_{REF} , the output V_{OUT} goes from LOW to HIGH.



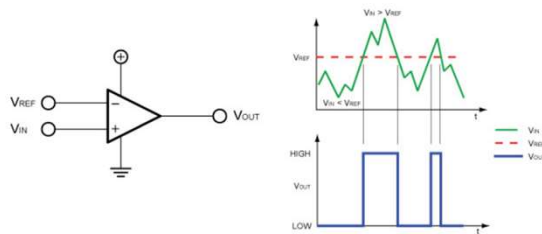The non-inverting operation can be represented in another graph:




Non-inverting Comparator Operation

1


555 Timer IC

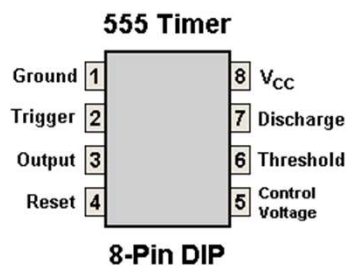- For lowish frequencies (<1MHz), a cheap and reliable clock can be made with a 555 timer chip.




2

555 Timer: Block Diagram

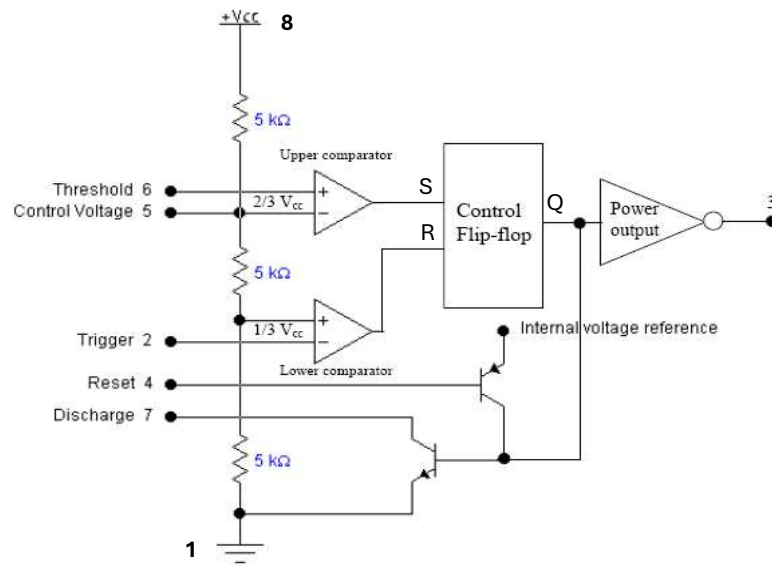


3

555 Timer

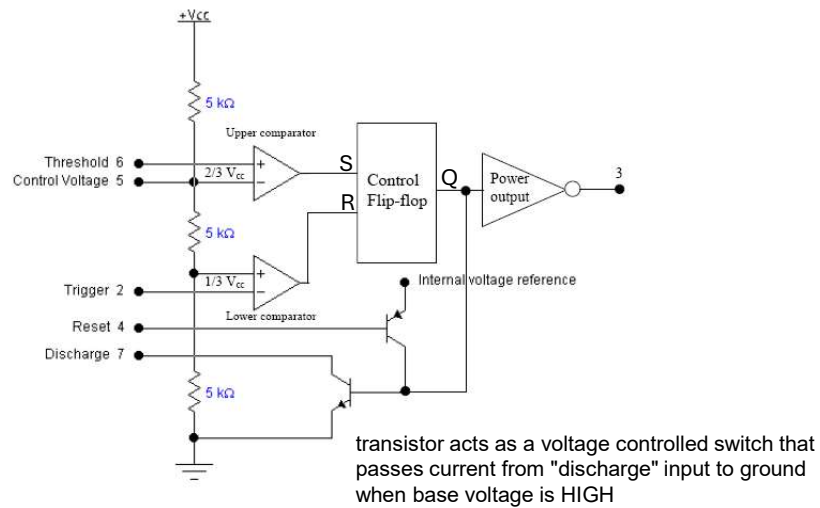


4

555 Timer

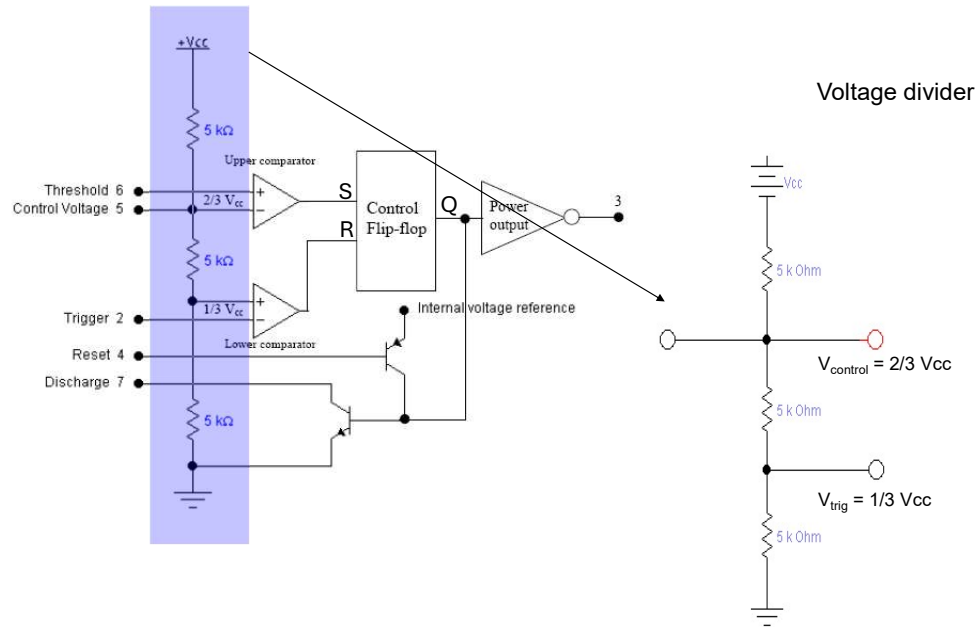


5

555 Timer

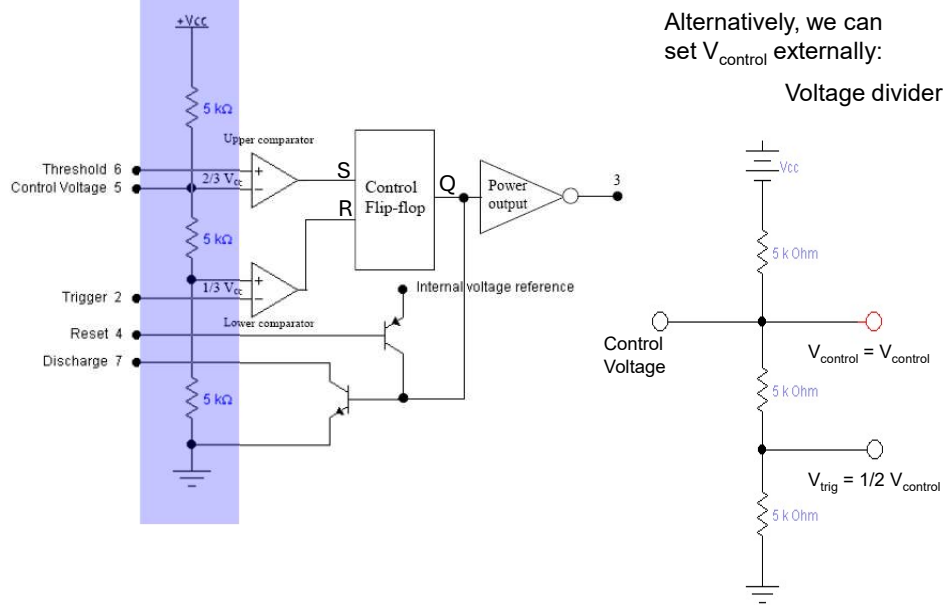

6

555 Timer

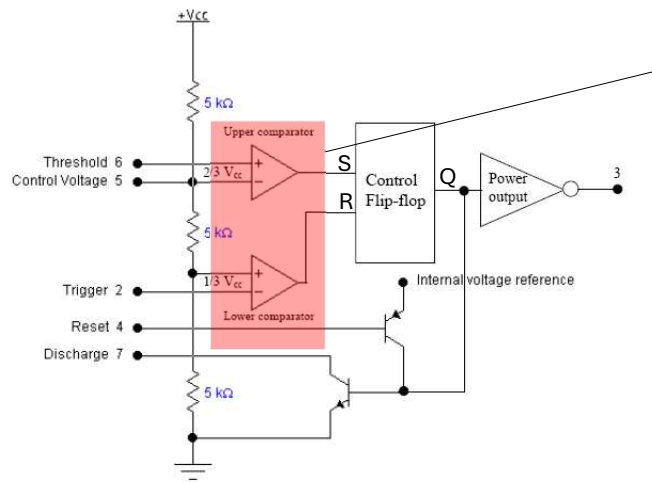

Two Comparators:
Output a HIGH voltage level when the "+" input is greater than the "-" input.


Upper comparator:
Threshold input is compared to V_{control}

Lower comparator: Trigger input is compared to V_{trig} .

Results are passed to a flipflop

7

555 Timer

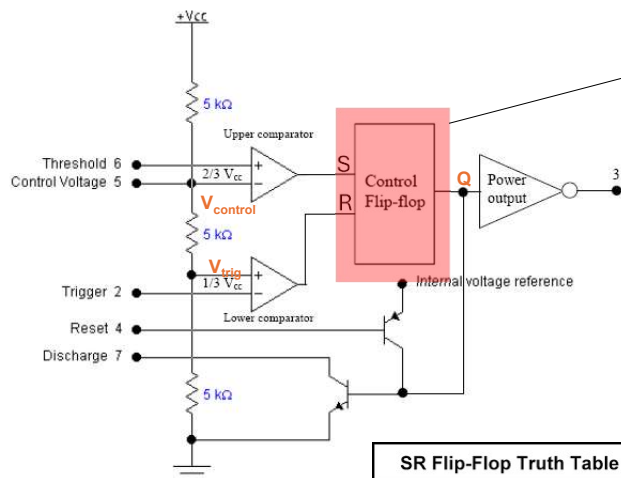

Flipflop:
Stores the information of which comparator last passed it a high voltage.

If Threshold $> V_{\text{control}}$;
S=1
Output state is HIGH.
Transistor is switched on

If Trigger $< V_{\text{trig}}$;
R=1
Output state is LOW
Transistor is switched off.


SR Flip-Flop Truth Table			
Inputs		Outputs	
S	R	Q	\bar{Q}
0	0	No Change	
0	1	0	1
1	0	1	0
1	1	Undefined	

8


555 Timer: Monostable configuration

Single pulse in response to single input trigger signal

- Initial state: flipflop is "set". Point C is HIGH.
- Transistor is on - passing capacitor charge to ground.
- When trigger input at A goes LOW, bottom comparator triggers and E goes HIGH.
- Flipflop changes state: C goes LOW
- Transistor is off - capacitor starts charging (B) through R
- When point B reaches $2/3 V_{CC}$, flipflop changes state, transistor is on, capacitor discharges rapidly.
- Output pulse is just the inverse of C

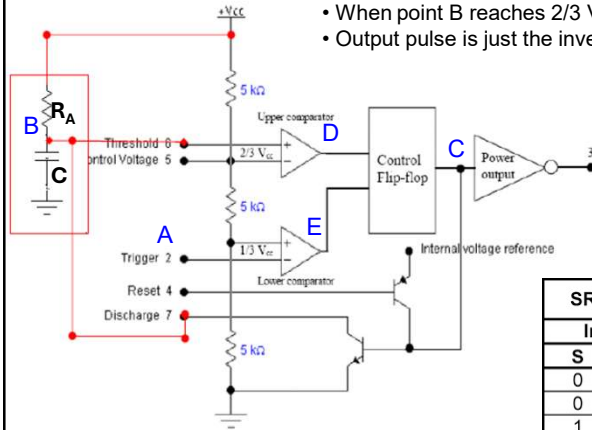

SR Flip-Flop Truth Table			
Inputs		Outputs	
S	R	Q	\bar{Q}
0	0	No Change	
0	1	0	1
1	0	1	0
1	1	Undefined	

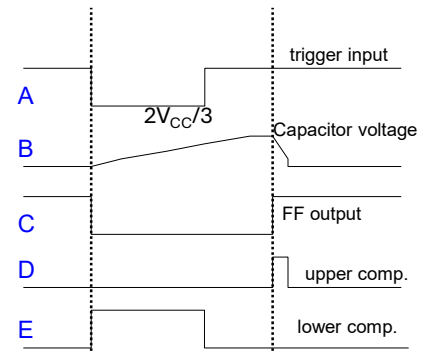


9

Time duration for which output remains High in Monostable Multivibrator / configuration:
 T_H = The Time Required to charge Capacitor C with Voltage $v_c = 2V_{CC}/3$.

Capacitor Charging Equation $v_c = V_{CC}(1 - e^{-t/RC})$

At $v_c = 2V_{CC}/3$
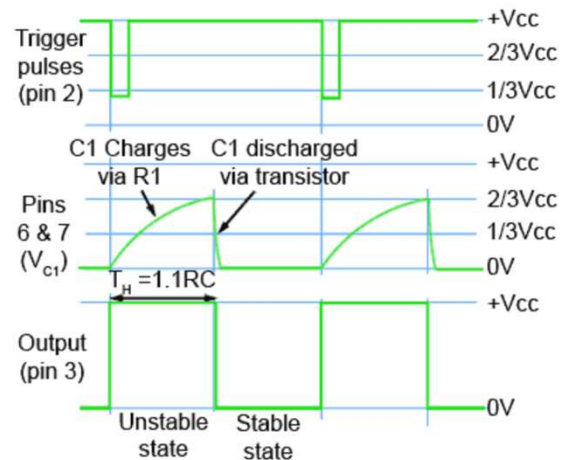
$$t = R_A C \ln(3) = 1.0986 R_A C \approx 1.1 R_A C$$




The monostable circuit has only one stable state (output low).

Monostable 555 operation

10


555 Timer: Astable configuration

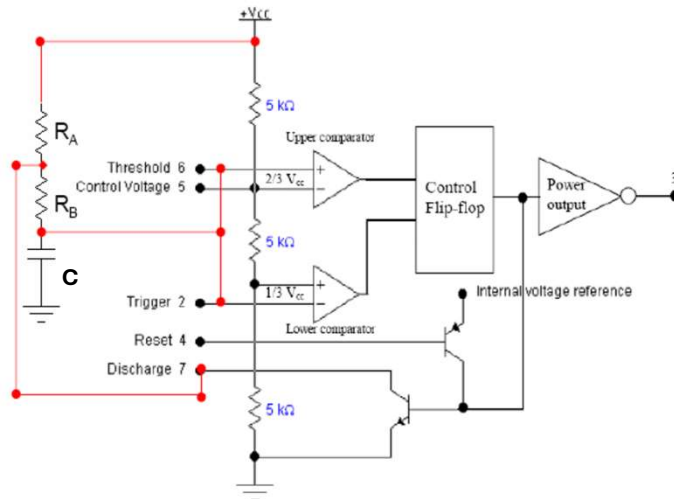- In this mode, connect both comparator inputs to the capacitor in order to generate a clock.
- Charge up through $R_A + R_B$, discharge through R_B
- Capacitor charging and discharging times can be controlled by resistor selection, in order to define the clock period and duty cycle



$$\tau_c = (R_A + R_B)C \quad T_H = (R_A + R_B)C \ln 2$$
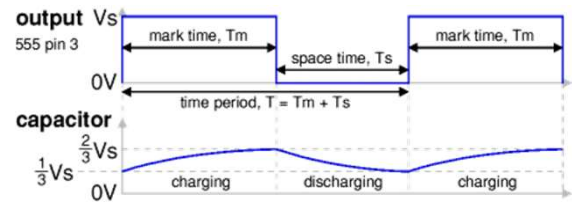
$$\tau_d = R_B C \quad T_L = R_B C \ln 2$$



11

Time duration for which output remains High in Astable configuration:

T_H = The Time Required to charge Capacitor C from $V_{cc}/3$ to $2V_{cc}/3$ through R_A and R_B

$$\text{Gen. eq. of Capacitor Charging } v_c = V_{cc}(1 - e^{-t/RC})$$

Time required from 0 V to $V_{cc}/3 = t_1$

$$\Rightarrow V_{cc}/3 = V_{cc}(1 - e^{-t_1/(R_A + R_B)C}) \Rightarrow t_1 = (R_A + R_B)C \ln(3/2)$$

Time required from 0 V to $2V_{cc}/3 = t_2$

$$2V_{cc}/3 = V_{cc}(1 - e^{-t_2/(R_A + R_B)C}) \Rightarrow t_2 = (R_A + R_B)C \ln(2)$$

Therefore, Time required to charge $V_{cc}/3$ to $2V_{cc}/3 = t_2 - t_1 = T_H = (R_A + R_B)C \ln(2) = 0.693 (R_A + R_B)C$

Time duration for which output remains LOW in Astable configuration:


Similarly, the discharging equation from $2V_{cc}/3$ at any instant t , is given by $v_c = 2V_{cc}/3 * e^{-t/R_B C}$

If Time of discharging from $2V_{cc}/3$ to $V_{cc}/3 = T_L$

$$V_{cc}/3 = 2V_{cc}/3 * e^{-T_L/R_B C} \Rightarrow T_L = R_B C \ln(2) = 0.693 R_B C$$

Overall, period of the square wave $T = T_H + T_L = 0.693(R_A + 2R_B)C$
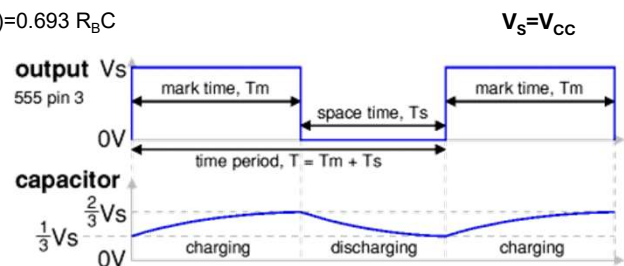
$$\text{Duty cycle} = T_H / (T_H + T_L) = (R_B + R_A) / (2R_B + R_A)$$




12

Basics of Transistors


13

Transistor Technologies (Review)

Bipolar Junction Transistor


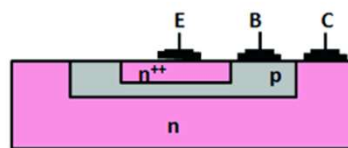


NPN Transistor

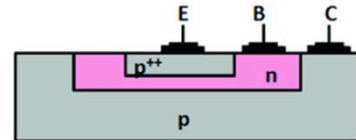


PNP Transistor

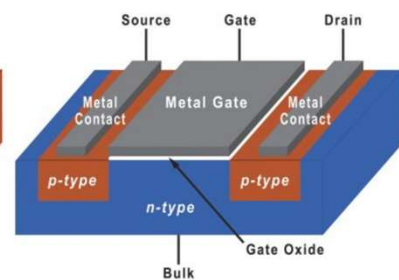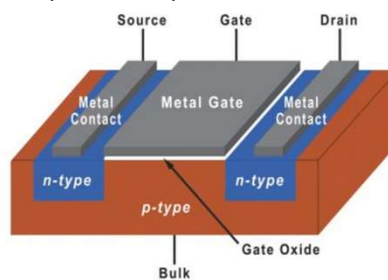Metal-Oxide-Field Effect Transistor (MOSFET)




14

Bipolar Junction Transistor

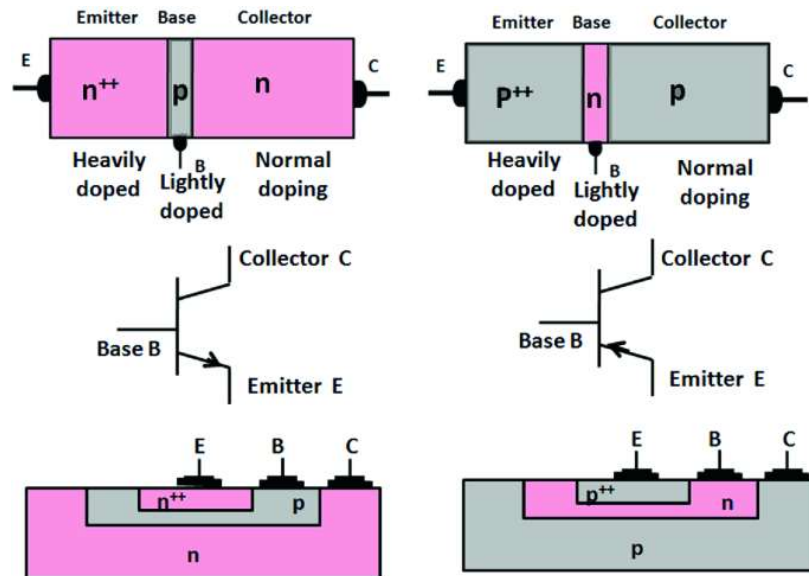


15

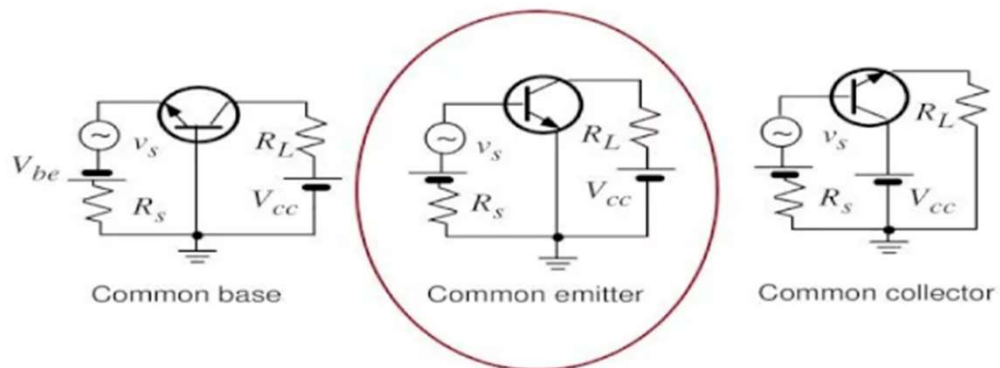Three Fundamental BJT Amplifier/biasing Configurations




16

Common Emitter I-V characteristics

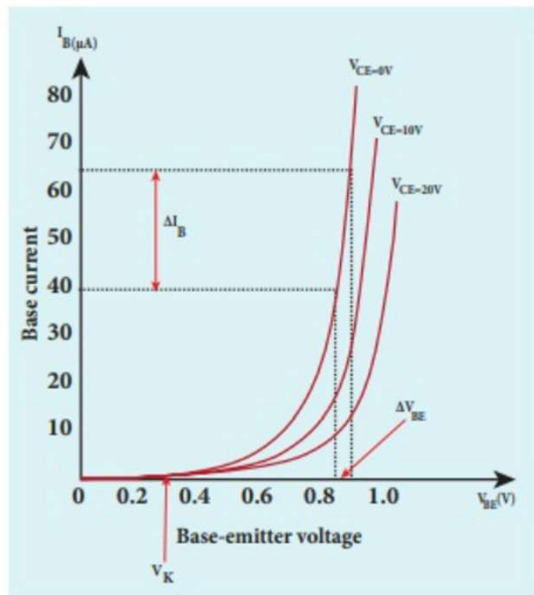

$I_B - V_{BE}$ Input

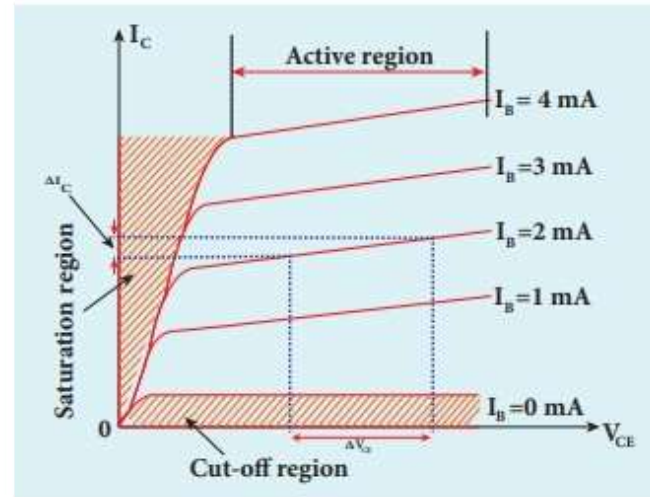


$I_C - V_{CE}$ Output Characteristics

17

Physical structure of bipolar junction transistor (BJT)

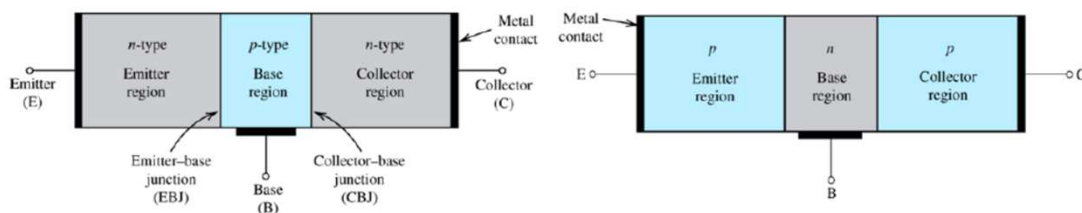- Both electrons and holes participate in the conduction process for bipolar devices
- BJT consists of two pn junctions constructed in a special way and connected in series, back to back
- The transistor is a three-terminal device with **emitter**, **base** and **collector** terminals
- From the physical structure, BJTs can be divided into two groups: *npn* and *pnp* transistors



Modes of operation

- The two junctions of BJT can be either forward or reverse-biased
- The BJT can operate in different modes depending on the junction bias
- The BJT operates in active mode for amplifier circuits
- Switching applications utilize both the cutoff and saturation modes

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

18


Operation of the npn transistor in the active mode

□ Terminal currents of BJT in active mode:

i_E (emitter current) = i_{En} (electron injection from E to B) + i_{Ep} (hole injection from B to E)

i_C (collector current) = i_{Cn} (electron drift) + i_{CBO} (CBJ reverse saturation current with emitter open)

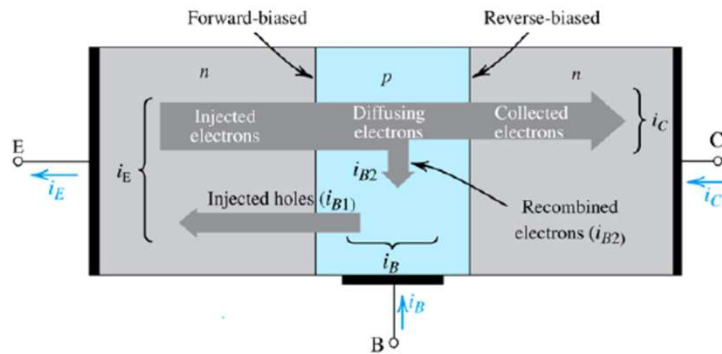i_B (base current) = i_{B1} (hole injection from B to E) + i_{B2} (recombination in base region)




19

Circuit symbols, voltage polarities and current flow

□ Terminal currents are defined in the direction as current flow in active mode

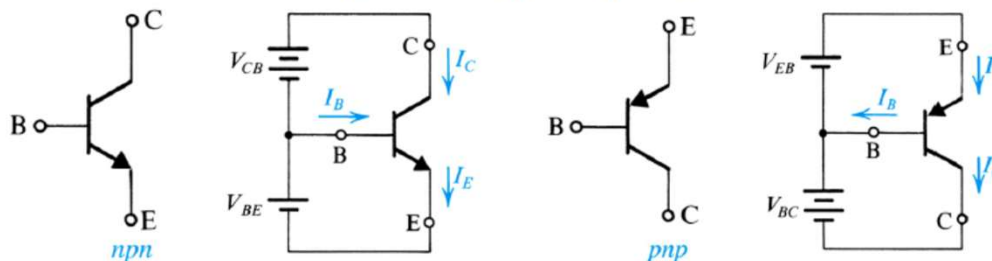□ Negative values of current or voltage mean in opposite polarity (direction)



20

Summary of the BJT current-voltage relationships in the active mode


- ❑ The terminal currents for a BJT in active mode solely depend on the junction voltage of EBJ
- ❑ The ratios of the terminal currents for a BJT in active mode are constant
- ❑ The current directions for *nnp* and *pnp* transistors are opposite

<i>nnp</i> transistor	<i>pnp</i> transistor	
$i_C = I_S e^{v_{BE}/V_T}$	$i_C = I_S e^{v_{EB}/V_T}$	$i_E = i_C + i_B$
$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$	$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$	$\alpha = \frac{\beta}{\beta + 1}$
$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$	$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$	$\beta = \frac{\alpha}{1 - \alpha}$

21

Current-voltage characteristics of BJT


The i_C - v_{CE} characteristics

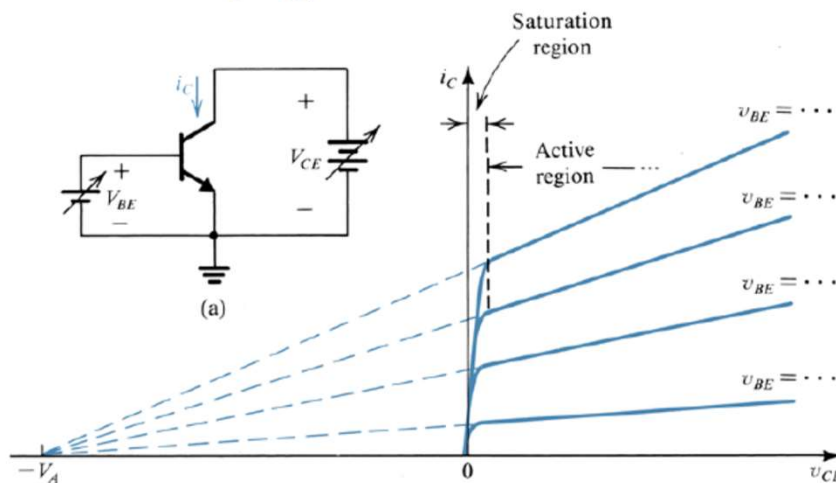

22

BJT operation modes

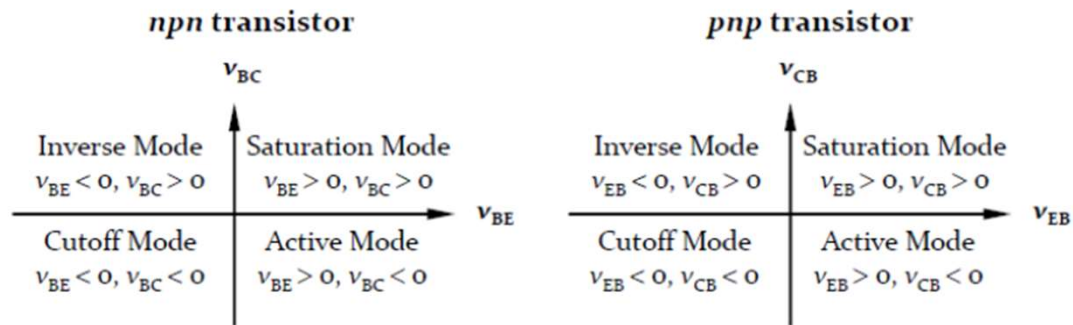- ❑ The BJT operation mode depends on the voltages at EBJ and BCJ
- ❑ The I-V characteristics are strongly nonlinear
- ❑ Simplified models and classifications are needed to speed up the hand-calculation analysis




Applications: as a switch and as an Amplifier

23

BJT voltage amplifier

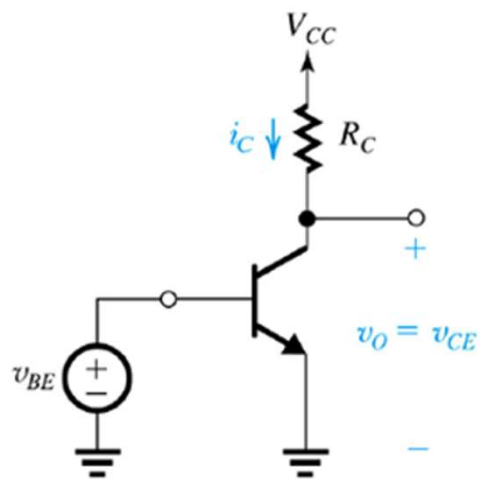- ❑ A BJT circuit with a collector resistor R_C can be used as a simple voltage amplifier
- ❑ Base terminal is used the amplifier input and the collector is considered the amplifier output
- ❑ The voltage transfer characteristic (VTC) is obtained by solving the circuit from low to high v_{BE}



24

■ Cutoff mode:

→ $0 \text{ V} \leq v_{BE} < 0.5 \text{ V}$ and $i_C = 0$

→ $v_O = v_{CE} = V_{CC}$

■ Active mode:

→ $v_{BE} > 0.5 \text{ V}$ and $i_C = I_S \exp(v_{BE}/V_T)$


→ $v_O = V_{CC} - i_C R_C = V_{CC} - R_C I_S \exp(v_{BE}/V_T)$

■ Saturation:


→ v_{BE} further increases

→ $v_{CE} = v_{CEsat} = 0.2 \text{ V}$

→ $v_O = 0.2 \text{ V}$

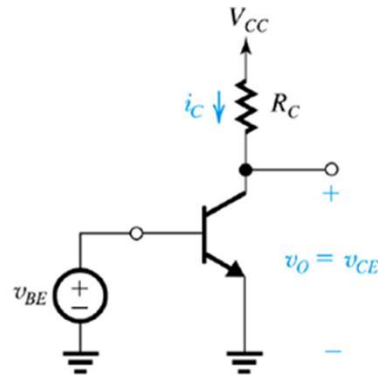

Voltage Transfer Characteristics

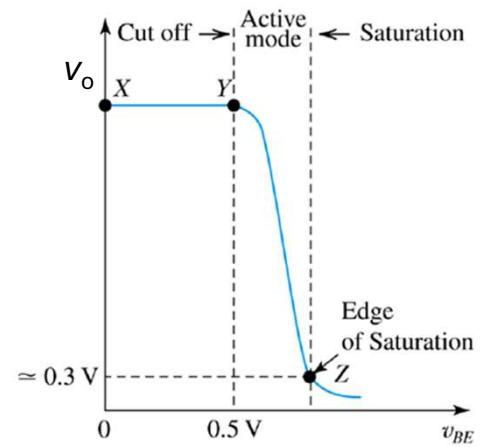

25

Thanks

26