

Certificate

Name: ADYA SINGHAL

Roll No.: 2410110027 Class: Exam No:

Institution: Shiv Nadar Institute of Eminence (SNIoE)

This is certified to be the bonafide work of the student in
the Laboratory during the academic
year 2024 / 2025....

Number of practicals certified out of
in the subject of ECE101.....

Examiner's Signature

Teacher In-charge

Principal

Date:

Institution Rubber Stamp

(N.B: The candidate is expected to retain his/her journal till he/she passes in the subject.)

INDEX

S.R. NO.	NAME OF THE EXPERIMENT	PAGE NO.	DATE OF EXPERIMENT	DATE OF SUBMISSION	SIGNATURE
1	Familiarization with Basic Test Equipment		15/1/25	22/1/25	Cant 23/1/25 A
2	Characteristics of Common Passive Devices		22/1/25	5/2/25	Cant 6/2/25 A
3	Verification of Kirchoff's Law & Superposition		29/1/25	5/2/25	Cant 6/2/25 A
4	Thevenin's & Max ^m Power Transfer Theorem		5/2/25	12/2/25	max Feb 13/25 B
5	Transients in Capacitors & Common RC Filter Circuits		12/2/25	19/2/25	→ max Feb 19/25 CANT work A
6	Series and Parallel Resonance		19/2/25		→ max 19/2/25 Place A B
7	Voltage amplifiers using Op-Amp		12/3/25	19/3/25	→ Cant 26/3/25 B
8	Mini Project - 1		19/3/25	26/3/25	→ Cant 26/3/25 B
9	Mini Project - 2		26/3/25	2/4/25	Cant 2/4/25 B
10	Mini Project - 3		2/4/25	9/4/25	→ max 9/4/25 A P T
11	Mini Project - 5		9/4/25	16/4/25	
12	Mini Project - 6		9/4/25	16/4/25	

Experiment-1

(Familiarization with basic test equipment)

Objective

Familiarization with basic test equipment which will be used throughout the course.

Apparatus Required

DSO, DC Power Supply, Digital Multimeter, bread board, ~~multimeter~~ BNC cables

Theory

i) DSO (Digital storage oscilloscope):

An oscilloscope is an instrument used to produce a display of the two signals applied to the 2 channels (denoted by CH1 & CH2) and analyse the waveform of electronic signals.

It has 2 modes:-

- Y-t mode (Voltage vs time)
- X-Y mode (CH2 voltage vs CH1 voltage)

ii) Digital Voltmeter:

It is used to measure AC & DC voltages & it displays the result digitally.

iii) Function Generator (Wavegen):


It generates various waveforms like sine, square, triangular etc. with these parameters - frequency, amplitude, DC offset.

It provides test signals for the oscilloscope.


Waveform - Ramp Triangular



Waveform - Sine

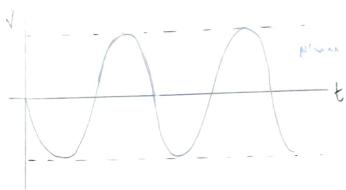

Waveform - Square

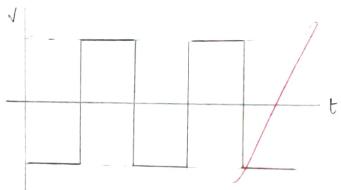

Expt. No. _____

v) BNC cables:

These are coaxial cables used for transmission of electrical signals b/w the oscilloscope and function generator.

v) Breadboard:

It is used for prototyping electronic circuits.

Observations

1) We set the following settings of the wavegen:-

Waveform - Sinusoidal

Frequency - 1 kHz

Amplitude - 4V p-p

DC offset - zero

We observe the signal waveform and note down their types.

2) Trigger settings

Trigger	Run position	Stop position
Auto	Unstable	Frozen
Normal	Frozen	Frozen

3) Measure the peak to peak value of voltage and frequency of the Wavegen output at DSO by the 3 different methods.

i) Method-1: By manually counting no. of divisions along horizontal, vertical axis.

$$V_{\max} = 2 \times 1 \text{ V} = 2 \text{ V}$$

$$V_{\min} = -2 \times 1 \text{ V} = -2 \text{ V}$$

$$V_{pp} = 4 \times 1 \text{ V} = 4 \text{ V}$$

$$\text{Time Period} = 5 \times 200 \mu\text{s} = 1 \text{ ms}$$

$$\text{Freq.} = 1/1 \text{ ms} = 1 \text{ kHz}$$

ii) Method-2: Measuring by using cursors along vertical, horizontal axes

iii) Method-3: By using measurement feature to get direct digital readouts.

Method	V_{\max}	V_{\min}	$V_{\max} - V_{\min}$	V_{pp}	Time Period	Frequency
i)	2 V	-2 V	4 V	4 V	1 ms	1 kHz
ii)	2.1375 V	-1.9875 V	4.125 V	4.0875 V	1.018 ms	982.32 Hz
iii)	1.95 V	-2.15 V	4.1 V	4.1 V	999.96 ms	1 kHz

4) DC Power Supply & Multimeter

Voltage Sources	Company Name	Type	Voltage Range (Display of power supply)		Voltage Range (multimeter readings)		Current Rating
			V_{\max}	V_{\min}	V_{\max}	V_{\min}	
(A)	1	Scientific Variable	32.1 V	30 V	32.4 V	30.4 V	2 A
(C)	2	Scientific Variable	5.8 V	4.4 V	5.79 V	4.42 V	5 A
(B)	3	Scientific Dual, Variable	15.8 V	0 V	15.81 V	0.005 V	1 A
			15.7 V	0 V	-15.8 V	-0.006 V	

Conclusion

We could familiarise ourselves with the basic test equipments through this experiment.

Experiment -2

(Characteristics of Common Passive Devices)

Objective

To obtain the I-V characteristics of common passive devices on the DSO.

Apparatus Required

- i) Resistors
- ii) LDR
- iii) Thermistors
- iv) Different types of diodes
- v) Capacitors
- vi) DSO
- vii) DC Power Supply
- viii) Breadboard
- ix) BNC cables

Theory


i) Resistors

→ They are usually classified according to composition, tolerance and power rating.


→ The resistor is coded by 3-4 coloured bands, 1st and 2nd giving significant digits and the last one giving the number of zeroes.

→ The ideal I-V characteristics of a linear resistor is a straight line passing through the origin and the slope gives the resistance.

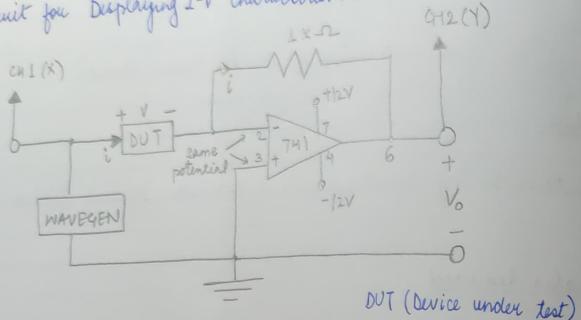
Circuit for Displaying I-V Characteristics:



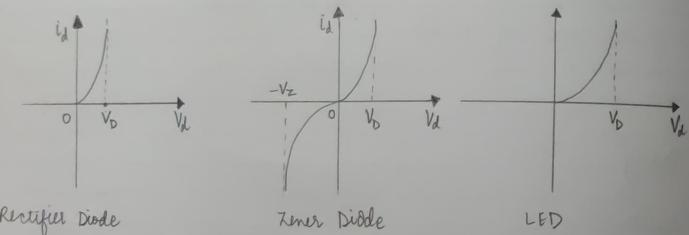I-V Characteristics of different types of diodes:



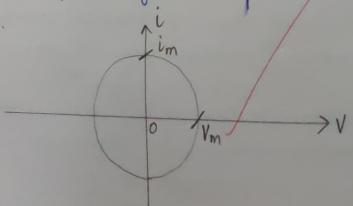I-V Characteristic pattern of Ideal Capacitor:



ii) LDR and Thermistors:

- The light dependent resistor is a linear resistor whose resistance decreases as illumination increases.
- A thermistor is a linear resistor which has temperature dependent resistance. It is of 2 types - NTC & PTC.

iii) Diodes:

- All diodes are non-linear resistors
- The forward bias V_f is 0.5V - 0.6V for rectifier diodes & zener diodes, while LED's of different colors have different values of V_f .

iv) Capacitors:

- They are classified according to the dielectric material used in the fabrication of the capacitor and the range of values varies.

• electrolytic - ($\geq 1\mu F$) - cylindrical body with printed value & polarity indicated by +/-.

Polyester - (0.001-10 μF) - moulded body with either printed or color coded.

ceramic - ($\leq 1\mu F$) - disc shaped body with value printed on the body.

→ The ideal I-V characteristic graph of a capacitor is a circle, indicating 90° phase difference b/w current and voltage.


Expt. No. _____

Observations & Calculations


[Freq. : 1kHz, peak-to-peak value = 1V, offset = 0V]

• Resistors

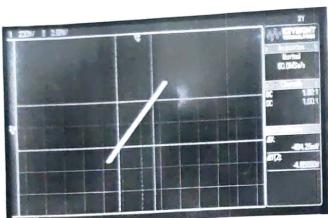
shape of graph = straight line
 slope / inclination = 45°



100 ohm wire wound resistor

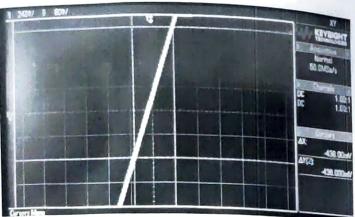

1k-ohm carbon film resistor

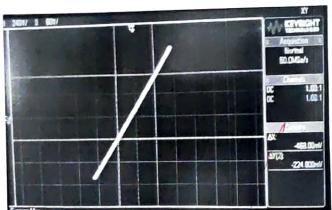

2.2k-ohm carbon film resistor

Component	V (Δx)	V _b (by)	calculated Value
i) 1/4 W 1% 1k-ohm carbon film resistor	438mV	438mV	1kΩ
ii) 1/2 W 5% 2.2k-ohm carbon film resistor	468mV	224mV	2.1 kΩ
iii) 5 W 100 ohm wire wound resistor	404.25mV	4.05 V	99.8 Ω

$$\text{Resistance} = \frac{\Delta V}{\Delta I \times 10^{-3}}$$

Calculations \Rightarrow i) $R = \frac{438}{438 \times 10^{-3}} = 10^3 \Omega$

ii) $R = \frac{468}{224 \times 10^{-3}} = 2.1 \times 10^3 \Omega$

iii) $R = \frac{404.25}{4.05} = 99.8 \Omega$

Teacher's Signature _____

Exp No.

- LDR (Light Dependent Resistor)

	V	V_0	Calculated Value
i) Maximum (Dark)	(Δx) 453.75mV	(Δy) 30mV	$15.125\text{ k}\Omega$

- ii) minimum


	445.5mV	10.875mV	$6.28\text{ k}\Omega$
--	---------	----------	-----------------------

Calculations \Rightarrow i) Maximum = $\frac{V}{I} = \frac{453.75}{30 \times 10^{-3}} = 15.125\text{ k}\Omega$

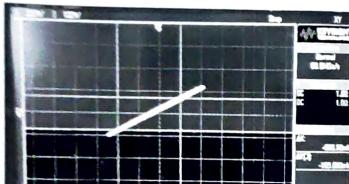
ii) Minimum = $\frac{V}{I} = \frac{445.5}{10.875 \times 10^{-3}} = 6.28\text{ k}\Omega$

- Thermistors


shape of graph: straight line
slope/inclination : 45°




PTC Thermistor (Maximum Temperature)

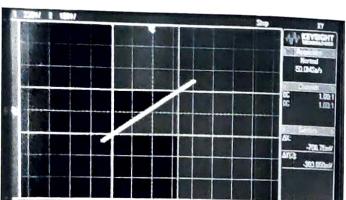

PTC Thermistor (Minimum Temperature)

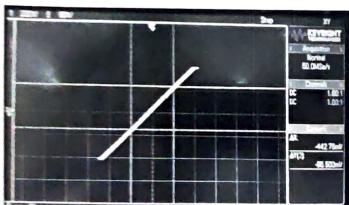

NTC Thermistor (Maximum Temperature)

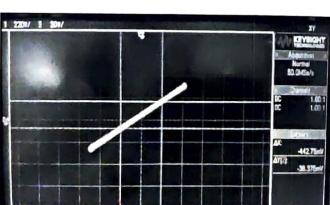

NTC Thermistor (Minimum Temperature)

- i) NTC Thermistor

→ Maximum Temperature
→ Room Temperature

Components	V (Δx)	V_0 (Δy)	Calculated Value
------------	---------------------	-------------------------	------------------

i) NTC Thermistor	442.75mV	95.5mV	$0.0046\text{ }\Omega$
-------------------	----------	--------	------------------------

→ Maximum Temperature	442.75mV	56.75mV	$0.012\text{ }\Omega$
-----------------------	----------	---------	---


- ii) PTC Thermistor

→ Maximum Temperature
→ Room Temperature


ii) PTC Thermistor	665.5mV	193.05mV	$0.0034\text{ }\Omega$
--------------------	---------	----------	--

→ Maximum Temperature	706.75mV	383.05mV	$0.0018\text{ }\Omega$
-----------------------	----------	----------	--


Teacher's Signature _____

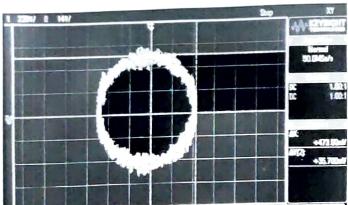

Polyester Capacitor

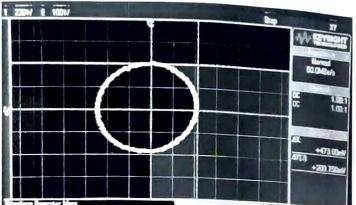

Ceramic Capacitor

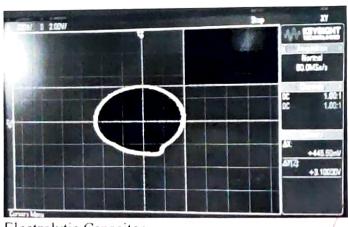

Electrolytic Capacitor

Capacitors

Shape of graph = circle

Frequency = 1KHz

$$X_C = \frac{V_m}{I_m} \quad C = \frac{1}{2\pi f X_C}$$

Component	V_m	I_m	X_C	C
i) 0.01 uF Polyester capacitor	473mV	35.7mV	13.25	0.012 uF
ii) 0.1 uF Ceramic capacitor	473mV	203.75mV	2.32	0.08 uF
iii) 1 uF electrolytic capacitor	445.5mV	3.1V	0.14	1.1 uF

Calculations \Rightarrow i) $X_C = \frac{V_m}{I_m} = \frac{473}{35.7} = 13.25 \quad C = \frac{1}{2\pi f X_C} = 0.012 \mu F$






ii) $X_C = \frac{V_m}{I_m} = \frac{473}{203.75} = 2.32 \quad C = \frac{1}{2\pi f X_C} = 0.08 \mu F$

iii) ~~$X_C = \frac{V_m}{I_m} = \frac{445.5}{3.1} = 0.14 \quad C = \frac{1}{2\pi f X_C} = 1.1 \mu F$~~

Diodes

Peak to Peak value = 4V

offset : As necessary for each case

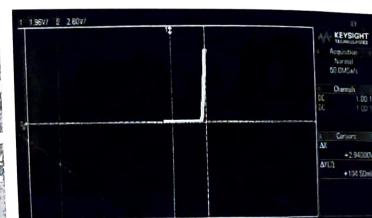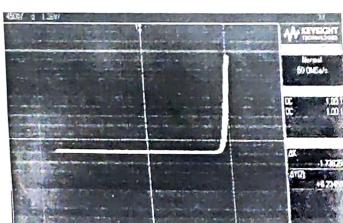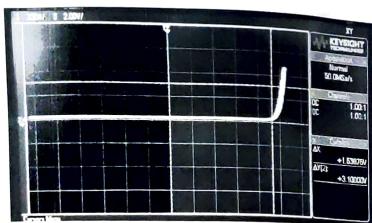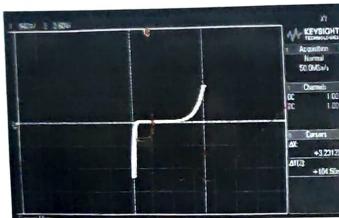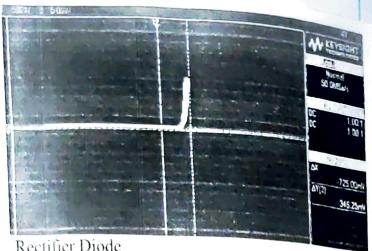Component

i) Rectifier Diode

Component	V_x	V_z
i) Rectifier Diode	7.25mV	-

ii) Zener Diode

ii) Zener Diode	1.23V	1.031 V
-----------------	-------	---------

iii) Red LED

iii) Red LED	1.538 V	-
--------------	---------	---

iv) Green LED

iv) Green LED	1.73825V	-
---------------	----------	---

v) White LED

v) White LED	2.94V	-
--------------	-------	---

Conclusion

Observed V-I graphs of every component on DSO and calculated their ratings using the graph.
It almost matches the ratings on the component.

Experiment - 8

(Verification of Kirchoff's Law and Superposition Principle)

Objective

To learn how superposition can simplify the analysis of linear circuits.


Apparatus Required

- | | |
|--------------------|-----------------|
| i) Power Supply | v) Inductors |
| ii) Breadboard | vi) Resistors |
| iii) Jumper cables | vii) Multimeter |
| iv) Capacitors | |



Theory

The superposition principle states that the response of the circuit to 2 voltage sources is given by the algebraic sum of the responses obtained from 2 separate circuits obtained by keeping only one of the 2 sources and short circuiting the voltage sources.

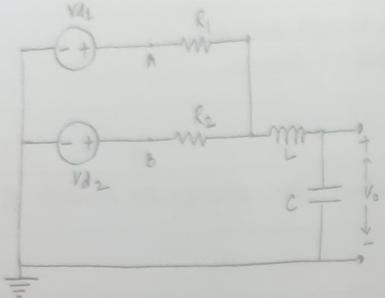Circuit with 2 Independent DC Voltage Sources:



Equivalent circuit for one source

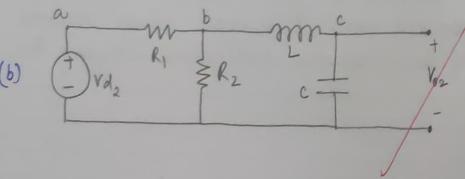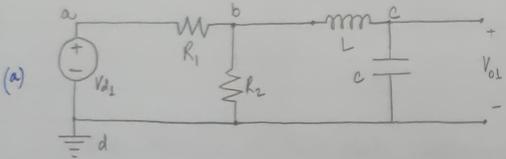

Expt. No. _____ Date _____

Page No. _____

Observations

Table 1: (Both sources together)

V_{d1} (DC source 1)	V_{d2}	V_o
4V	-3V	0.511V

Table 2: (V_{d1} only)

V_{d1}	V_{d2}	V_o
4V	0V	2.074V

Table 3: (V_{d2} only)

V_{d1}	V_{d2}	V_o
0V	-3V	-1.556V

Calculations (Both sources together)

$$+4 - 3kI - 3kI + 3 = 0$$

$$6kI = 7 \quad I = \frac{1}{6k} \quad V_o = \frac{7 \times 3k}{6k} = 3.5V$$


$$V_a - 3 + 3.5 = V_b \Rightarrow V_a - V_b = -0.5$$

$$V_o = 0.5V$$

Teacher's Signature _____

(V_{d1} only)

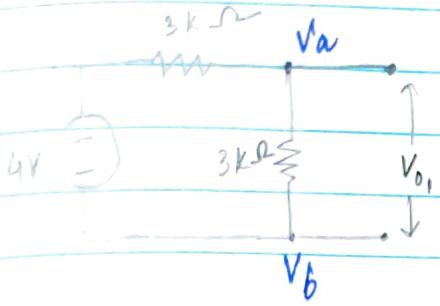⇒ Capacitor behaves as an open circuit in case of DC power supply.



$$V_a - V_b = V_{d_1}$$

$$4 - 3kI - 3kI = 0$$


$$I = \frac{4}{6k}$$

$$V_a + \left(-\frac{4}{6k} \times 3k \right) = V_b$$

$$\Rightarrow V_a - V_b = 2V = V_{d_1}$$

(V_{d2} only)

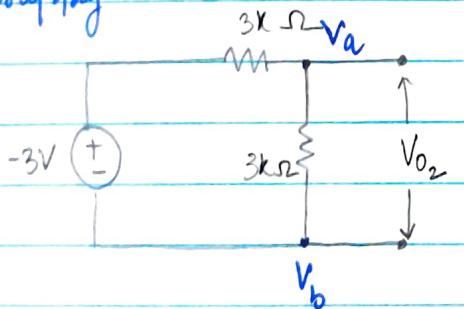⇒ Capacitor behaves as an open circuit in case of DC power supply.



$$V_a - V_b = V_{d_2}$$

$$-3 - 3kI - 3kI = 0$$

$$I = \frac{-3}{2 \times 3k} = \frac{-1}{2k}$$

$$V_a - 3k \left(\frac{-1}{2k} \right) = V_b$$

$$V_a - V_b = -\frac{3}{2} = -1.5V$$

$$V_{d_2} = -1.5V$$

ConclusionTable 4:

	V_{O_1}	V_{O_2}	V_o	$V_{O_1} + V_{O_2}$
Practical	2.074 V	-1.556 V	0.511 V	0.518 V
Theoretical	2 V	-1.5 V	0.5 V	0.5 V

** KCL & KVL Verification using DC Voltage Source.

We modify the previous circuit and obtain a circuit as drawn.
(Fig. 1)

Table 5:


V_{ab}	V_{bc}	V_{cd}	V_{da}	V_{ab}
3.3 V	0.001 V	0.831 V	-0.832 V	-4.13 V

Verify for following loops:

$$i) abcda = V_{ab} + V_{bc} + V_{cd} + V_{da} = 0$$

$$3.3 + 0.001 + 0.831 + (-4.13) = 0.002$$

$$ii) abda = V_{ab} + V_{bd} + V_{da} = 0$$

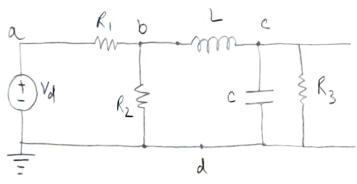Fig. 1

Expt. No. _____

$$3.3 + 0.833 - 4.13 = 0.003$$

iii) $V_{bcda} = V_{bc} + V_{cd} + V_{db} = 0$

$$0.001 + 0.831 + (-0.832) = 0$$

Table 6:

I_{ab}	I_{bc}	$I(C)$	$I(R_3)$	I_{bd}
1.093mA	0.812mA	0A	0.813mA	0.275mA

Verify for node B and node C :

i) node B : $I_{ab} = I_{bd} + I_{bc}$

$$I_{ab} = 1.093 \text{ mA}$$

$$\begin{aligned} I_{bd} + I_{bc} &= 0.812 + 0.275 \\ &= 1.087 \text{ mA} \end{aligned}$$

ii) node C : $I_{bc} = I(C) + I(R_3)$

$$I_{bc} = 0.812$$

$$\begin{aligned} I(C) + I(R_3) &= 0 + 0.813 \\ &= 0.813 \end{aligned}$$

Conclusion

We have verified KCL and KVL with the above experiment.

Experiment -4(Thevenin's And Max^m Power Transfer Theorems)Objective

To prove Thevenin's Theorem and maximum power transfer theorem.

Apparatus Required


- i) Breadboard
- ii) Resistors of different values
- iii) Jumpers
- iv) Capacitor
- v) Diode
- vi) Multimeter
- vii) DSO

Theory


V_o : open circuit voltage

I_{sc} : short circuit current


$$R_o = R_{Th} = \frac{V_o}{I_{sc}}$$

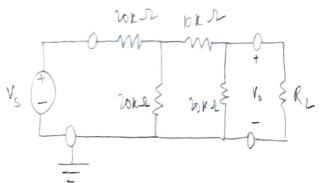


(a) Actual Circuit

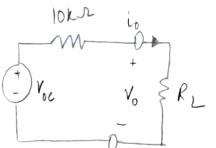


(b) Thevenin Equivalent-

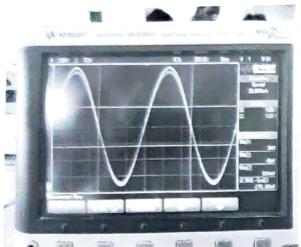


10k-ohm Thevenin circuit

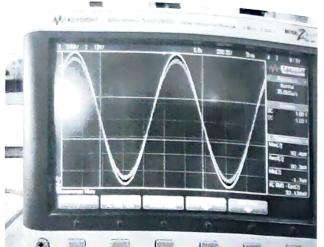


10k-ohm actual circuit

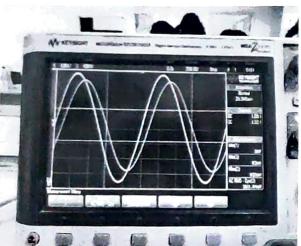

Capacitor Thevenin circuit

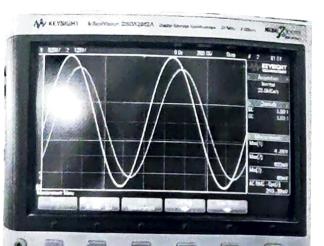

Capacitor actual circuit

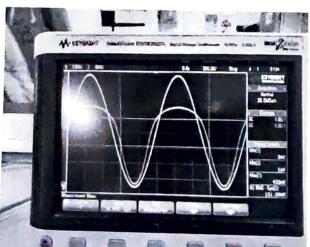

Diode



Expt. No. _____

Observations

Measurement Table for Actual Circuit : (Table 1)



Load Resistance (R_L)	V_o (min.)	V_o (max.)	V_o (rms)	$i_o(rms) =$ $V_o(rms)/R_L$	Power (V_{rms}^2/R_L)
(i) $1k\Omega$	-1.7 mV	92.4 mV	32.136 mV	32.136 μA	$103.27 \times 10^{-9} W$
(ii) $2.2k\Omega$	-4 mV	183 mV	63.842 mV	29.024 μA	$1852.7 \times 10^{-9} W$
(iii) $4.7k\Omega$	-5 mV	326 mV	113.78 mV	24.214 μA	$2754.61 \times 10^{-9} W$
(iv) $10k\Omega$	-1 mV	508 mV	176.38 mV	1763.8 μA	$3110.99 \times 10^{-9} W$
(v) $22k\Omega$	-2 mV	693 mV	240.89 mV	10.95 μA	$2637.74 \times 10^{-9} W$
(vi) $47k\Omega$	-3 mV	840 mV	292.01 mV	6.213 μA	$1814.26 \times 10^{-9} W$
(vii) $100k\Omega$	3 mV	913 mV	317.69 mV	3.1764 μA	$1008.95 \times 10^{-9} W$

Measurement Table : (Table 2)

Load	V_o (min.)	V_o (max.)	V_{rms}
(i) $0.01\mu F$ Capacitor	89 mV	922 mV	273.38 mV
(ii) Diode	10 mV	435 mV	147.72 mV

Do not manipulate
this table

Expt. No. _____

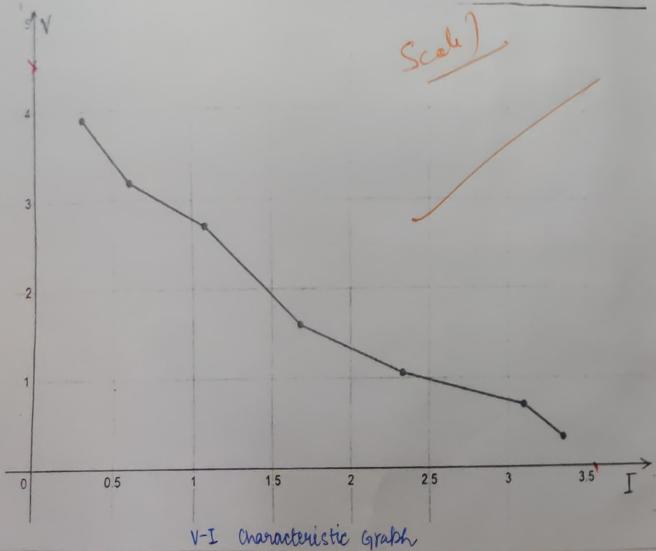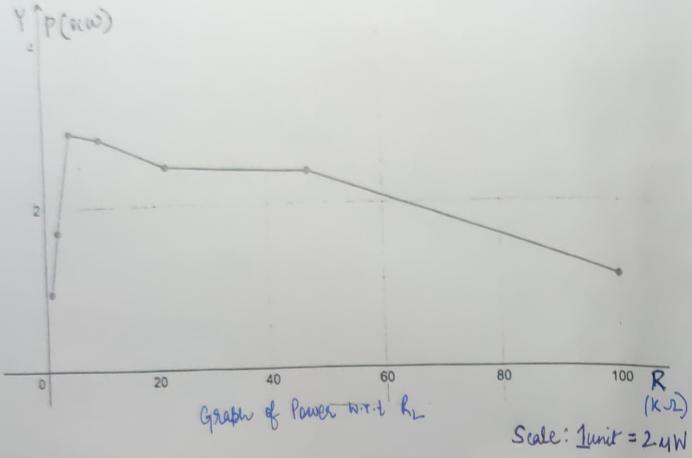

Measurement Table for Thévenin's Circuit: (Table 3)

Load	V_o (min.)	V_o (max.)	V_{RMS}	$I_{transf} = \frac{V_{(RMS)}}{R_L}$	Power ($V_{RMS} * I_{RMS}$)
$R_L = 10\text{k}\Omega$	-5mV	504mV	175.96mV	17.596 28.64A	$3.096 \cdot 19.2 \times 10^{-9}$
Capacitor	83mV	920mV	293.94mV	-	-
Diode	1mV	433mV	151.08mV	-	-

Conclusion

Comparing the value of $R = 10\Omega$ from Table 1 & Table 3:

$$\text{Table 1: } \text{Power} = 3110.99 \times 10^{-9} \text{ W}$$

$$\text{Table 3: } \text{Power} = 3096.192 \times 10^{-9} \text{ W}$$

$$\therefore [P = P_{Th}]$$

From Table 3, we can also conclude that max^m power is transferred when $R = R_L$

$$\Rightarrow [R = R_L]$$

Max
Power
 P_{Th}

Experiment-5(Transients in Capacitors and Convenor.
RC Filter Circuits)Objective

Understanding common RC circuits and observing the transient behaviour in capacitor.

Apparatus Required


- i) 10kΩ and 20kΩ resistors
- ii) 0.001μF capacitors
- iii) Jumper wires
- iv) DSO
- v) Breadboard

Theory - LPFLOWPASS RC FILTER


Gain is maximum at low frequencies, & falls off beyond a cut-off frequency.

$$\text{The Voltage Gain } A = V_o / V_s$$

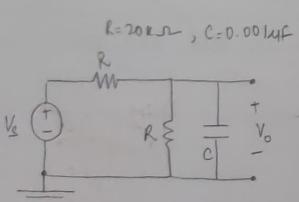A remains constant at a value A_m at low frequencies and falls off as frequency increases. The frequency f_c at which $A = \frac{A_m}{\sqrt{2}}$ is called cut-off frequency. The theoretically expected values are: $A_m = 0.5$ and $f_c = \frac{1}{\pi R C}$



(a) Circuit diagram

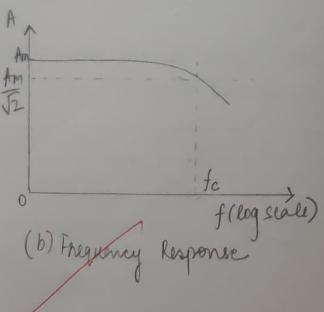

Observations & Calculations - LPF

Frequency = 100 Hz

Amplitude = 4V

offset = 0V

$$A = \frac{V_o}{V_s} = \text{slope of line in x-y mode}$$

Here, $A_m = \frac{\Delta Y}{\Delta X} = \frac{1.15625}{35} = 0.032 \approx 0.5 \therefore \text{Verified}$
 $(A_m)_{\text{practical}} = A_m$

$$\therefore A_m = \frac{0.3444}{\sqrt{2}}$$

$$\text{Now, } \frac{V_o}{V_s} = \frac{A_m}{\sqrt{2}} \Rightarrow V_o = 0.3444 \times 4 \\ = 1.3776 \text{ V pp}$$


The frequency corresponding to $V_o = 1.3776 \text{ V pp}$ is 16.026 kHz

V_s	Gain A_m	f_o	f_c	B.W. ($f_o - f_c$)
4V	0.492	8kHz	16.026kHz	8.026kHz

Theoretically,




$$f_c = \frac{1}{2\pi RC} = \frac{1}{(3.14)(20 \times 10^3)(10^{-9})} = 15.98 \text{ kHz} \approx 16 \text{ kHz} \therefore \text{Verified}$$

$$(f_c)_{\text{practical}} = f_c$$

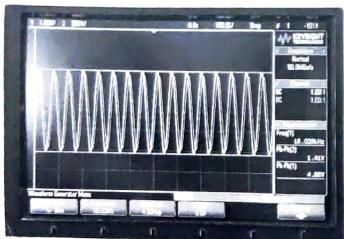


Sinewave - LPF

Expt. No. _____

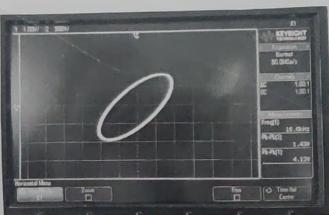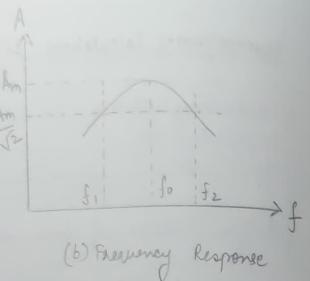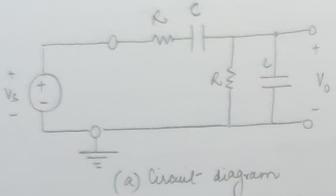

Initial Stage:
ellipse - BPF

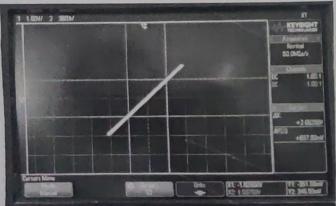

Straight line - BPF

Later

Theory - BPF

BANDPASS RC FILTER

Gain falls off on either side of a centre frequency

Voltage Gain A has a max^m value A_m at centre frequency f_0 , and falls off both at lower and higher frequencies

The theoretical values of f_0 and voltage gain A_m at f_0 are given by:

$$f_0 = \frac{1}{2\pi RC} \quad \text{and} \quad A_m = \frac{1}{3}$$

Observations & Calculations - BPF

The graph starts off as an ellipse in X-Y mode. We change the frequency till we obtain a straight line, indicating V_o & V_s in same phase at $f = 8.292 \text{ kHz}$.

$$A_m = \frac{V_o}{V_s} = \frac{69.50 \times 10^{-3}}{2.0625} = 0.3381$$

$$\frac{A_m}{\sqrt{2}} = 0.23626 \text{ V}$$

$$\frac{V_o}{V_s} = \frac{A_m}{\sqrt{2}} \Rightarrow V_o = 0.2367 \times V_s$$

$$= 0.9468 \text{ V pp.}$$

$$V_o(\text{max.}) = 0.9468 \text{ V pp.}$$


Teacher's Signature _____

10 kΩ resistor


$$T = RC$$

$$T = 10 \times 10^{-5} = 10 \text{ ms}$$

Charging (τ)	Freq.	Amp.	V_o at τ	2τ	3τ	5τ
10 ms	1 kHz	4V	2.425V	3.8V	3.66V	3.8125V
Discharging (τ)	Freq.	Amp.	V_o at τ	2τ	3τ	5τ
10 ms	1 kHz	4V	1.4125V	462.5mV	150mV	0V

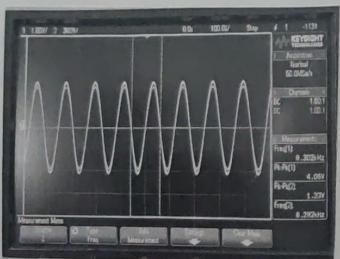

Sinusoidal Wave

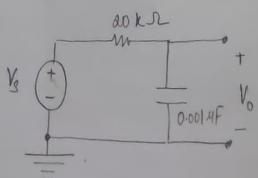

Expt. No. _____

V_s	Gain Am	$f_0(\text{perc})$	f_1	f_2	$B.W(f_2 - f_1)$
4V	0.3381	8.292 kHz	2.5 kHz	28 kHz	25.5 kHz

Theoretically,

$$\text{Am} = \frac{V_o}{V_s}$$

$$\Rightarrow V_o = \frac{1 \times 4}{\sqrt{2}} = 0.933 \approx 0.94V \quad V_o(\text{theor.}) = 0.94V \text{ pp}$$

$$V_o(\text{perc}) \approx V_o(\text{meas.}) \therefore \text{Verified}$$

$$f_0^2 = f_1 f_2$$

$$f_0^2 = (8.292)^2 = 68.75 \quad f_1 f_2 = 70$$

$$f_0^2 = f_1 f_2 \therefore \text{Verified}$$



$$③ f_0 = \frac{1}{2\pi RC} = \frac{1}{2(3.14) \times 20 \times 10^3 \times 10^{-3}} = 7.95 \text{ kHz} \quad f_0(\text{meas.}) = 7.95 \text{ kHz}$$

$$f_0(\text{perc}) \approx f_0(\text{meas.}) \therefore \text{Verified}$$

Theory - Transients in Capacitors

Observe the transient behaviour in capacitor using square wave. Implement the given circuit. Generate square wave voltage (at 1 kHz) $V_s = 4V$ with Min. 0 to Max. 4V using desired offset through function generator (wavegen).

Teacher's Signature _____

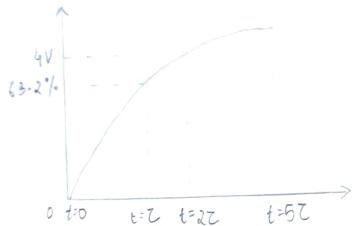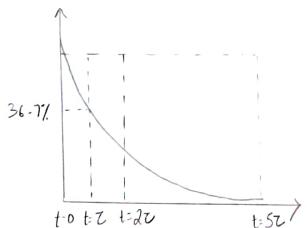ChargingDischargingObservations

Charging and Discharging Observations:

Charging:

$C = R \times C$	Applied freq.	V_o ($t=0$)	V_o ($t=2$)	V_o ($t=2Z$)	V_o ($t=5Z$)	V_s
20μs	1 kHz	25mV	2.5V	3.425V	3.9125V	4V

Discharging:

$C = R \times C$	Applied freq.	V_o ($t=0$)	V_o ($t=2$)	V_o ($t=2Z$)	V_o ($t=5Z$)	V_s
20μs	1 kHz	3.95V	1.425V	550mV	125mV	4V

Conclusion

We understood common RC circuits and observed the transient behaviour in capacitor.

$C = 10 \mu F$
 $R = 10 k\Omega$ → on blank page of previous page
 graph $i-t$ curve
 $i = \frac{V_o}{R + R_o} e^{-\frac{t}{RC}}$