


RL and RC Circuits with DC Charging and Discharging

And

AC Circuits

1

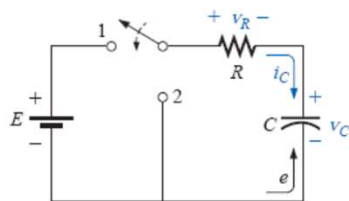TRANSIENTS IN CAPACITIVE NETWORKS: CHARGING PHASE



$$i_C = \frac{E}{R} e^{-t/RC}$$

$$v_C = E(1 - e^{-t/RC})$$

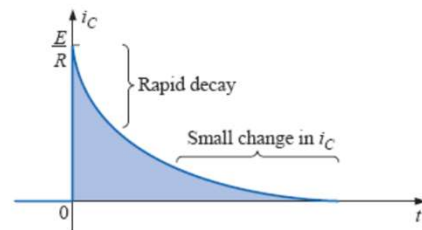


FIG. 10.25
 i_C during the charging phase.

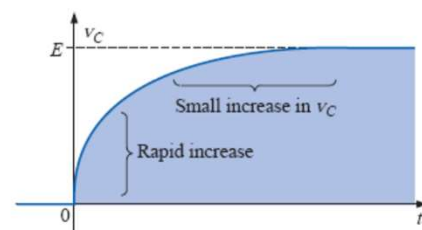


FIG. 10.26

The voltage across a capacitor cannot change instantaneously.

2


TRANSIENTS IN CAPACITIVE NETWORKS: DISCHARGING PHASE

$$i_C = \frac{E}{R} e^{-t/RC} \quad \text{discharging}$$

$$V_C = E e^{-t/RC} \quad \text{discharging}$$


The voltage $V_R = V_C$, and
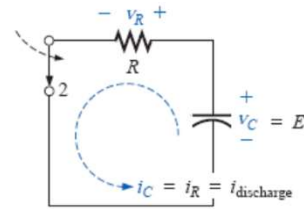
$$V_R = E e^{-t/RC} \quad \text{discharging}$$




3

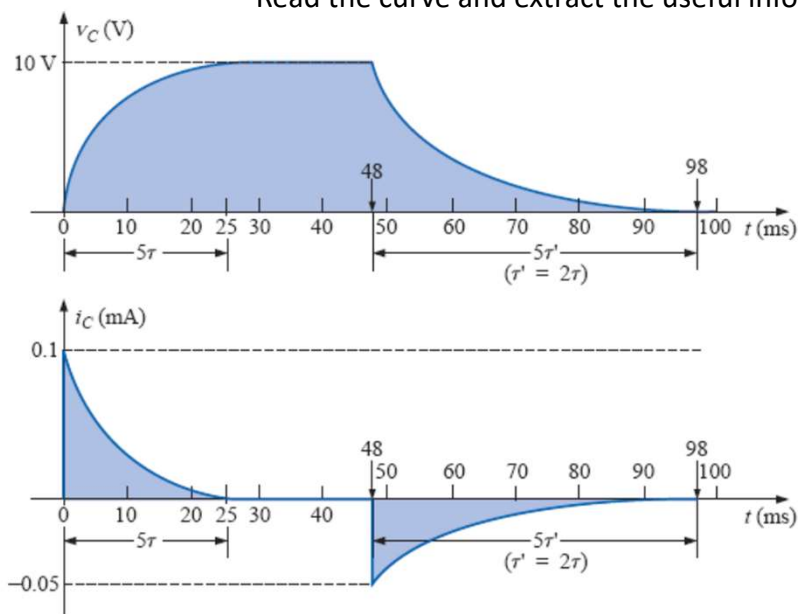Read the curve and extract the useful information




Note: The time constant of charging and discharging may or may not be same.

4

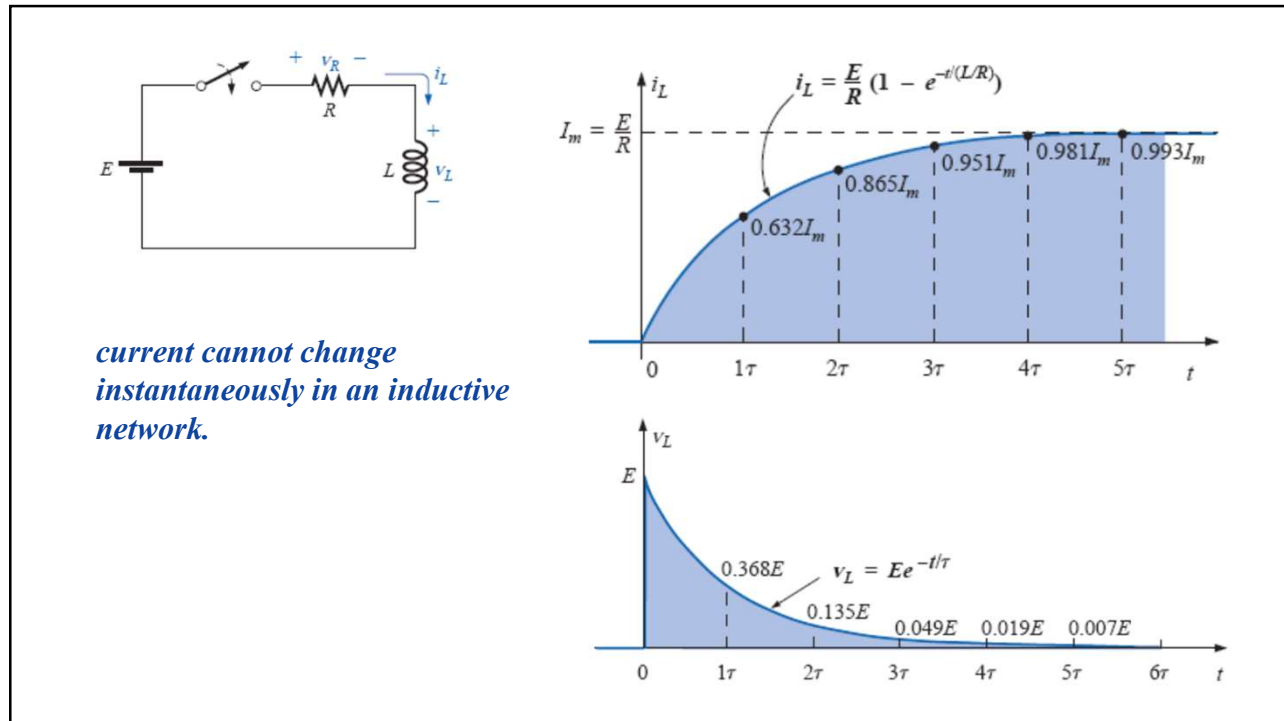

5

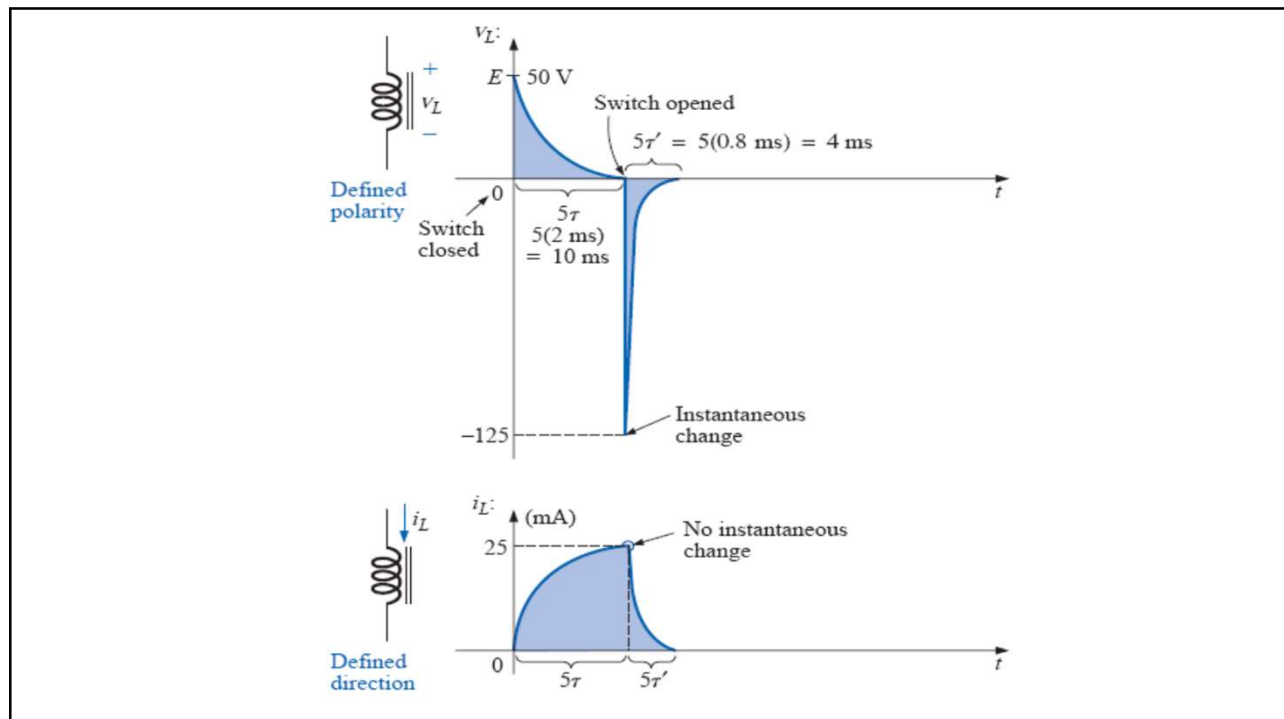

6

RC circuitsTime constant $\tau = RC$ Independent sources to zero, calculate R_{eq} , C_{eq} , τ_{eq} Determine initial conditions $V(0+)$ or $I(0+)$

$$V_c(0+) = V_c(0-)$$

$$I_L(0+) \neq I_L(0-)$$

Determine final condition $V(\infty)$ or $I(\infty)$

Final response

$$V(t) = V(\infty) + [V(0+) - V(\infty)] e^{-t/\tau}$$

Or

$$I(t) = I(\infty) + [I(0+) - I(\infty)] e^{-t/\tau}$$

RL circuitsTime constant $\tau = L/R$ Independent sources to zero, calculate R_{eq} , L_{eq} , τ_{eq} Determine initial conditions $V(0+)$ or $I(0+)$

$$I_L(0+) = I_L(0-)$$

$$V_c(0+) \neq V_c(0-)$$

Determine final condition $V(\infty)$ or $I(\infty)$

Final response

$$V(t) = V(\infty) + [V(0+) - V(\infty)] e^{-t/\tau}$$

Or

$$I(t) = I(\infty) + [I(0+) - I(\infty)] e^{-t/\tau}$$

7


AC Circuits (Steady State)

8


THE SINUSOIDAL VOLTAGE OR CURRENT WAVE FORM

$$i = I_m \sin \omega t = I_m \sin \alpha$$
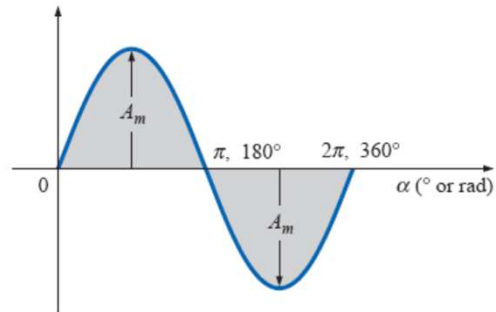
$$e = E_m \sin \omega t = E_m \sin \alpha$$




9

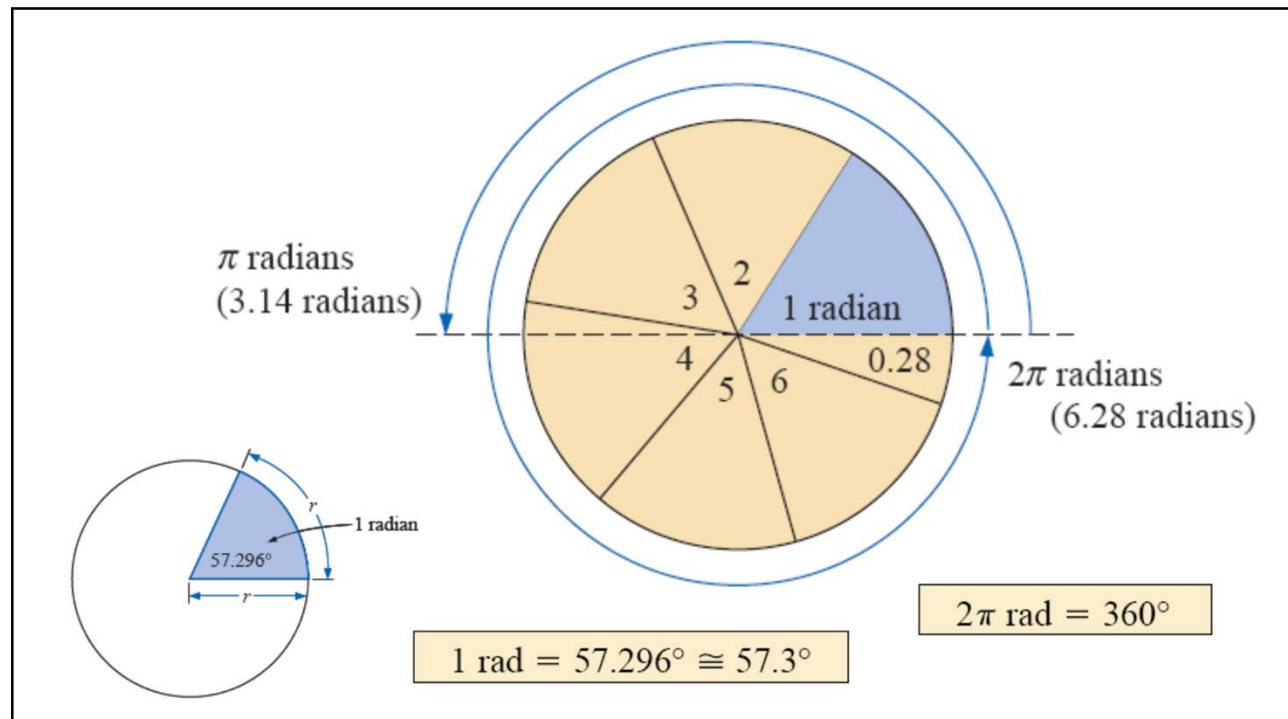

10


Concept of Lead and Lag

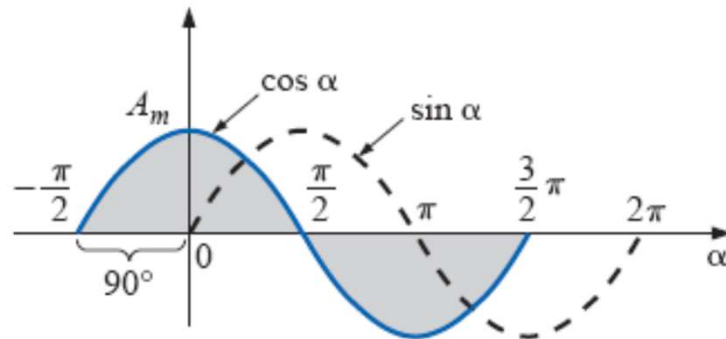

The terms *lead* and *lag* are used to indicate the relationship between two sinusoidal waveforms of the *same frequency* plotted on the same set of axes.

11

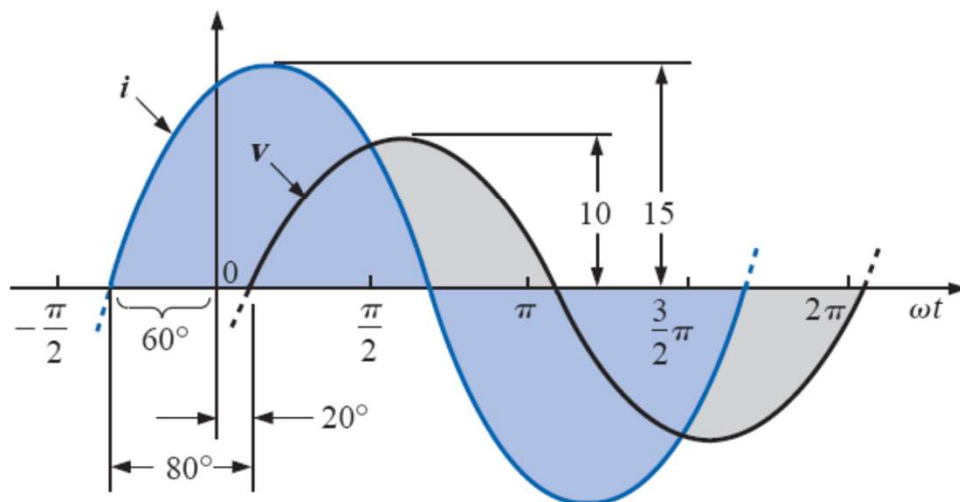***i* leads *v* by 80° , or *v* lags *i* by 80° .**



12

EFFECTIVE (rms) VALUES



$$I_{\text{eq(dc)}} = I_{\text{eff}} = 0.707 I_m$$

I_m = Peak Value (amplitude)

$$I_{\text{eff}} = I_{\text{rms}} = I_m / \sqrt{2}$$

13

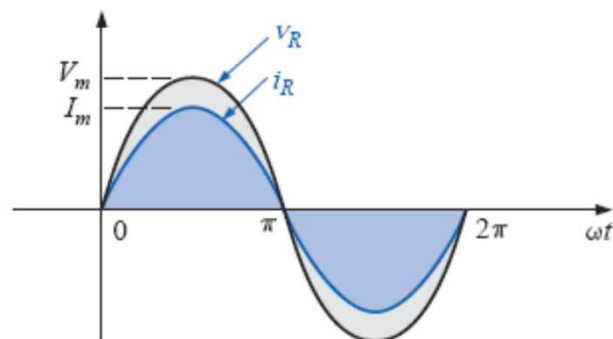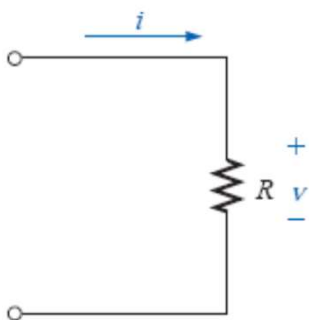
RESPONSE OF R to SINUSOIDAL VOLTAGE OR CURRENT



For a purely resistive element, the voltage across and the current through the element are in phase, with their peak values related by Ohm's law.

14

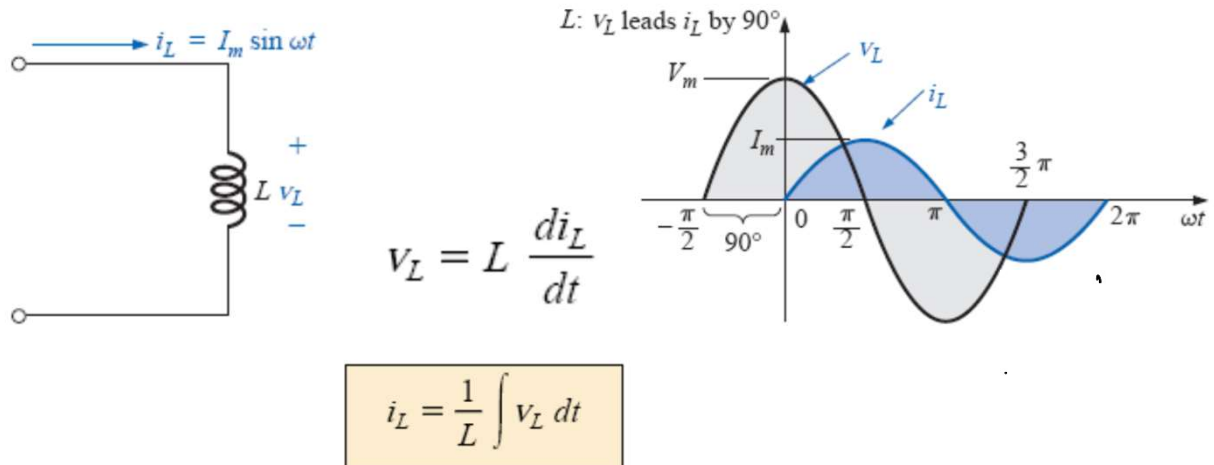RESPONSE OF “L” to SINUSOIDAL VOLTAGE OR CURRENT



For an inductor, v_L leads i_L by 90° , or i_L lags v_L by 90° .

15


Reactance Offered by an Inductor

$$X_L = \omega L \quad (\text{ohms}, \Omega)$$

$$X_L = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega)$$

16

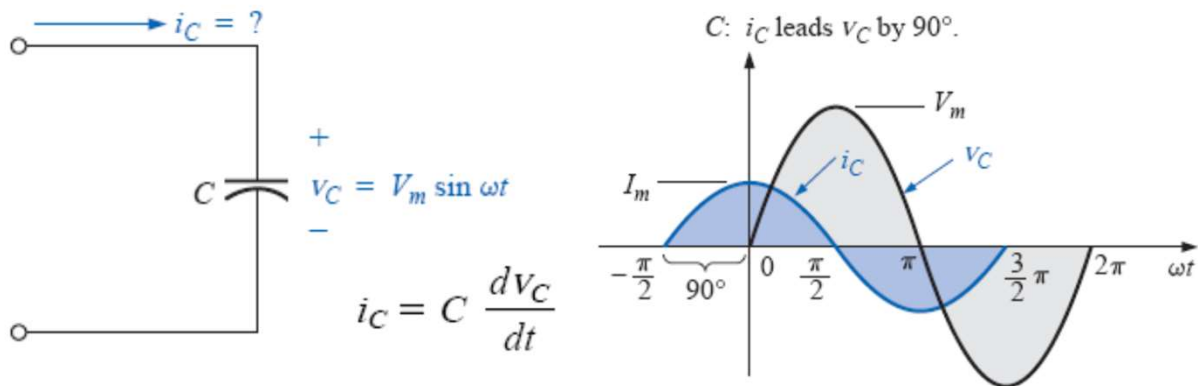RESPONSE OF "C" to SINUSOIDAL VOLTAGE OR CURRENT



$$v_C = \frac{1}{C} \int i_C dt$$

For a capacitor, i_C leads v_C by 90° , or v_C lags i_C by 90° .

17

Reactance Offered by a Capacitor

$$X_C = \frac{1}{\omega C}$$

(ohms, Ω)


$$X_C = \frac{V_m}{I_m}$$

(ohms, Ω)

Like the inductor, the capacitor does *not* dissipate energy in any form (ignoring the effects of the leakage resistance)


18

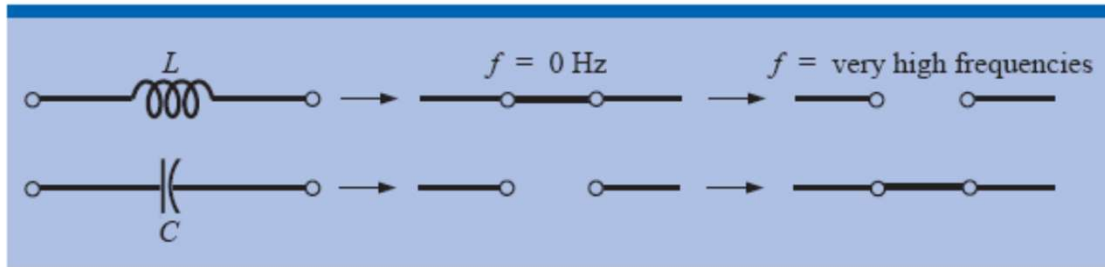Effect of high and low frequencies on the circuit model of an inductor and a capacitor.




19

FREQUENCY RESPONSE OF THE BASIC ELEMENTS

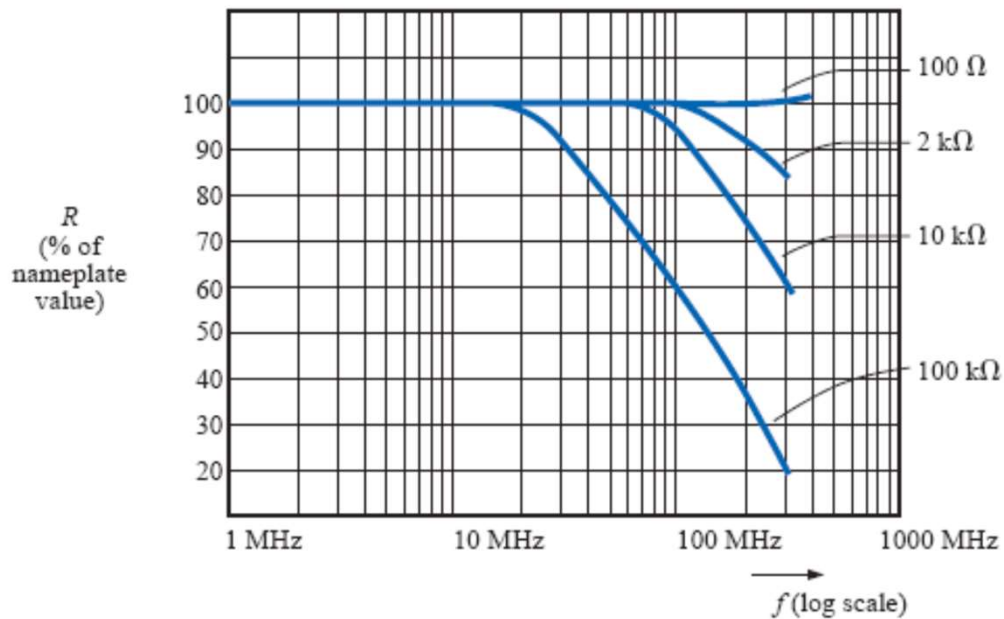

20

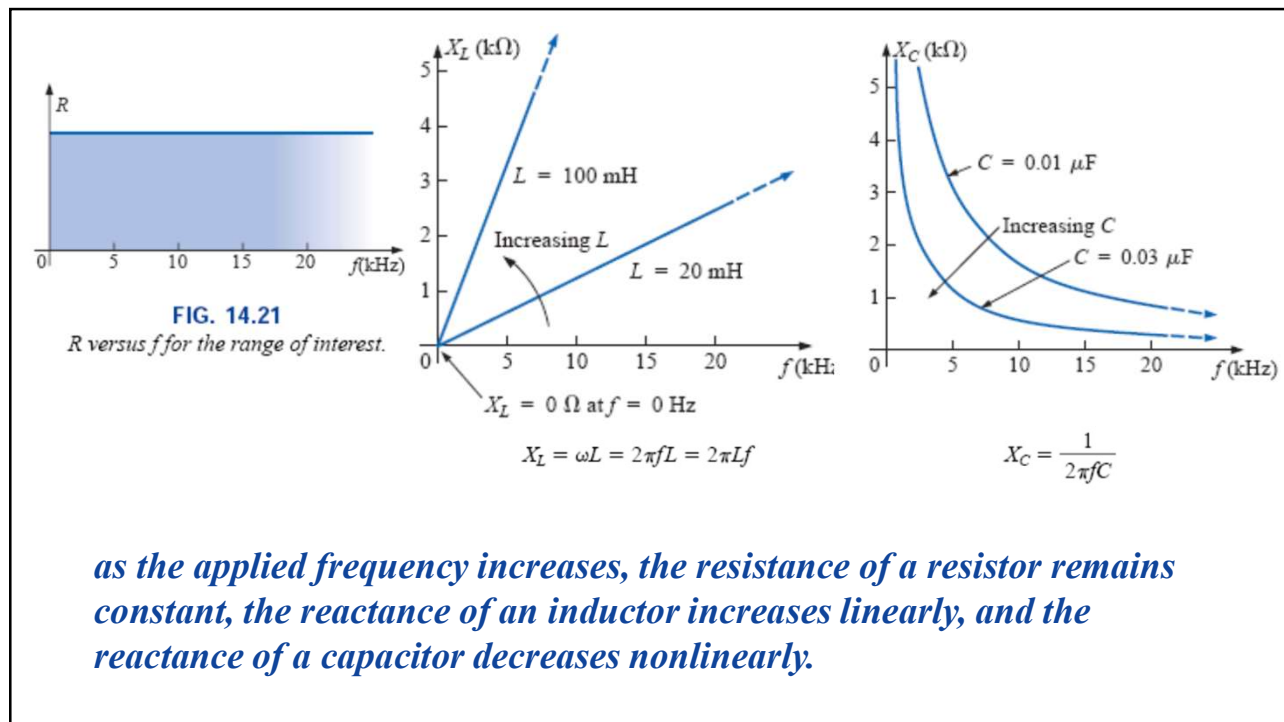

21

Instantaneous Power

$$v = V_m \sin(\omega t + \theta_v)$$

$$i = I_m \sin(\omega t + \theta_i)$$

$$p = vi$$

Using the trigonometric identity

$$\sin A \sin B = \frac{\cos(A - B) - \cos(A + B)}{2}$$

so that

$$p = \left[\overbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}^{\text{Fixed value}} \right] - \left[\overbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}^{\text{Time-varying (function of } t \text{)}} \right]$$

FIG. 14.28
 Determining the power delivered in a sinusoidal ac network.

22

so that

$$p = \left[\overbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}^{\text{Fixed value}} \right] - \left[\overbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}^{\text{Time-varying (function of } t)} \right]$$

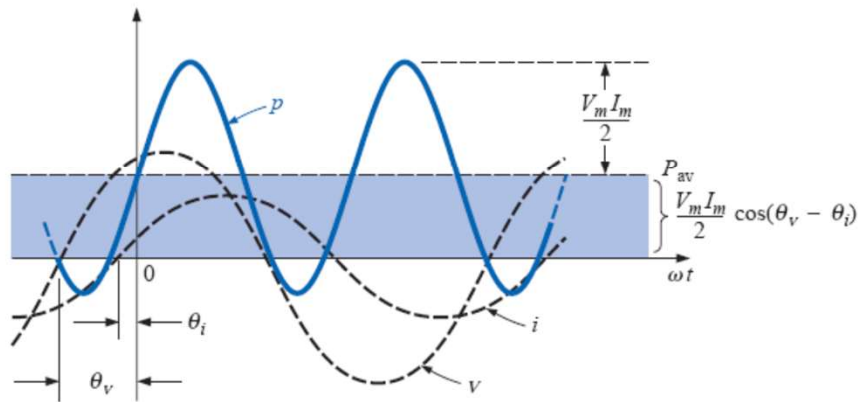


FIG. 14.29

Defining the average power for a sinusoidal ac network.

23

Average power

The average power, or **real power** is sometimes called, the power delivered to and dissipated by the load.

the magnitude of average power delivered is independent of whether v leads i or i leads v .

$$P = \frac{V_m I_m}{2} \cos \theta \quad (\text{watts, W})$$

$$\theta = |\theta_v - \theta_i|$$

$$P = V_{\text{eff}} I_{\text{eff}} \cos \theta$$

$$V_{\text{eff}} = \frac{V_m}{\sqrt{2}} \quad \text{and} \quad I_{\text{eff}} = \frac{I_m}{\sqrt{2}}$$

24

For R

$$P = \frac{V_m I_m}{2} = V_{\text{eff}} I_{\text{eff}} \quad (\text{W})$$

$$I_{\text{eff}} = \frac{V_{\text{eff}}}{R}$$

$$P = \frac{V_{\text{eff}}^2}{R} = I_{\text{eff}}^2 R \quad (\text{W})$$

For L and C

The average power or power dissipated by the ideal inductor (no associated resistance) is zero watts.

The average power or power dissipated by the ideal capacitor (no associated resistance) is zero watts.

25

Thanks

26