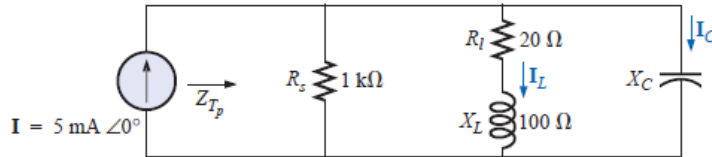


ECE101: Basic Electrical and Electronic Circuits
Tutorial -10

Q. 1. For the networks given below:




- Find the value of X_C at resonance (f_p).
- Find the total impedance Z_{Tp} at resonance (f_p).
- Find the currents I_L and I_C at resonance (f_p).
- If the resonant frequency is 20,000 Hz, find the value of L and C at resonance.
- Find Q_p and the BW. Hint: $BW = f_2 - f_1 = \frac{f_p}{Q_p}$

Q.2. A constant voltage at a frequency of 1 MHz is applied to an inductor in series with a variable capacitor. When the capacitor is set 500 pF, the current has its maximum value while it is reduced to one-half when the capacitance is 600 pF.

Find (i) the resistance, (ii) the inductance, (iii) the Q-factor of the inductor.

Q.3. For the circuit shown below:

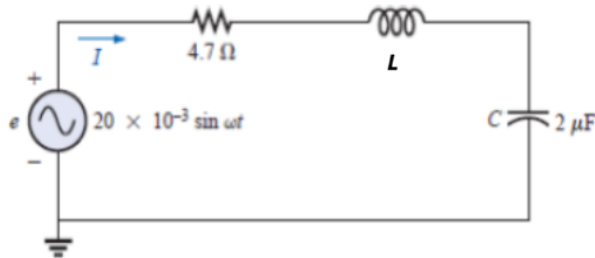


- Find the value of L in milli henries if the resonant frequency is 1800 Hz.
- Calculate X_L and X_C at resonance. How do they compare?
- Find the magnitude of the current I_{rms} at resonance.
- Find the power dissipated by the circuit at resonance.
- What is the apparent power delivered to the system at resonance?
- What is the power factor of the circuit at resonance?
- Calculate the Q of the circuit and the resulting bandwidth.
- calculate half power cutoff frequencies and the power dissipated by the circuit at half power cutoff frequencies.

Hint: For series resonance

$$f_1 = \frac{1}{2\pi} \left[-\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right] \quad f_2 = \frac{1}{2\pi} \left[\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

Q.4.

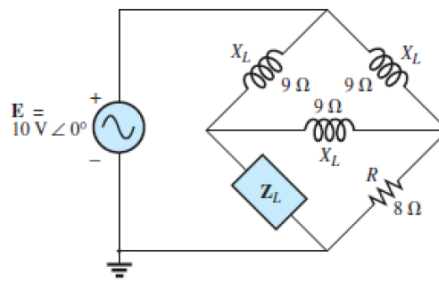

Find load impedance to transfer maximum power and maximum power to the load. [Hint: use delta to star transformation (i.e. Δ -Y)].

Ans: $Z_L = 0.72 \Omega - j 5.46 \Omega$

$P_{\max} = 25.32 \text{ W}$