


ECE Lab Exam




Diode



CBE

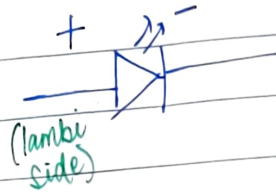

LED

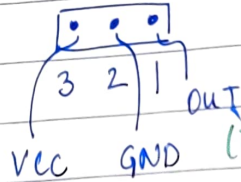


IR Module

(Black LED ki side)


The one closer to tabs
is emitter

Case I:

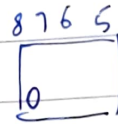


IC

Case II:

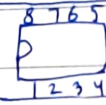

IC

1. (DSO)

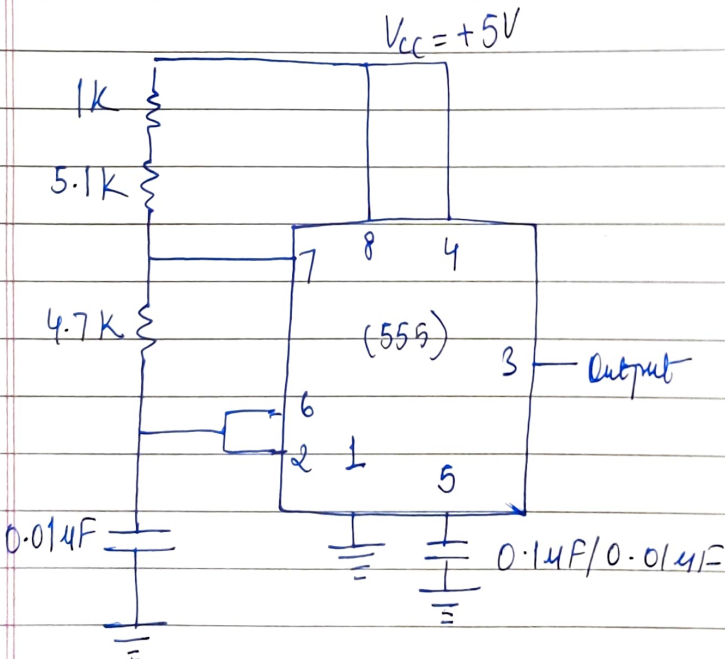

Given: Duty cycle = 0.7

$$0.7 = \frac{R_1 + R_2}{R_1 + 2R_2}$$

$$0.7 R_1 + 1.4 R_2 = R_1 + R_2$$

$$0.4 R_2 = 0.3 R_1$$

$$\frac{R_1}{R_2} = \frac{4}{3} = 1.33$$

$$\frac{R_1}{R_2} = \frac{4}{3}$$

$$R_1 = 5.1 \text{ k}\Omega + 1 \text{ k}\Omega = 6.1 \text{ k}\Omega$$

$$R_2 = 4.7 \text{ k}\Omega$$

$$\frac{R_1}{R_2} = 1.29 \approx 1.3$$


$$6.1$$

$$\frac{4.7}{1.3} = 15.5$$

$$T = 0.693 \times (R_1 + 2R_2) \times C$$

$$= 0.693 \times 15.5 \times 0.01 \times 10^3 \times 10^{-6}$$

$$f = 1/T$$

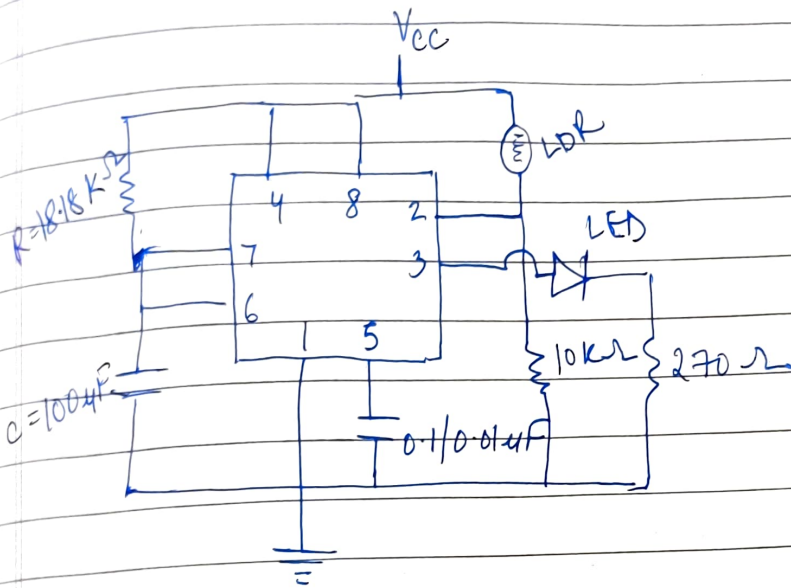

$$2 = 1.1 RC$$

$$R = \frac{2}{1.1 \times 100 \times 10^{-3}}$$


$$= \frac{2}{1.1 \times 10^{-1}} = \frac{2}{0.11} = 18.18 \text{ k}\Omega$$

The formula for ON-Time (T) when 555 Timer IC is used in monostable mode is given by:-

Formula: $T = 1.1 R C$

where, R_{eff} = Eff. Resistance in circuit
 C = Capacitance Value

3. Series Resonant RLC Circuit

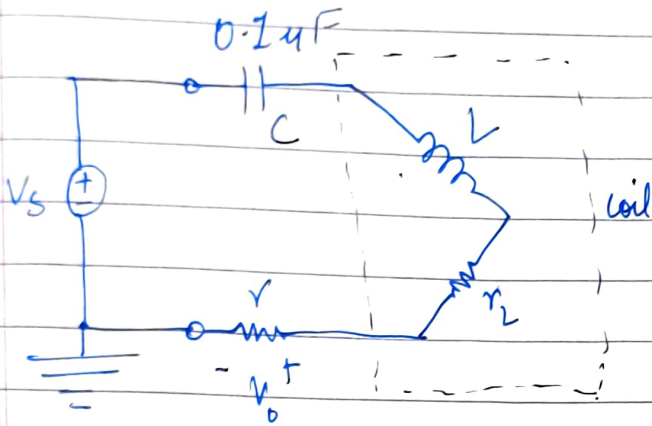

Theory

Resonance is a property that enables one to select a particular freq. out of a signal containing many frequencies.

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

$$\frac{V_o}{V_s} = \frac{r}{r + r_2} = \text{slope} = \frac{\Delta Y}{\Delta X} = (\text{from DSO}) = A_m$$

(find r_2)

$$\frac{A_m}{\sqrt{2}} = x = \frac{CH_2}{CH_1}$$

$$CH_2 = x \times 500$$

$$V_{out} = x \times 500$$

(Scale factor)


Applying V_{in} as 500 mV and V_{out} as 500 u.

Experimental r_2

Measured from multimeter r_2



(DSO)

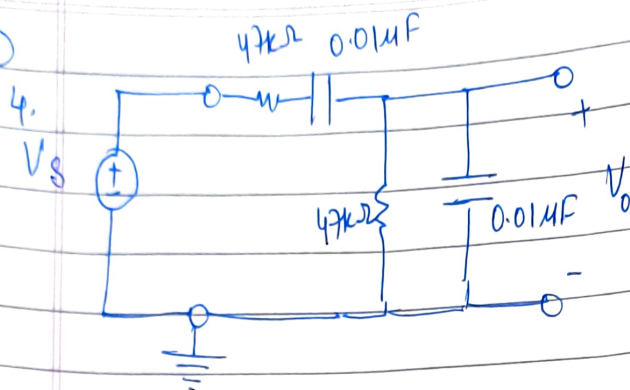

Theoretical Calculations:-

(1) Center frequency (f_0)

$$f_0 = \frac{1}{2\pi RC}$$

$$f_0 = \frac{1}{2\pi \times 47 \times 10^3 \times 10^{-8}} = \frac{10^5}{2\pi \times 47} = 338.8 \text{ Hz}$$

(theor.)

(2) B.W is same as f_0 for this configuration
(theor.)

(3) Gain at center frequency:-

~~$$A_m = \frac{V_o}{V_s} = \frac{47k\Omega}{47k\Omega + 47k\Omega} = \frac{1}{2}$$~~

$$A_m = \frac{1}{3}$$


Observations & Calculations

As per slope of line with \log of f at f_0

$$A_m = \frac{\Delta Y}{\Delta X}$$

(calculate A_m)
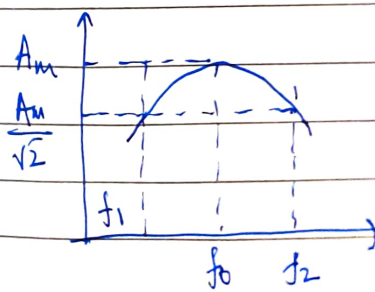
$$\frac{V_o}{V_s} = \frac{A_m}{\sqrt{2}} \rightarrow \text{calculate } V_o(\text{prac})$$




$$V_o (\text{theor.}) = \frac{\frac{1}{3} \times \frac{V_s}{\frac{1}{\sqrt{2}}}}{\frac{1}{\sqrt{2}}} = \frac{V_o}{3\sqrt{2}}$$

V_s	Gain A_m	f_o (prac.)	f_1	f_2	B.W ($f_2 - f_1$)
-------	------------	---------------	-------	-------	---------------------

$$f_o^2 = f_1 f_2$$

5.
Circuit
Supply
multi meters

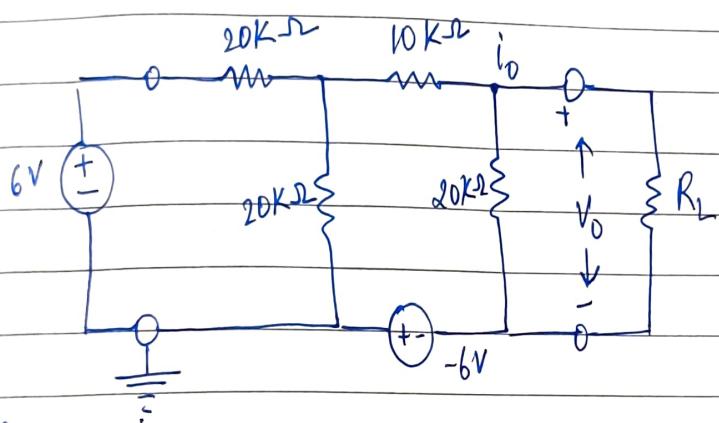

Calculations

$R_{Th} \Rightarrow$

$$R_1 = \frac{20 \times 20}{20 + 20} = 10K\Omega$$

$$R_2 = 10K\Omega + 10K\Omega = 20K\Omega$$

$$R_{Th} = \frac{20 \times 20}{20 + 20} = 10K\Omega$$


~~$V_{Th} = 1V$~~

~~$P_{max} = \frac{V_{Th}^2}{4R_L}$~~

- $V_{Th} \Rightarrow$
- With 6V source only
 $V_{o1} = 2V$
 - With -6V source only
 $V_{o2} = -1V$

} $V_{Th} = 1V$
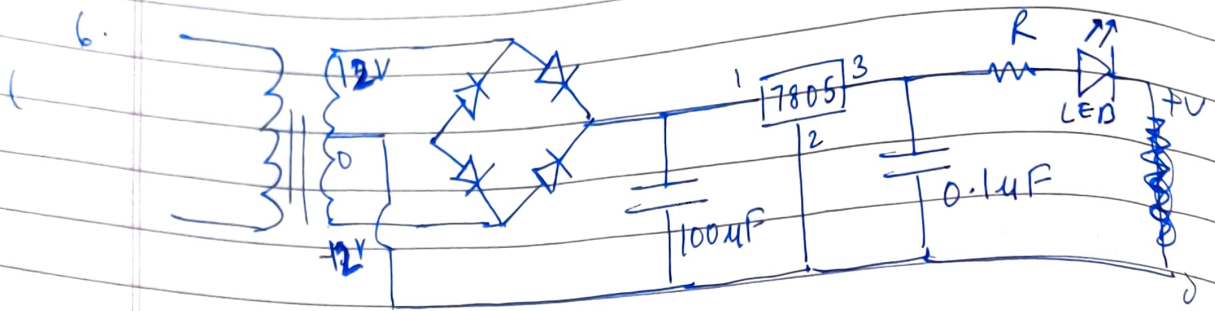
$$P = \frac{V_{Th}^2 \cdot R_L}{(R_{Th} + R_L)^2}$$



Theory:

Step down Transformer reduces the high voltage AC to a lower AC voltage suitable for rectification.

Obs.:

Voltage across rectifier (o/p): (AC-RMS)

Across fve: 5.....

Voltage across regulator 7805 o/p: No edges (Graph is a st. line)



Result:

- The circuit successfully converted 220V AC to 12V DC
- Voltage regulator provided stable output, almost equal to +5V and -5V DC.
- LEDs connected to regular output lit up.

Conclusion:

The exp. demonstrated working of DC Power supply including voltage step down.

7.

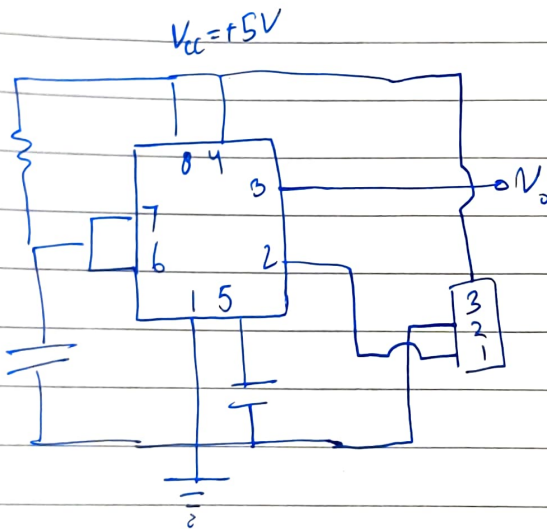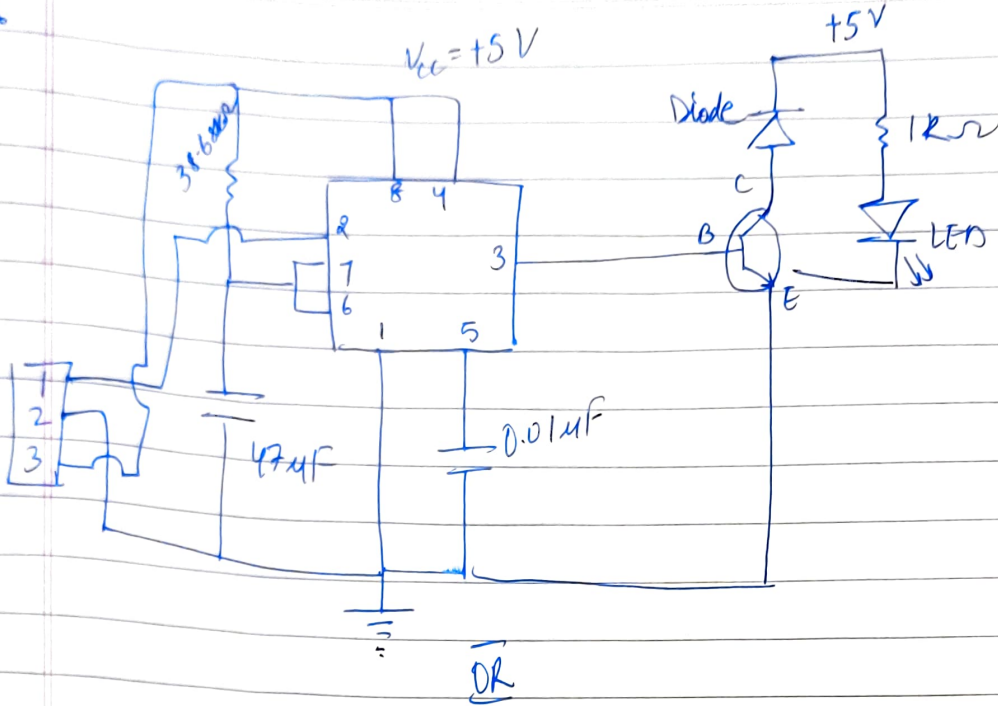


$$T(ON) = \ln 3 R_{eff} C$$

$$R = 38.68k\Omega$$

S. No	C_3 value	Charging cycle Resistor value	ON Time dura ⁿ (theor.)	(prac.)	Mode of Timer IC
Set circuit to get ON Time as 2 sec	47 μF	38.68k Ω	2		Monostable

8.

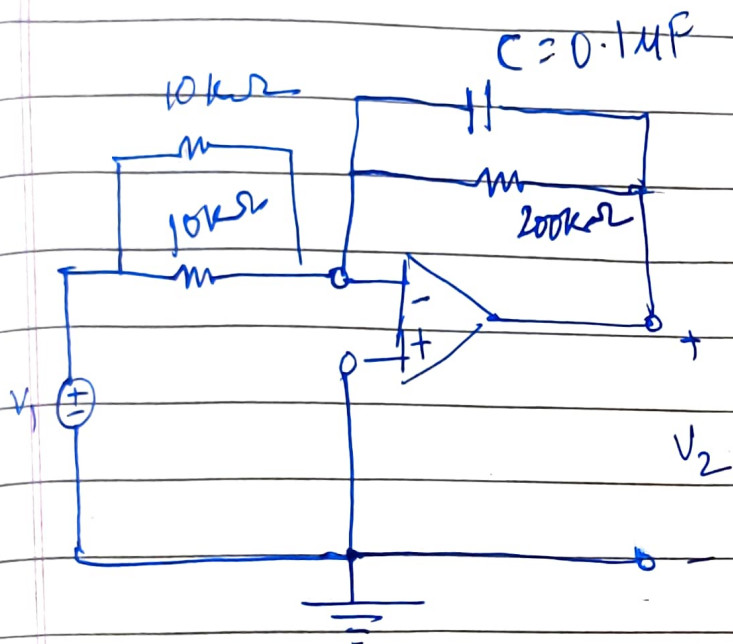

$$\begin{aligned}
 C &= 0.1 \mu F \\
 R_1 &= 10k\Omega \\
 \omega &= 2\pi f \\
 f &= 500Hz
 \end{aligned}$$

Theory:

Waveshape

The output of integrator follows: $V_2 = \frac{-1}{CR_2} \int V_1 dt$

A sq. wave input results in triangular output.

Observations:

Waveshape	V_{1p}	V_{2p}	V_{2p}/V_{1p}	$T/4CR_1$ or $1/\omega CR_1$
-----------	----------	----------	-----------------	------------------------------

Square