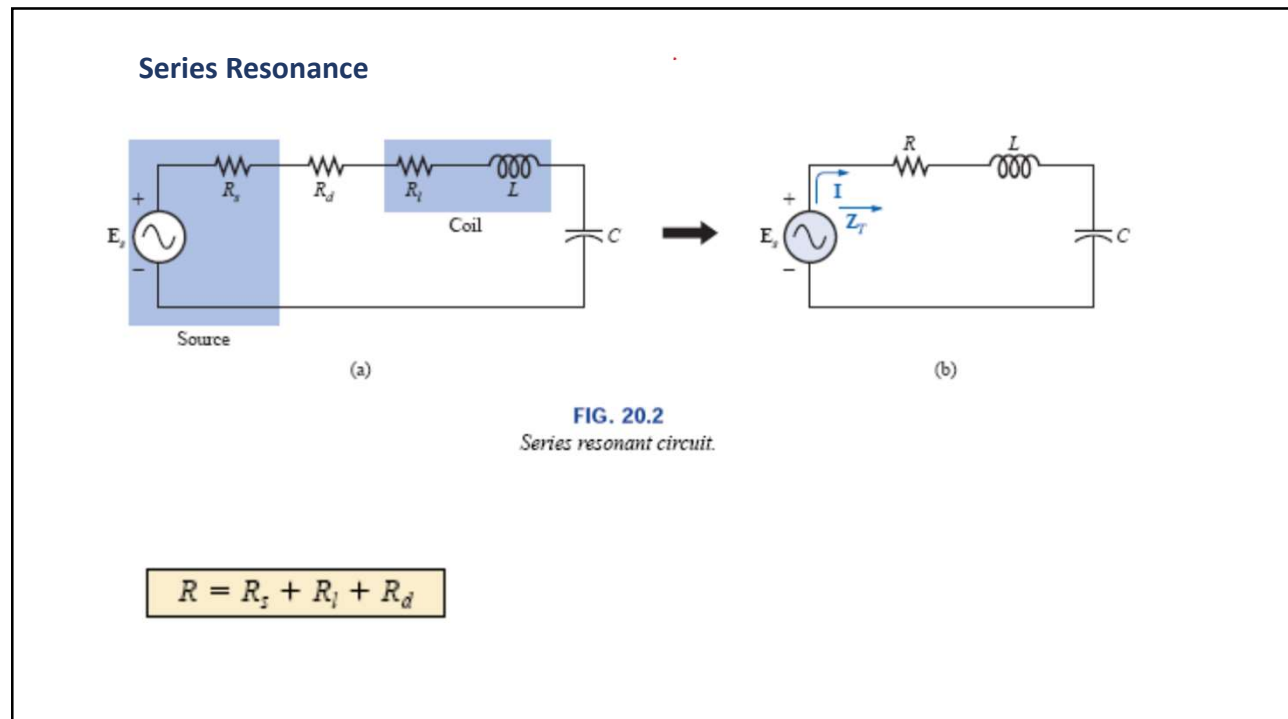


Resonance

SERIES RESONANT CIRCUIT

PARALLEL RESONANT CIRCUIT

1



2

$$X_L = X_C$$

Substituting yields

$$\omega L = \frac{1}{\omega C} \quad \text{and} \quad \omega^2 = \frac{1}{LC}$$

and

$$\omega_r = \frac{1}{\sqrt{LC}}$$

or

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

f = hertz (Hz)
 L = henries (H)
 C = farads (F)

The current through the circuit at resonance is

$$\mathbf{I} = \frac{E \angle 0^\circ}{R \angle 0^\circ} = \frac{E}{R} \angle 0^\circ$$

which you will note is the maximum current for the circuit.

3

Since the current is the same through the capacitor and inductor, the voltage across each is equal in magnitude but 180° out of phase at resonance:

$$\left. \begin{aligned} \mathbf{V}_L &= (I \angle 0^\circ)(X_L \angle 90^\circ) = IX_L \angle 90^\circ \\ \mathbf{V}_C &= (I \angle 0^\circ)(X_C \angle -90^\circ) = IX_C \angle -90^\circ \end{aligned} \right\} \begin{array}{l} 180^\circ \\ \text{out of} \\ \text{phase} \end{array}$$

and, since $X_L = X_C$, the magnitude of V_L equals V_C at resonance; that is,

$$V_{L_s} = V_{C_s}$$

(20.6)

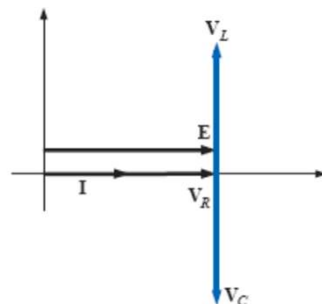


Figure 20.3, a phasor diagram of the voltages and current, clearly indicates that the voltage across the resistor at resonance is the input voltage, and \mathbf{E} , and \mathbf{I} , and \mathbf{V}_R are in phase at resonance.

4

The power triangle at resonance (Fig. 20.4) shows that the total apparent power is equal to the average power dissipated by the resistor since $Q_L = Q_C$. The power factor of the circuit at resonance is

$$F_p = \cos \theta = \frac{P}{S}$$

and

$$F_{p_s} = 1$$

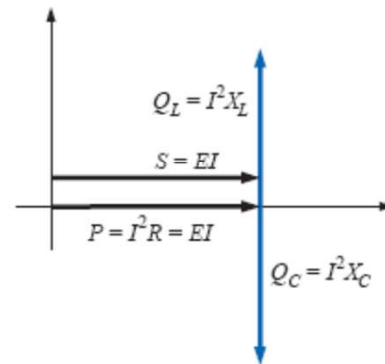


FIG. 20.4

Power triangle for the series resonant circuit at resonance.

5

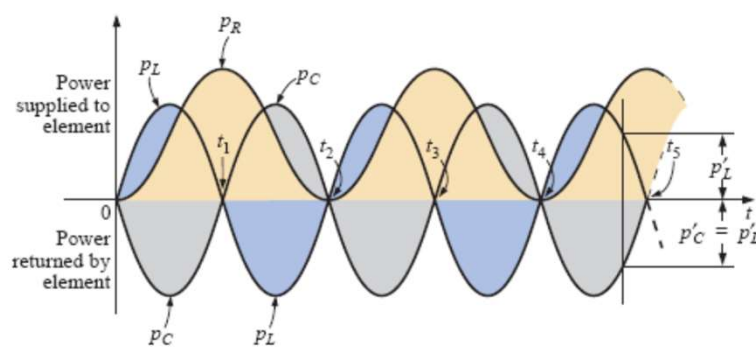


FIG. 20.5

Power curves at resonance for the series resonant circuit.

6

The **quality factor** Q of a series resonant circuit is defined as the ratio of the reactive power of either the inductor or the capacitor to the average power of the resistor **at resonance**;

$$Q_s = \frac{\text{reactive power}}{\text{average power}}$$

$$Q_s = \frac{I^2 X_L}{I^2 R}$$

The lower the level of dissipation for the same reactive power, the larger the Q_s factor and the more concentrated and intense the region of resonance.

$$Q_s = \frac{X_L}{R} = \frac{\omega_s L}{R}$$

If the resistance R is just the resistance of the coil (R_l), we can speak of the Q of the coil, where

$$Q_{\text{coil}} = Q_l = \frac{X_L}{R_l}$$

$$R = R_l \quad (20.10)$$

7

If we substitute

$$\omega_s = 2\pi f_s$$

and then

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

into Eq. (20.9), we have

$$\begin{aligned} Q_s &= \frac{\omega_s L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi}{R} \left(\frac{1}{2\pi\sqrt{LC}} \right) L \\ &= \frac{L}{R} \left(\frac{1}{\sqrt{LC}} \right) = \left(\frac{\sqrt{L}}{\sqrt{L}} \right) \frac{L}{R\sqrt{LC}} \end{aligned}$$

and

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

providing Q_s in terms of the circuit parameters.

8

$$V_L = \frac{X_L E}{Z_T} = \frac{X_L E}{R} \quad (\text{at resonance})$$

and

$$V_{L_s} = Q_s E$$

or


$$V_C = \frac{X_C E}{Z_T} = \frac{X_C E}{R}$$

and

$$V_{C_s} = Q_s E$$

Q_s is usually greater than 1, the voltage across the capacitor or inductor of a series resonant circuit can be significantly greater than the input voltage.

9

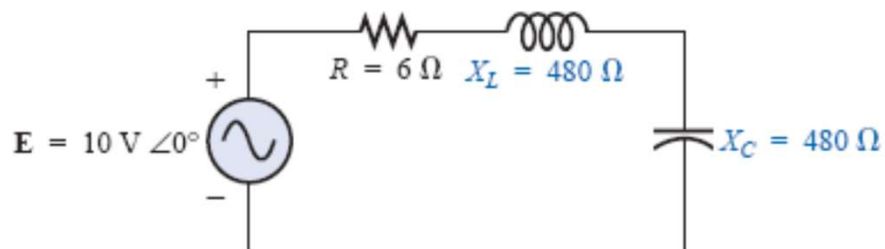

$$Q_s = \frac{X_L}{R} = \frac{480 \, \Omega}{6 \, \Omega} = 80$$

$$V_L = V_C = Q_s E = (80)(10 \, \text{V}) = 800 \, \text{V}$$

10

$f < f_z$: network capacitive; **I** leads **E**
 $f > f_z$: network inductive; **E** leads **I**
 $f = f_z$: network resistive; **E** and **I** are in phase

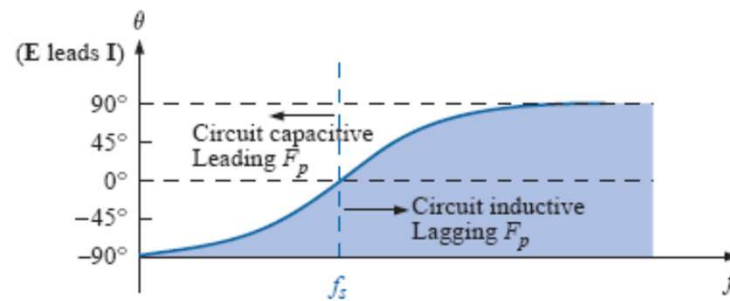


FIG. 20.13

Phase plot for the series resonant circuit.

11

SELECTIVITY

Band frequencies, cutoff frequencies, or half-power frequencies.

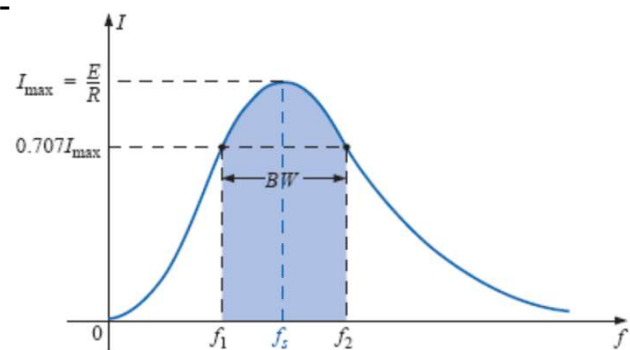


FIG. 20.14

I versus frequency for the series resonant circuit.

The range of frequencies between the f_1 and f_2 is referred to as the **bandwidth** (abbreviated *BW*) of the resonant circuit.

12

$$P_{\max} = I_{\max}^2 R$$

$$\text{and } P_{\text{HPF}} = I^2 R = (0.707 I_{\max})^2 R = (0.5)(I_{\max}^2 R) = \frac{1}{2} P_{\max}$$

Half-power frequencies are those frequencies at which the power delivered is one-half that delivered at the resonant frequency; that is,

$$P_{\text{HPF}} = \frac{1}{2} P_{\max} \quad (20.17)$$

13

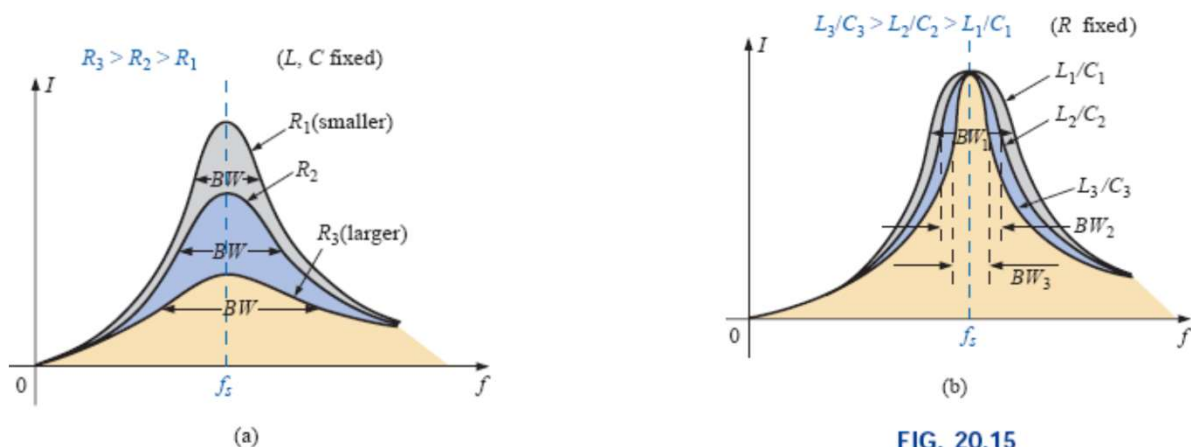


FIG. 20.15

Effect of R , L , and C on the selectivity curve for the series resonant circuit.

A small Q_s , therefore, is associated with a resonant curve having a large bandwidth and a small selectivity, while a large Q_s indicates the opposite.

14

PARALLEL RESONANT CIRCUIT

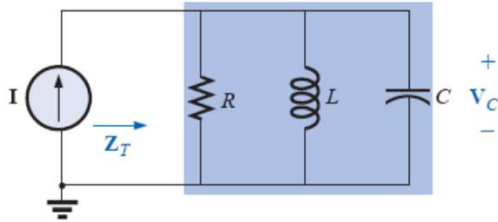


FIG. 20.21

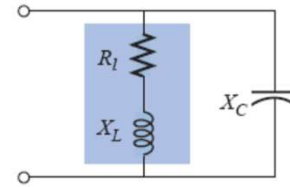
Ideal parallel resonant network.

FIG. 20.22

Practical parallel L-C network.

15

Find a parallel network equivalent (at the terminals) for the series R - L branch

$$\begin{aligned} \mathbf{Z}_{R-L} &= R_l + j X_L \\ \text{and } \mathbf{Y}_{R-L} &= \frac{1}{\mathbf{Z}_{R-L}} = \frac{1}{R_l + j X_L} = \frac{R_l}{R_l^2 + X_L^2} - j \frac{X_L}{R_l^2 + X_L^2} \\ &= \frac{1}{\frac{R_l^2 + X_L^2}{R_l}} + \frac{1}{j \left(\frac{R_l^2 + X_L^2}{X_L} \right)} = \frac{1}{R_p} + \frac{1}{j X_{Lp}} \end{aligned}$$


with

$$R_p = \frac{R_l^2 + X_L^2}{R_l} \quad (20.24)$$

and

$$X_{Lp} = \frac{R_l^2 + X_L^2}{X_L} \quad (20.25)$$


16

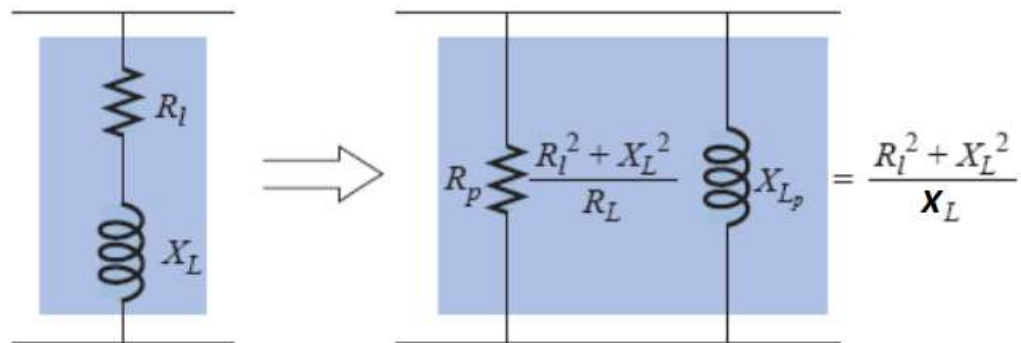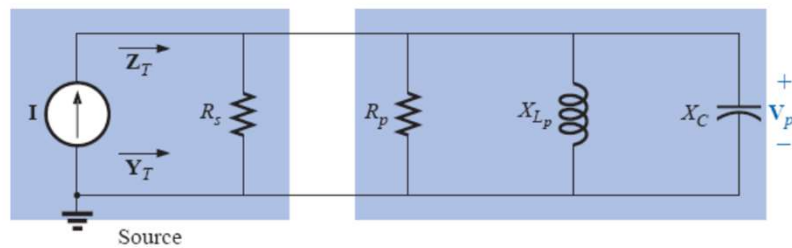**FIG. 20.23**

Equivalent parallel network for a series R-L combination.

17

A practical current source having an internal resistance R_s will result in the network


**FIG. 20.24**

Substituting the equivalent parallel network for the series R-L combination of Fig. 20.22.

If we define the parallel combination of R_s and R_p by the notation

$$R = R_s \parallel R_p \quad (20.26)$$

18

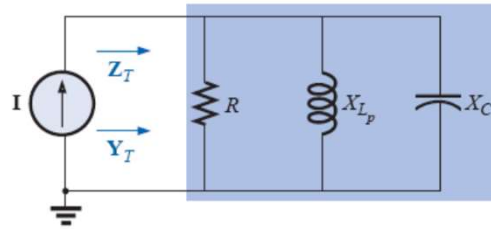**FIG. 20.25**

Substituting $R = R_s \parallel R_p$ for the network of Fig. 20.24.

19

Unity Power Factor, f_p

At resonance $X_{L_p} = X_C$

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_l^2 C}{L}}$$

$$f_p = f_s \sqrt{1 - \frac{R_l^2 C}{L}}$$

where f_p is the resonant frequency of a parallel resonant circuit (for $F_p = 1$) and f_s is the resonant frequency as determined by $X_L = X_C$ for series resonance. Note that unlike a series resonant circuit, the resonant frequency f_p is less than f_s . Since the factor $\sqrt{1 - (R_l^2 C/L)}$ is less than 1, f_p is less than f_s . Recognize also that as the magnitude of R_l approaches zero, f_p rapidly approaches f_s .

20

Maximum Impedance, f_m

$$Z_{T_m} = R \parallel X_{L_p} \parallel X_C$$

If $R = R_i$

$f = f_m$

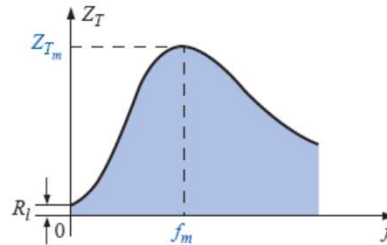


FIG. 20.26

Z_T versus frequency for the parallel resonant circuit.

$$f_m = f_s \sqrt{1 - \frac{1}{4} \left(\frac{R_i^2 C}{L} \right)}$$

Since the voltage across parallel elements is the same,

$$V_C = V_p = IZ_T$$

$$f_s > f_m > f_p$$

21

Cutoff Frequencies:

- ❑ Each cutoff frequency is the frequency at which the input impedance is 0.707 times its maximum value.
- ❑ Since the maximum value is the equivalent resistance R , the cutoff frequencies will be associated with an impedance equal to $0.707R$.

$$Z = \frac{1}{\frac{1}{R} \left[1 + jR \left(\omega C - \frac{1}{\omega L} \right) \right]} = \frac{R}{\sqrt{2}}$$

Magnitude of $Z = \text{Mod } Z$

$$f_1 = \frac{1}{4\pi C} \left[\frac{1}{R} - \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$

$$f_2 = \frac{1}{4\pi C} \left[\frac{1}{R} + \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$

22

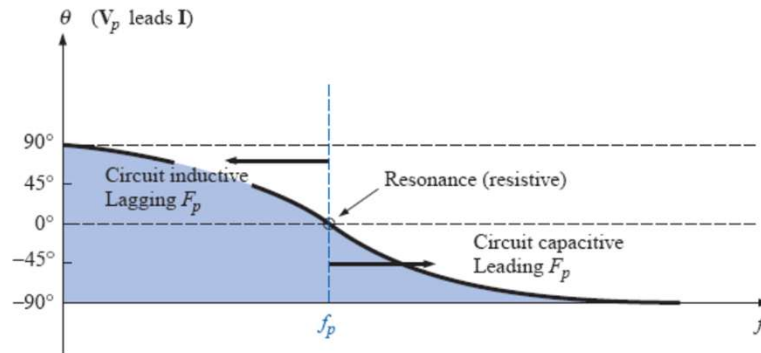


FIG. 20.29

Phase plot for the parallel resonant circuit.

23

Thanks

24