

Oscillator

- Oscillators are circuits that produce periodic waveforms **without any input signal**.
- Any signal generator whose output is periodic can be called an oscillator.
although most frequently the **word oscillator is reserved for a sinusoidal source**.

Applications:


- Local oscillator for radio receivers, mobile receivers, etc
- As a signal generators in the lab for testing.
- Square wave (Clock input) for analog-digital and digital-analog converters: Clock input for CPU, DSP chips.

Oscillator Requirement

An oscillator consists of:

- an amplifier and
- a positive feedback network

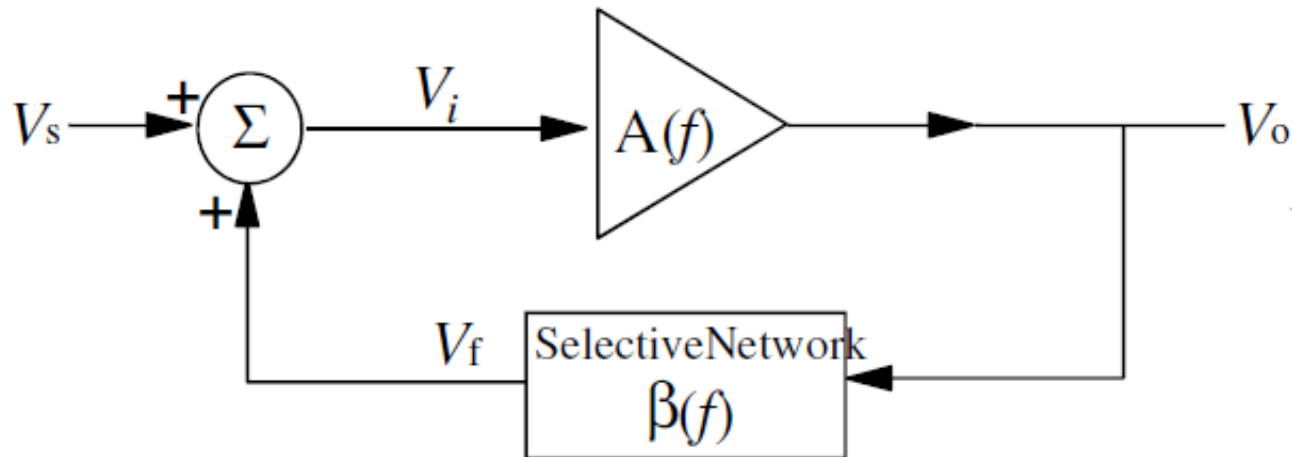1. 'Active device' i.e. Opmp is used as an amplifier.
2. Passive components such as R-C or L-C combinations are used as feedback network.



$$V_o = AV_i = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

Gain with feedback



$$\begin{aligned} A_f &= V_o/V_s \\ &= A / (1 - A\beta) \end{aligned}$$

Feedback Ratio $\beta = V_f/V_o$

If $\beta A = 1$ then $V_o = \infty$; Very high output with zero input.


Positive Feedback

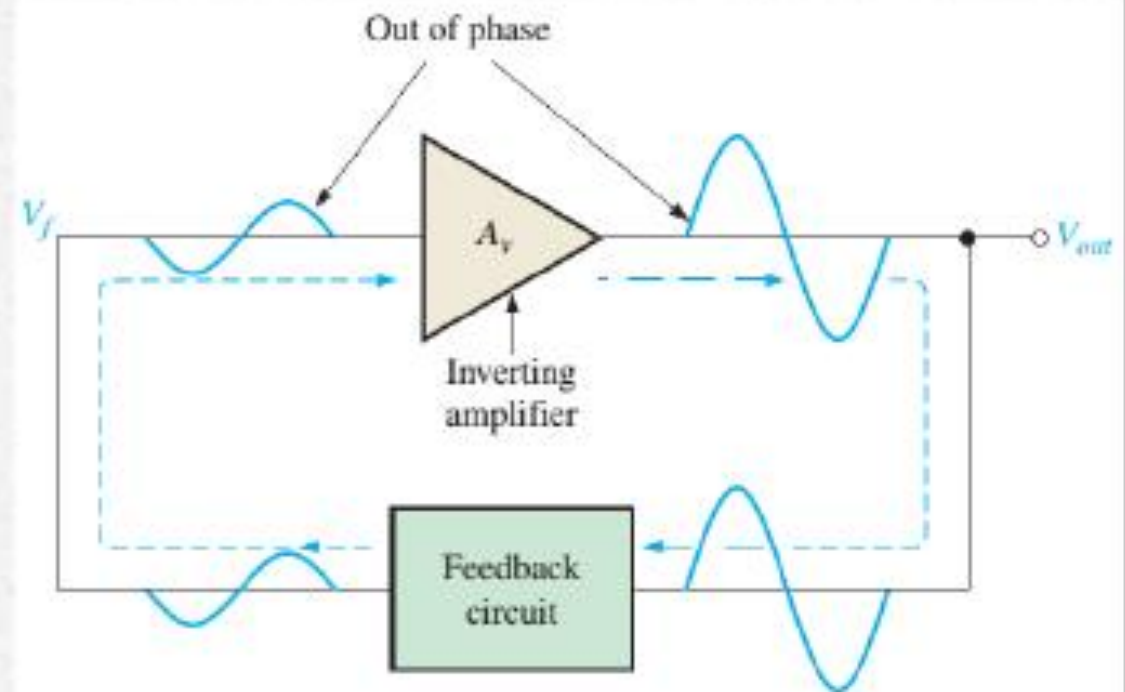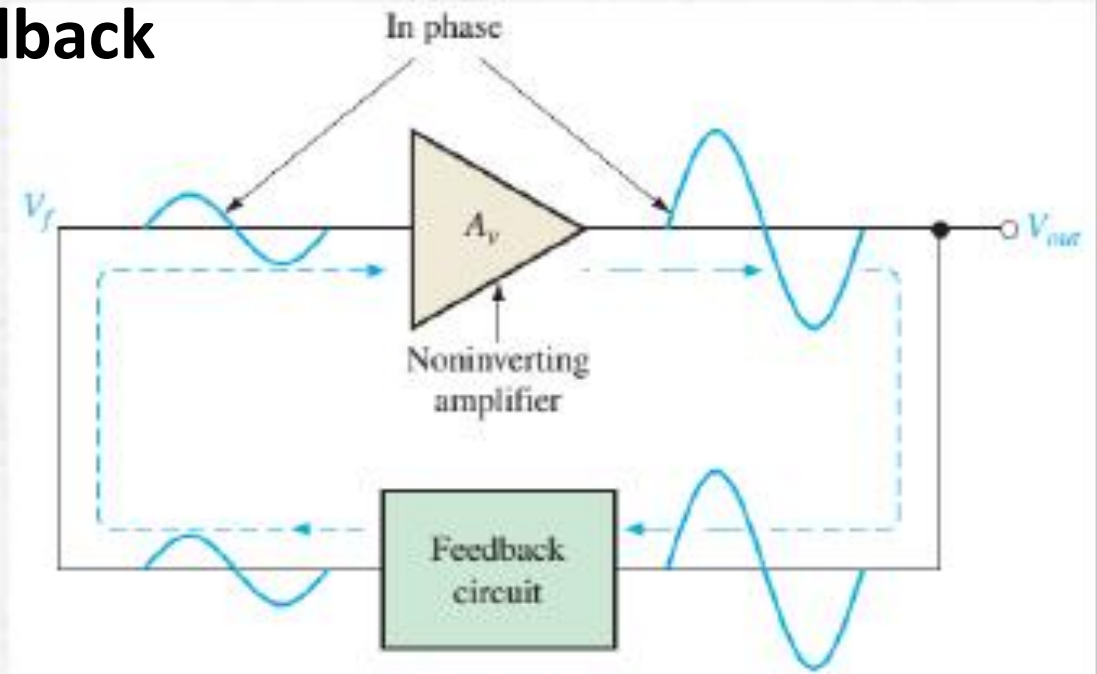- ❑ The in-phase feedback voltage is amplified to produce the output voltage, which in turn produces the feedback voltage.
- ❑ A loop is created in which the signal maintains itself and a continuous sinusoidal output is produced.
- ❑ This phenomenon is called oscillation




BARKHAUSEN CRITERION FOR SUSTAINED OSCILLATIONS

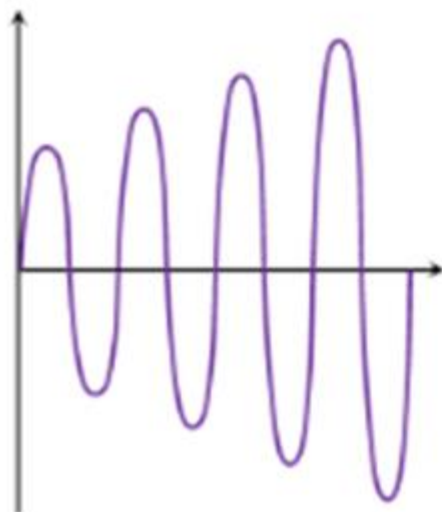
1. Magnitude of the loop gain $(A_v \beta) = 1$,
where, A_v = Amplifier gain and
 β = Feedback gain.
2. Phase shift around the loop must be 360°
or 0° .



(a)

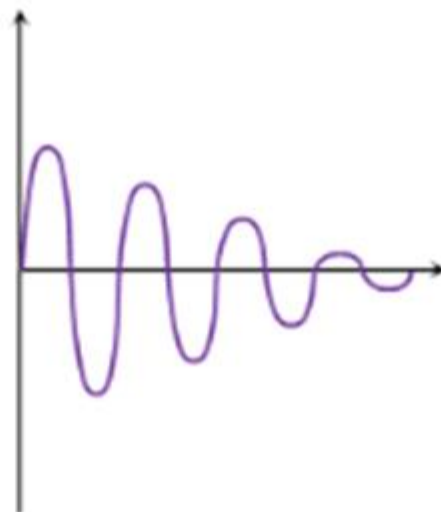

(b)

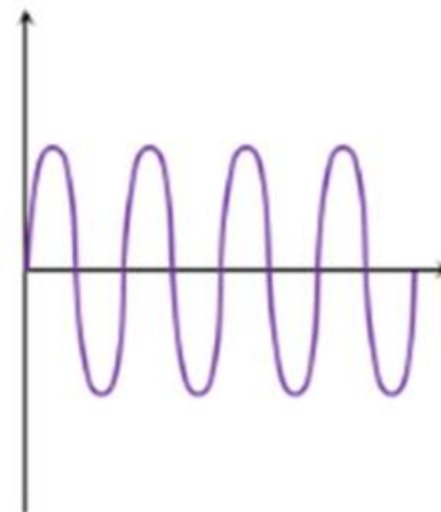

(c)

Figure (a) Increasing Oscillations (b) Decaying Oscillations (c) Constant-Amplitude Oscillations

$$A\beta > 1$$

$$A\beta < 1$$

$$A\beta = 1$$

Type of Oscillators

Oscillators can be categorized according to the types of feedback network used:

- **RC Oscillators: Phase shift and Wien Bridge Oscillators**
- **LC Oscillators: Colpitt and Hartley Oscillators**
- **Crystal Oscillators**

This course is limited to RC phase shift Oscillator only.

Type of Oscillators


Oscillators can be categorized according to the types of feedback network used:

- **RC Oscillators: Phase shift and Wien Bridge Oscillators**
- **LC Oscillators: Colpitt and Hartley Oscillators**
- **Crystal Oscillators**

This course is limited to RC phase shift Oscillator only.

RC Oscillators: Phase shift Oscillator

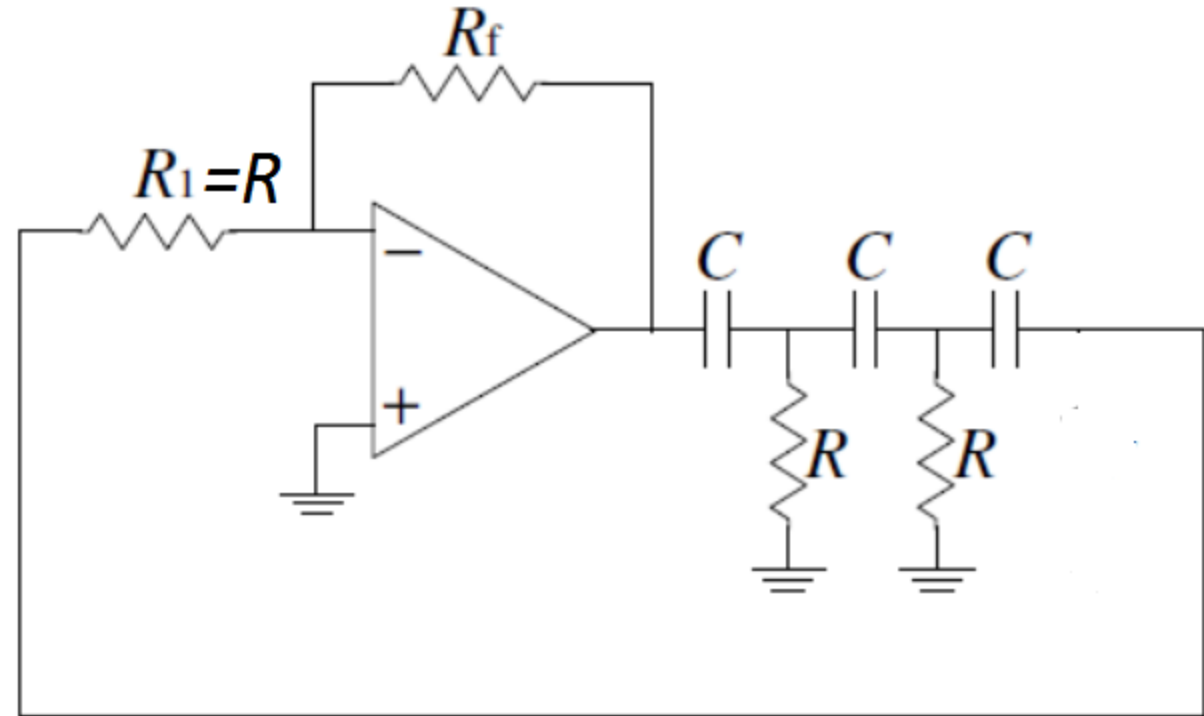- Use of an inverting amplifier.
- The additional 180° phase shift is provided by an RC ladder network.
- It can be used for very low frequencies and provides good frequency stability.



RC Oscillators: Phase shift Oscillator


As inverting is virtual ground. RC phase shift circuit can be considered as follows

At node V_2

$$V_2 = V_o + I_3 Z_c = V_o + \frac{I_3}{j\omega C}$$


But $I_3 = \frac{V_o}{R}$
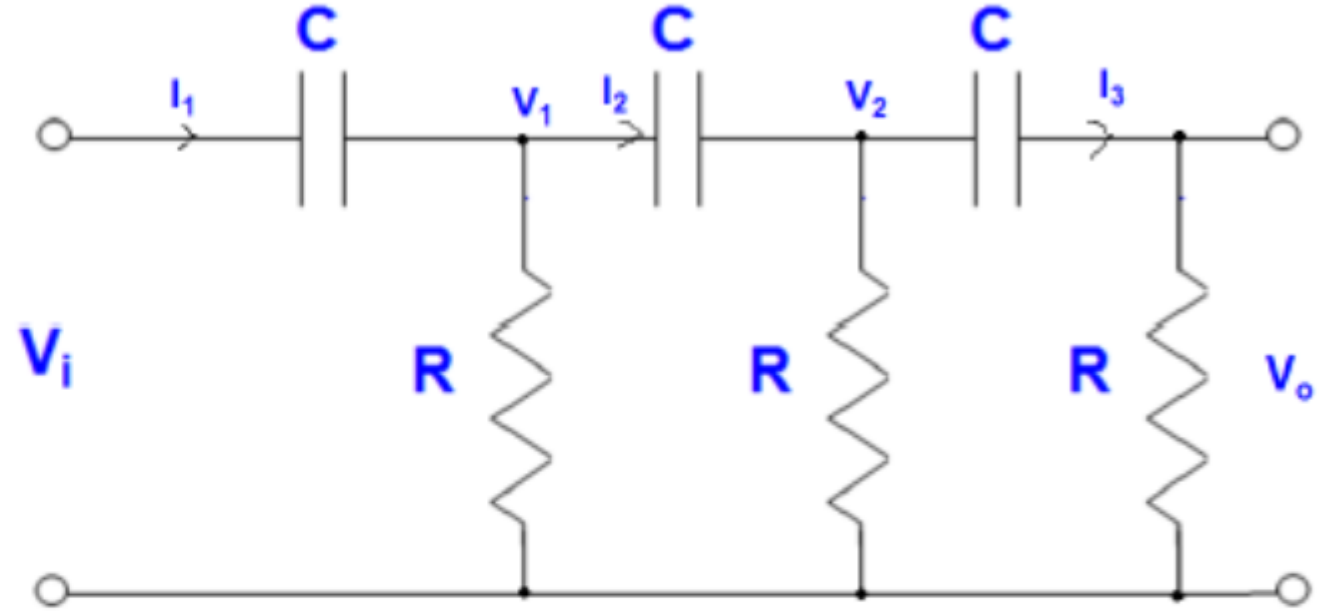
$$V_2 = V_o \left(1 + \frac{1}{j\omega CR}\right)$$



$$I_2 = I_3 + \frac{V_2}{R} = \frac{V_o}{R} + \frac{V_o}{R} \left(1 + \frac{1}{j\omega CR}\right)$$
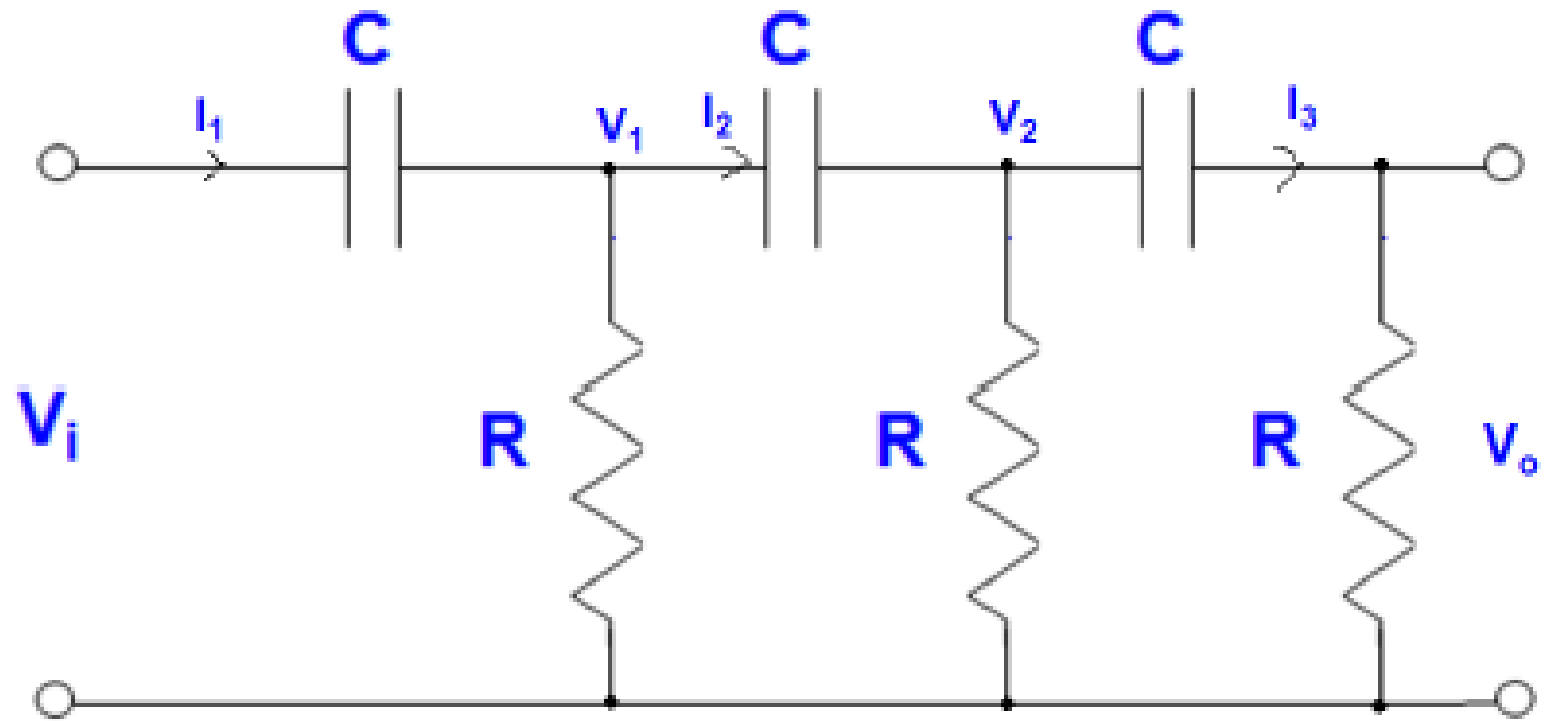
$$I_2 = \frac{V_o}{R} \left(2 + \frac{1}{j\omega CR}\right)$$



$$V_2 = V_o \left(1 + \frac{1}{j\omega CR} \right)$$

$$I_2 = I_3 + \frac{V_2}{R} = \frac{V_o}{R} + \frac{V_o}{R} \left(1 + \frac{1}{j\omega CR} \right)$$

$$I_2 = \frac{V_o}{R} \left(2 + \frac{1}{j\omega CR} \right)$$

At node V_1


$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega CR} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega CR} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$I_1 = I_2 + \frac{V_1}{R} = \frac{V_o}{R} \left(3 + \frac{4}{j\omega CR} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$V_i = V_1 + \frac{I_1}{j\omega C} = V_o \left(1 + \frac{6}{j\omega CR} - \frac{5}{\omega^2 C^2 R^2} - \frac{1}{j\omega^3 C^3 R^3} \right)$$

.....(A)

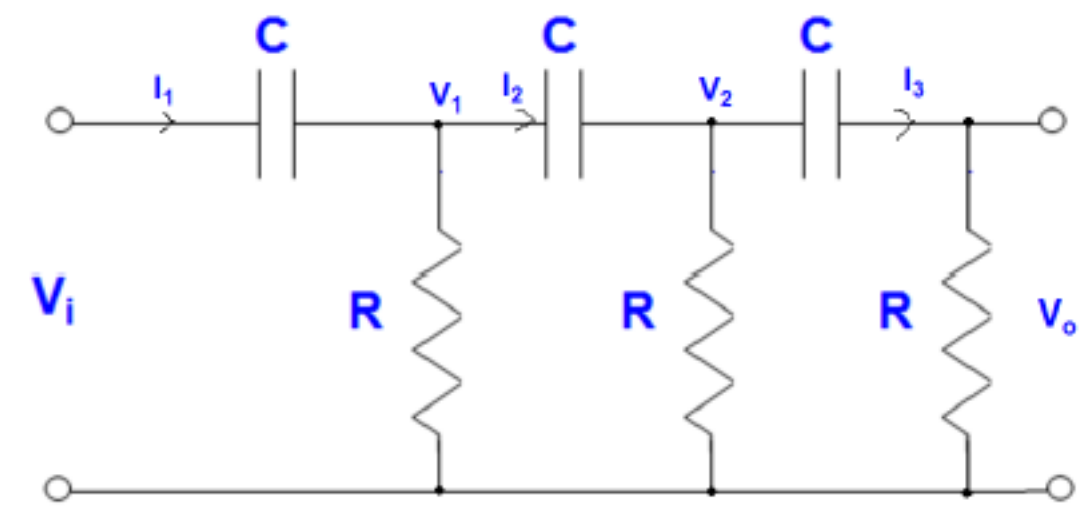

Output voltage should be real hence imaginary part equal to zero.

$$\frac{6}{j\omega CR} - \frac{1}{j\omega^3 C^3 R^3} = 0$$

$$6\omega^2 C^2 R^2 = 1$$

$$\omega = \frac{1}{RC\sqrt{6}}$$

From Eq. A, at this frequency $\beta = V_o/V_i = -1/29$,
and Therefore from Barkhausen Criterion $A_v \beta = 1 \Rightarrow A_v = -29 = -R_f/R_1$

Example: Design a phase-shift oscillator for a frequency of 800 Hz.
The capacitors are to be 10 nF.


Solution:

Start by solving for the resistors needed in the feedback circuit:

$$R = \frac{1}{2\pi\sqrt{6}f_r C} = \frac{1}{2\pi\sqrt{6}(800 \text{ Hz})(10 \text{ nF})} = 8.12 \text{ k}\Omega \quad (\text{Use } 8.2 \text{ k}\Omega.)$$


Calculate the feedback resistor needed:

$$R_f = 29R = 238 \text{ k}\Omega.$$

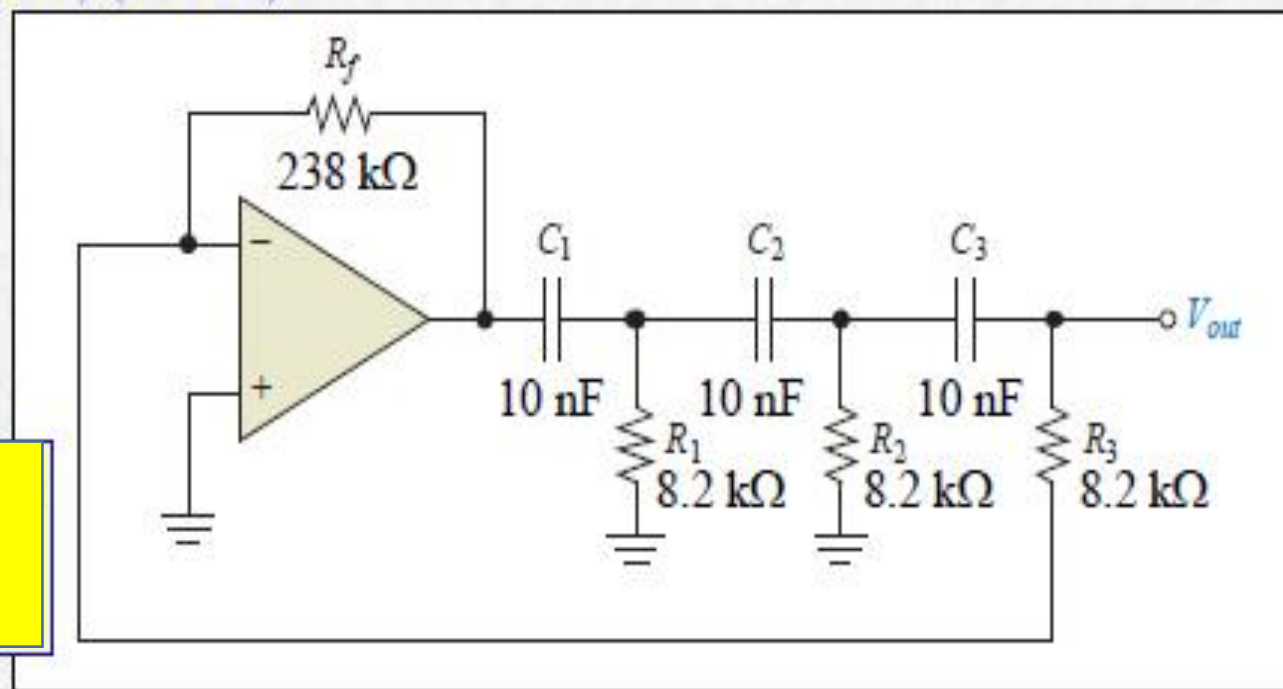

Lec-17 conti.....

RC Oscillators: Wien Bridge Oscillator

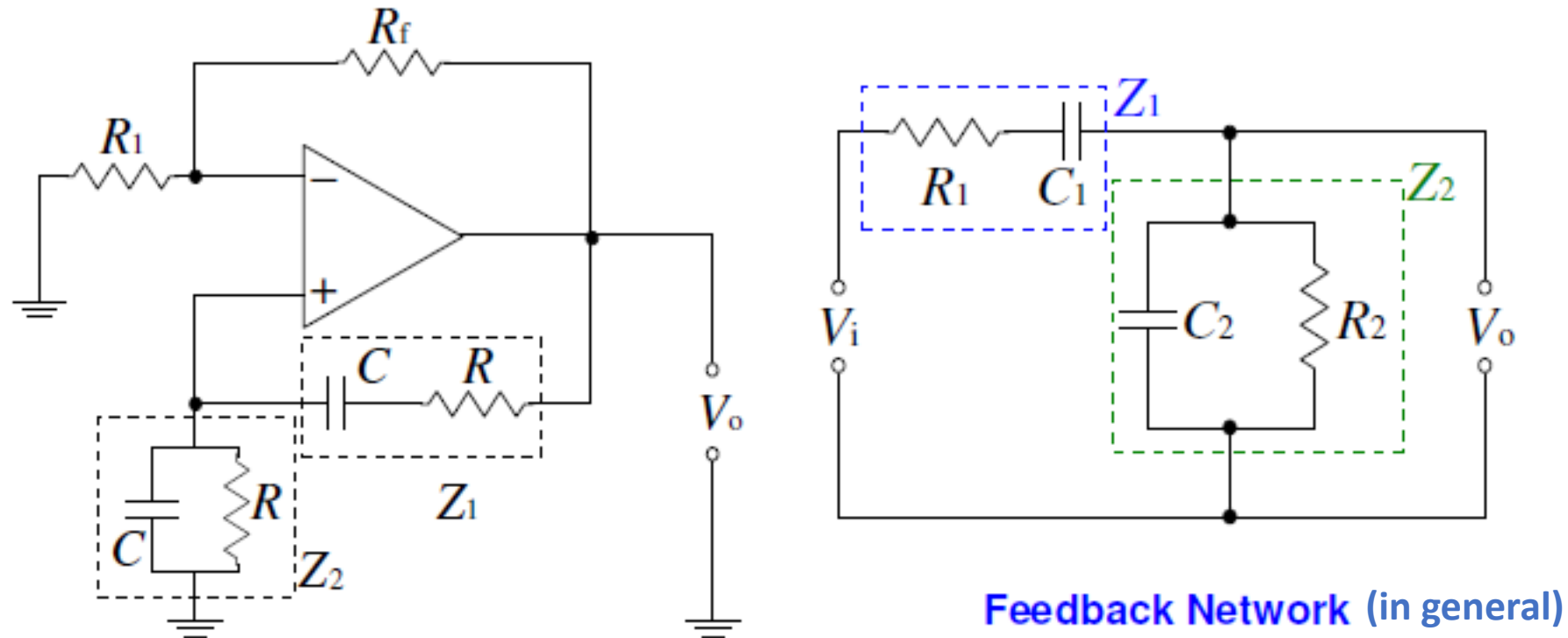

- Feedback network is a lead-lag circuit where R_1 , C_1 form the lag portion and R_2 , C_2 form the lead portion. Thus feedback network provides 0° phase shift.

RC Oscillators: Wien Bridge Oscillator

$$\text{Let } X_{C1} = \frac{1}{\omega C_1} \quad X_{C2} = \frac{1}{\omega C_2} \quad \text{and}$$

$$Z_1 = R_1 - jX_{C1}$$


$$Z_2 = \left[\frac{1}{R_2} + \frac{1}{-jX_{C2}} \right]^{-1} = \frac{-jR_2X_{C2}}{R_2 - jX_{C2}}$$

Therefore, the feedback factor,

$$\beta = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{(-jR_2X_{C2} / R_2 - jX_{C2})}{(R_1 - jX_{C1}) + (-jR_2X_{C2} / R_2 - jX_{C2})}$$

$$\beta = \frac{-jR_2X_{C2}}{(R_1 - jX_{C1})(R_2 - jX_{C2}) - jR_2X_{C2}}$$
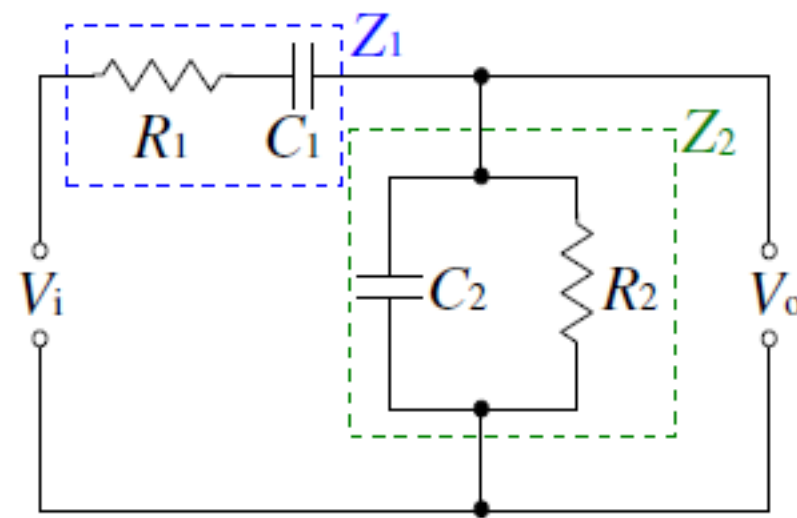
$$\beta = \frac{R_2X_{C2}}{R_1X_{C2} + R_2X_{C1} + R_2X_{C2} + j(R_1R_2 - X_{C1}X_{C2})}$$



$$\beta = \frac{R_2 X_{C2}}{R_1 X_{C2} + R_2 X_{C1} + R_2 X_{C2} + j(R_1 R_2 - X_{C1} X_{C2})}$$

For **Barkhausen Criterion**, imaginary part = 0,

$$R_1 R_2 - X_{C1} X_{C2} = 0$$

$$R_1 R_2 = \frac{1}{\omega C_1} \frac{1}{\omega C_2} \quad \boxed{\omega = 1 / \sqrt{R_1 R_2 C_1 C_2}}$$

Supposing, $R_1 = R_2 = R$ and $X_{C1} = X_{C2} = X_C$,

$$\beta = \frac{R X_C}{3 R X_C + j(R^2 - X_C^2)}$$

At this frequency: $\beta = 1 / 3$ and phase shift = 0°

Due to **Barkhausen Criterion**, gain $A_v \beta = 1$

Where A_v : Gain of the amplifier

$$A_v \beta = 1 \Rightarrow A_v = 3 = 1 + \frac{R_f}{R_1} \quad \boxed{\frac{R_f}{R_1} = 2}$$

Thanks