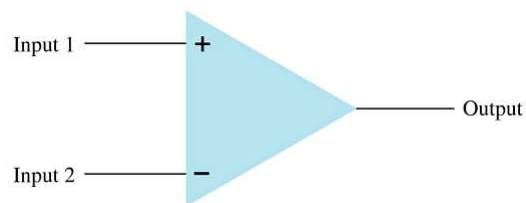


Lec-15

- Operational Amplifier
- Decibel & Bode Plot

1

Basic Op-Amp



Operational amplifier or op-amp, is a very high gain differential amplifier with a high input impedance (typically a few meg-Ohms) and low output impedance (less than 100 Ω).


Note the op-amp has two inputs and one output.

2


2

Amplifier and Bode Plot

Amplifier Model (VCVS)

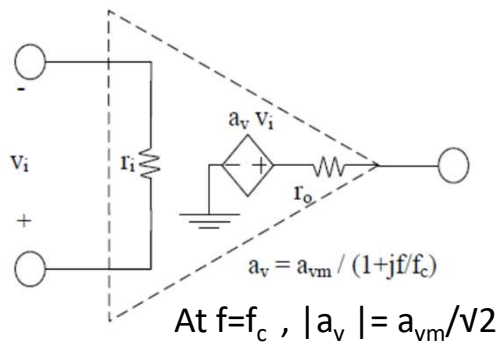

Frequency Response

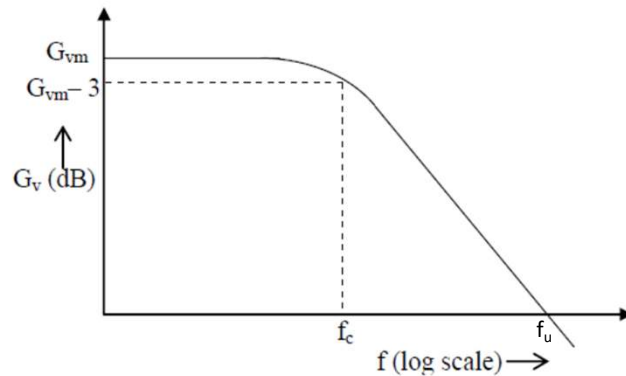

G_{vm} is maximum overall gain across load with respect to applied signal.

3

Bode Plots and Decibel

The voltage transfer function of a two-port network is usually expressed in Bel: (and/or the ratio of output to input)

$$\text{Number of Bels} = \log_{10} \left(\frac{P_o}{P_i} \right) \quad \text{or} \quad \text{Number of Bels} = 2 \log_{10} \left| \frac{V_o}{V_i} \right| \quad \text{because } P \propto V^2$$

Bel is a large unit and decibel (dB) is usually used:

$$\text{Number of decibels} = 20 \log_{10} \left| \frac{V_o}{V_i} \right| \quad \text{or} \quad \left| \frac{V_o}{V_i} \right|_{dB} = 20 \log_{10} \left| \frac{V_o}{V_i} \right|$$

using dB definition, 3 dB difference between maximum gain and gain at the cut-off frequency:

$$20 \log |H(j\omega_c)| - 20 \log |H(j\omega)|_{max} = 20 \log \left[\frac{|H(j\omega_c)|}{|H(j\omega)|_{max}} \right] = 20 \log \left(\frac{1}{\sqrt{2}} \right) \approx -3 \text{ dB}$$

4

Op-Amp Gain

Op-Amps have a very high gain. They can be connected open-loop or closed-loop.

- **Open-loop** : gain can exceed 10,000.
- **Closed-loop** configuration reduces the gain.
- This feedback is a negative feedback. A **negative feedback** reduces the gain and improves many characteristics of the op-amp.

5

5

Basic Block Diagram with Negative Feedback used in Amplifiers

Assume:

- Voltage gain **A** is without feedback and **A_f** is with feedback.
- β is known as feedback ratio.

Let:

$$E = V_{in} - \beta V_{out}$$

$$V_{out} = AE = A(V_{in} - \beta V_{out})$$

$$A_f = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}$$


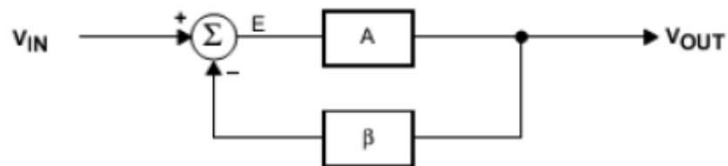


Figure 1 Basic block diagram explaining feedback

With Negative Feedback gain reduced as $(1 + A\beta) > 1$

6

Inverting Op-Amp

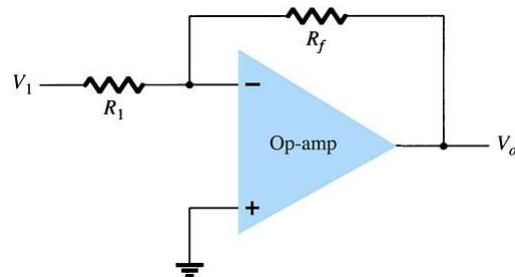

- The signal input is applied to the **inverting (-) input**
- The **non-inverting input (+)** is grounded
- The resistor R_f is the **feedback resistor**. It is connected from the output to the negative (inverting) input. This is **negative feedback**.

7

7

Inverting Op-Amp Gain

Gain can be determined from external resistors: R_f and R_1

$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$


Unity gain—voltage gain is 1

$$R_f = R_1$$

$$A_v = \frac{-R_f}{R_1} = -1$$

The negative sign denotes a 180° phase shift between input and output.

Constant Gain— R_f is a multiple of R_1

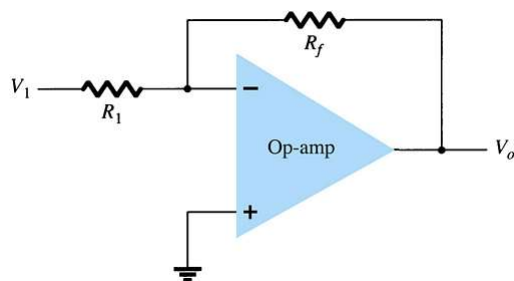

8



8

Virtual Ground

An understanding of the concept of **virtual ground** provides a better understanding of how an op-amp operates.

The *non-inverting* input pin is at ground.
The *inverting* input pin is also at 0 V for an AC signal.

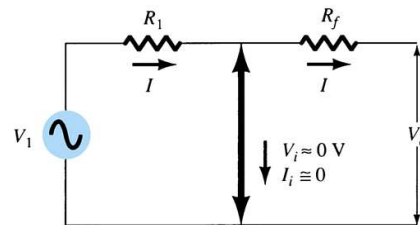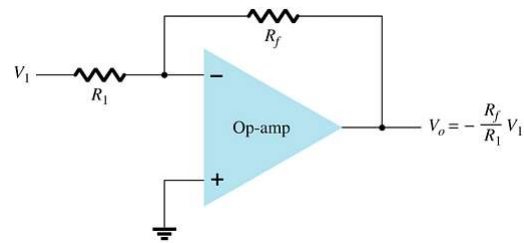The op-amp has such high input impedance that even with a high gain there is no current from inverting input pin, therefore there is no voltage from inverting pin to ground—all of the current is through R_f .



9

9

Ideal OpAmp Rule

1. No current ever flows into either input terminal . (current can flow at the output terminal).
2. there is no voltage difference between the 2 input terminals .

Note: This is valid for negative feedback case only.

10

Practical Op-Amp Circuits

Inverting amplifier
 Noninverting amplifier
 Unity follower
 Summing amplifier
 Integrator
 Differentiator


11

11

Inverting/Noninverting Op-Amps


Inverting Amplifier

$$V_o = -\frac{R_f}{R_1} V_1$$

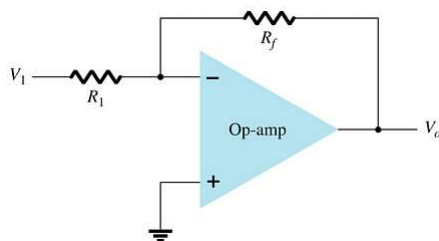

Noninverting Amplifier
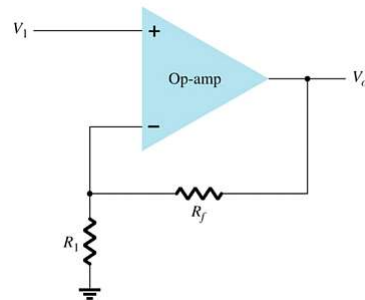
$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1$$




12

12

Unity Follower

$$V_o = V_1$$

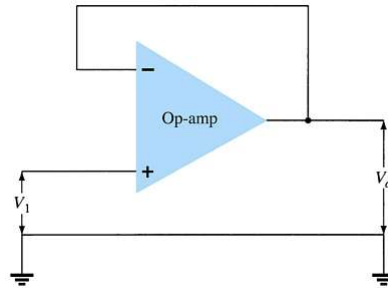


13

13

Summing Amplifier

Because the op-amp has a high input impedance, the multiple inputs are treated as separate inputs.
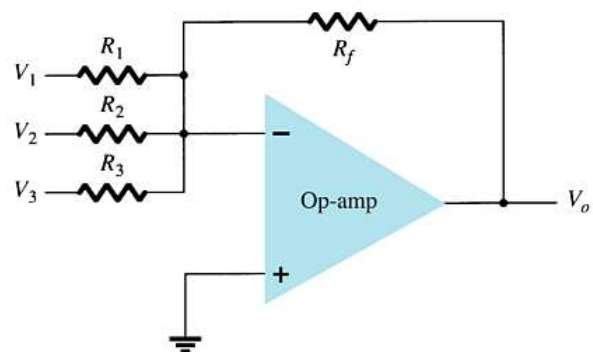
$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$




14

14

Integrator

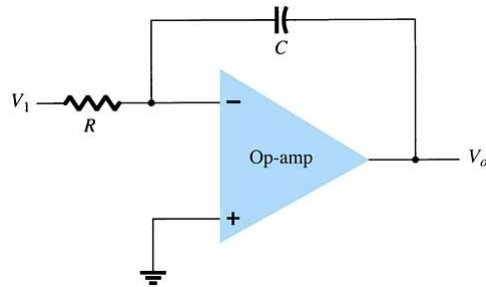The output is the integral of the input. Integration is the operation of summing the area under a waveform or curve over a period of time. This circuit is useful in low-pass filter circuits and sensor conditioning circuits.




$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$

15

15

Differentiator

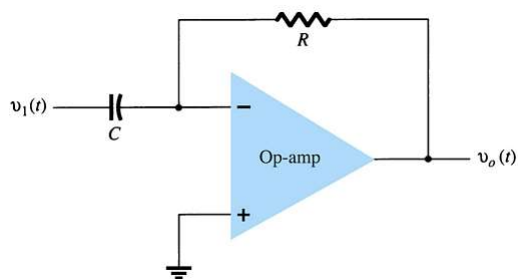The differentiator takes the derivative of the input. This circuit is useful in high-pass filter circuits.



$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

16

16

Electrical Characteristics

TABLE 13.2 mA741 Electrical Characteristics: $V_{CC} = \pm 15\text{ V}$, $T_A = 25^\circ\text{C}$



Characteristic	MIN	TYP	MAX	Unit
V_{IO} Input offset voltage		1	6	mV
I_{IO} Input offset current		20	200	nA
I_{IB} Input bias current		80	500	nA
V_{ICR} Common-mode input voltage range	± 12	± 13		V
V_{OM} Maximum peak output voltage swing	± 12	± 14		V
A_{VD} Large-signal differential voltage amplification	20	200		V/mV
r_i Input resistance	0.3	2		$M\Omega$
r_o Output resistance		75		Ω
C_i Input capacitance		1.4		pF
CMRR Common-mode rejection ratio	70	90		dB
I_{CC} Supply current		1.7	2.8	mA
P_D Total power dissipation		50	85	mW

Note: These ratings are for specific circuit conditions, and they often include minimum, maximum and typical values.

17


Ideal Op-AMP

Ideal OpAmp Model

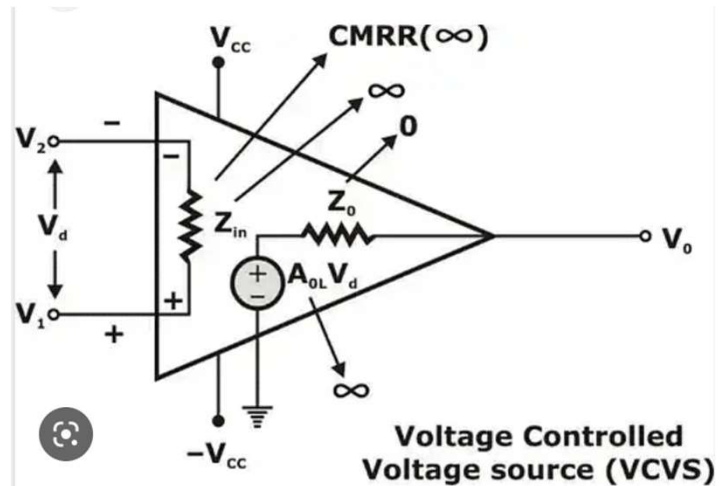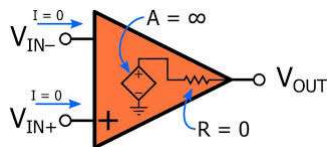

18

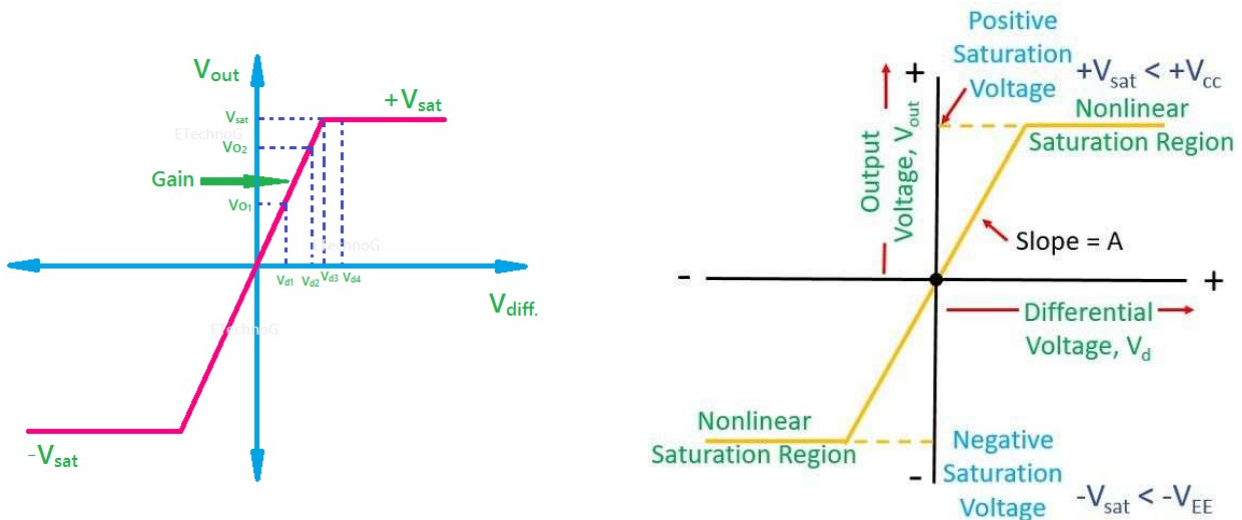Voltage Gain and Voltage Swing(G_v , G_{vo} and A_v & A_{vo})



19

Frequency Response: Cut-off Freq./Break Freq./ 3dB cut-off freq./ Half power freq.
Gain x Bandwidth= G.B.P= constant= unity-gain bandwidth product (f_u)

- Freq. dependency due to internal capacitance or total effective capacitance at output node.


$$f_o = \frac{1}{2\pi R_o C}$$

$$A_{OL}(f) = \frac{A_{OL}}{1 + j\left(\frac{f}{f_o}\right)}$$

f = Operating frequency

f_o = Break frequency or cutoff frequency

$$|A_{OL}(f)| = \frac{A_{OL}}{\sqrt{1 + \left(\frac{f}{f_o}\right)^2}}$$

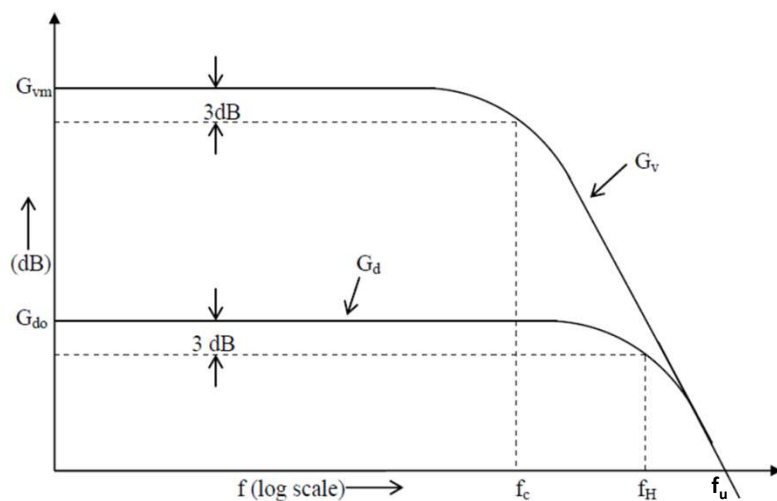

(b) Frequency Response

20


Thanks

21

Lec-15
OpAMP Cont.....


22

Differential and Common Mode Input

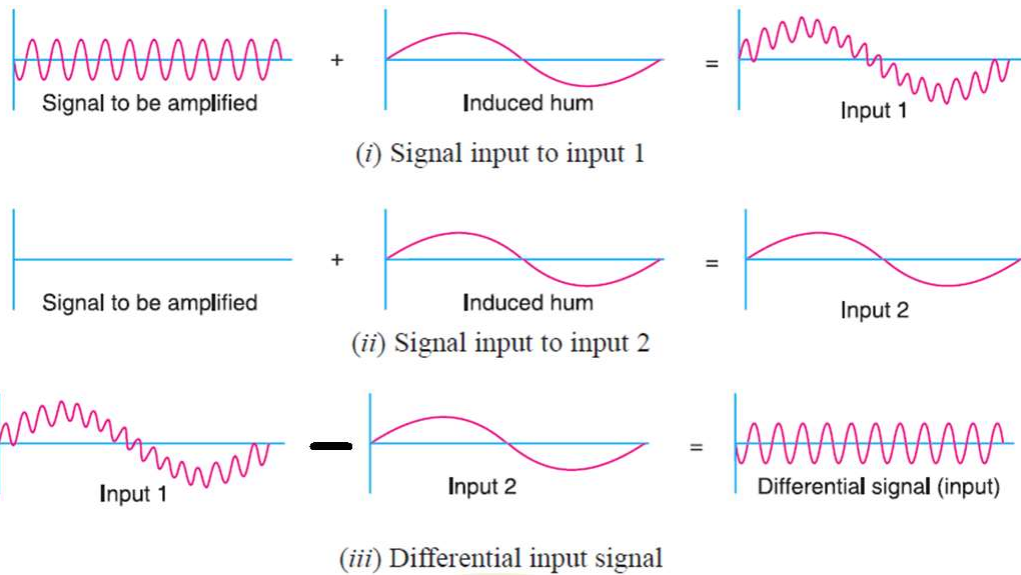

23

Differential and Common Mode Input

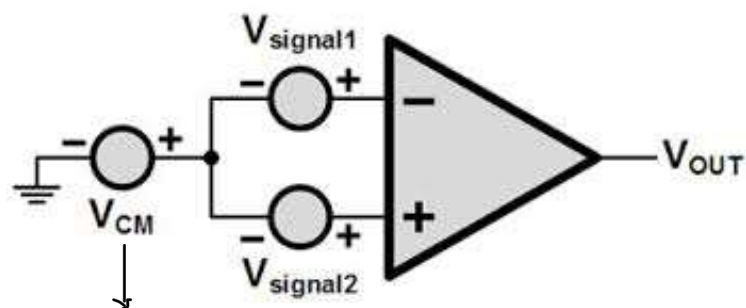

24

Common Mode Rejection Ratio

Differential Mode Gain: A_{dm} for differential mode input v_{dm}

Common Mode Gain: A_{cm} for common mode input v_{cm}

In general OpAMP Out put Voltage

$$v_o = A_{dm} \cdot v_{dm} + A_{cm} \cdot v_{cm}$$

$$CMRR = A_{dm}/A_{cm}$$

$$CMRR \text{ (in dB)} = 20 \log_{10}(A_{dm}/A_{cm})$$

25

Example 25.3. A differential amplifier has an output of 1V with a differential input of 10 mV and an output of 5 mV with a common-mode input of 10 mV. Find the CMRR in dB.

26

Example 25.3. A differential amplifier has an output of 1V with a differential input of 10 mV and an output of 5 mV with a common-mode input of 10 mV. Find the CMRR in dB.

Solution. Differential gain, $A_{DM} = 1\text{V}/10\text{ mV} = 100$

Common-mode gain, $A_{CM} = 5\text{ mV}/10\text{ mV} = 0.5$

$$\therefore \text{CMRR}_{dB} = 20 \log_{10} (100/0.5) = 46 \text{ dB}$$

27

Example 25.4. A differential amplifier has a voltage gain of 150 and a CMRR of 90 dB. The input signals are 50 mV and 100 mV with 1 mV of noise on each input. Find (i) the output signal (ii) the noise on the output.

28

Example 25.4. A differential amplifier has a voltage gain of 150 and a CMRR of 90 dB. The input signals are 50 mV and 100 mV with 1 mV of noise on each input. Find (i) the output signal (ii) the noise on the output.

Solution.

(i) Output signal, $v_{out} = A_{DM}(v_1 - v_2) = 150 (100 \text{ mV} - 50 \text{ mV}) = 7.5 \text{ V}$

(ii) $CMRR_{dB} = 20 \log_{10} (150/A_{CM})$

or $90 = 20 \log_{10} (150/A_{CM})$

$\therefore A_{CM} = 4.7 \times 10^{-3}$

Noise on output $= A_{CM} \times 1 \text{ mV} = 4.7 \times 10^{-3} \times 1 \text{ mV} = 4.7 \times 10^{-6} \text{ V}$


29

Assignment Problems Types and Discussion


1. Mic and Speaker with Amplifier (VCVS) Model
2. OPAMP based circuit analysis using ideal Op-Amp properties.
3. Design Problem using cascading multiple stage Op-AMP circuits

30


Assignment Problems Discussions:

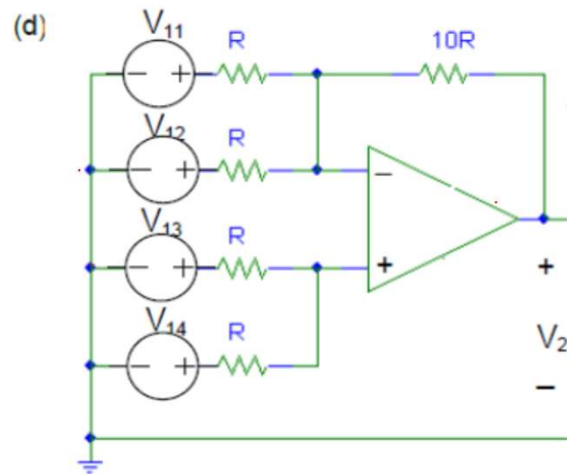

31

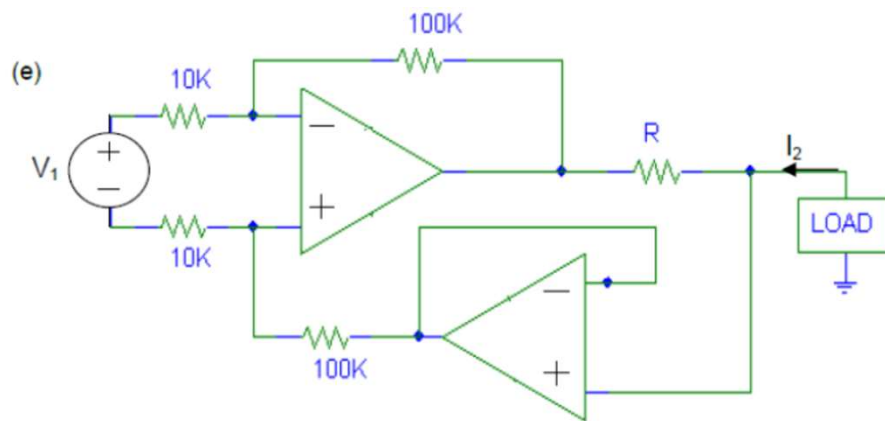

32

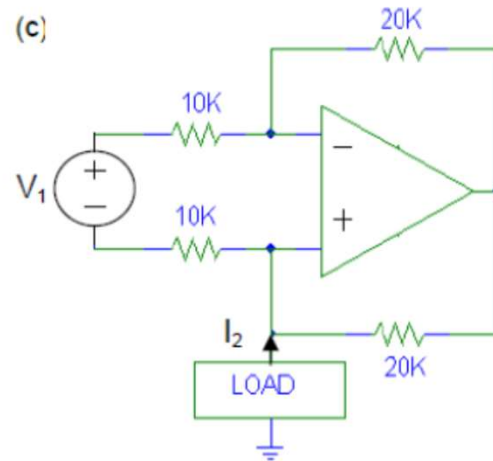

33

Thanks

34