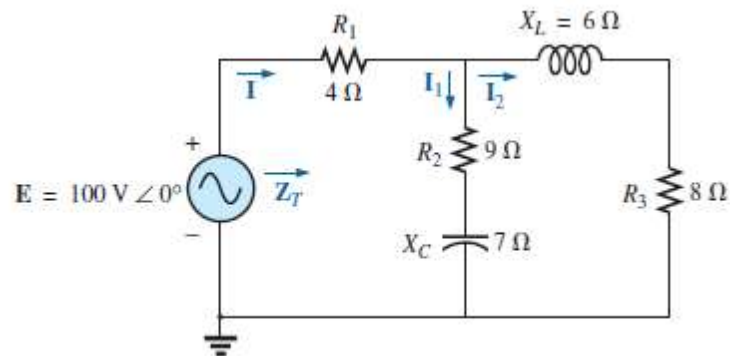



**ECE101: Basic Electrical and Electronic Circuits**

Q. 1.




- Calculate the total impedance  $Z_T$ .
- Compute  $I$ .
- Find the total power factor.
- Calculate  $I_1$  and  $I_2$ .
- Find the average power delivered to the circuit.

Q. 2. For the network of Figure:

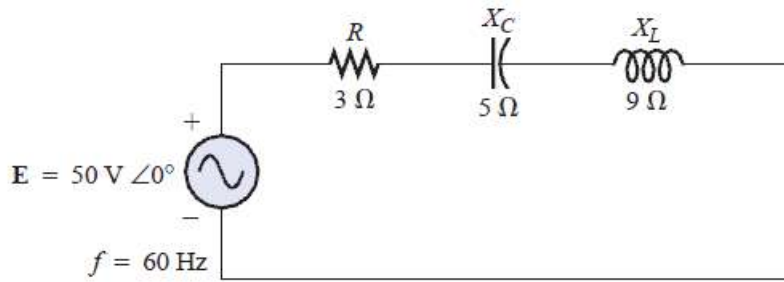


- Find the average power delivered to each element.
- Find the reactive power for each element.
- Find the apparent power for each element.
- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor  $F_p$  of the circuit.
- Sketch the power triangle.

Q. 3. For the circuit of Figure:

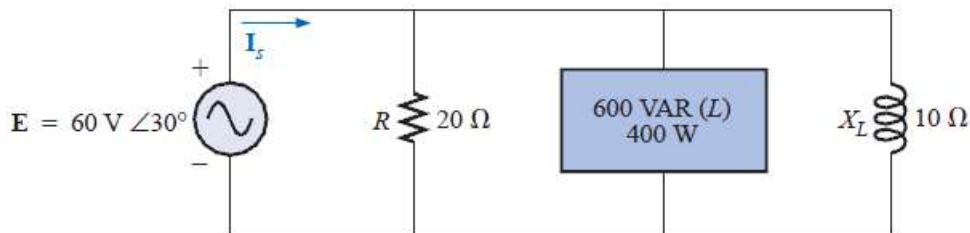

- Find the average, reactive, and apparent power for the 20- $\Omega$  resistor.
- Repeat part (a) for the 10- $\Omega$  inductive reactance.
- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor  $F_p$ .
- Find the current  $I_s$ .

Q. 4. For the network of Figure:

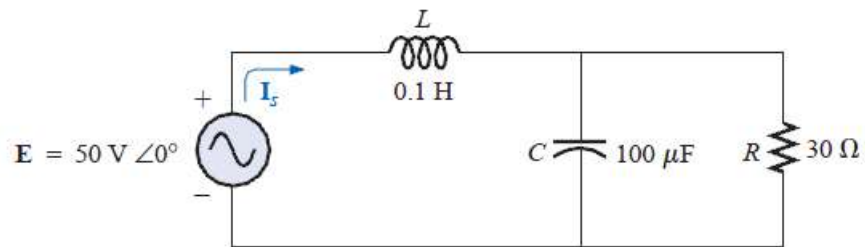

$$\omega = 400 \text{ rad/s}$$

- Find the average power delivered to each element.
- Find the reactive power for each element.
- Find the apparent power for each element.
- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor  $F_p$  of the circuit.
- Sketch the power triangle.