

# **Steady State AC Circuits AC Power and Complex Impedance Phasor**

1

## **Review-AC Circuits**

- Introduction
- Power in Resistive Components
- Power in Capacitors
- Power in Inductors
- Circuits with Resistance and Reactance
- Active and Reactive Power
- Power Factor Correction

2

## Introduction

- The **instantaneous power** dissipated in a component is a product of the instantaneous voltage and the instantaneous current

$$p = vi$$

- In a resistive circuit the voltage and current are in phase – calculation of  $p$  is straight forward
- In reactive circuits, there will normally be some phase shift between  $v$  and  $i$ , and calculating the power becomes more complicated

3

## Power in Resistive Components

- Suppose a voltage  $v = V_p \sin \omega t$  is applied across a resistance  $R$ . The resultant current  $i$  will be

$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R} = I_p \sin \omega t$$

- The result power  $p$  will be

$$p = vi = V_p \sin \omega t \times I_p \sin \omega t = V_p I_p (\sin^2 \omega t) = V_p I_p \left( \frac{1 - \cos 2\omega t}{2} \right)$$


- The average value of  $(1 - \cos 2\omega t)$  is 1, so

$$\text{Average Power } P = \frac{1}{2} V_p I_p = \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} = VI$$

where  $V$  and  $I$  are the **r.m.s. voltage and current**

4

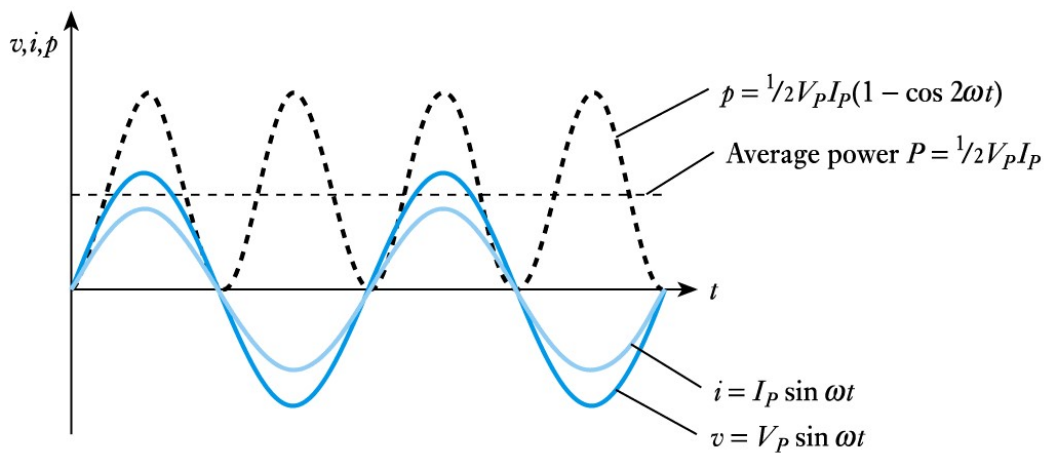- Relationship between  $v$ ,  $i$  and  $p$  in a Resistive Circuit



5

## Power in Capacitive Circuit

- From our discussion of capacitors we know that **the current leads the voltage by  $90^\circ$** . Therefore, if a voltage  $v = V_p \sin \omega t$  is applied across a capacitance  $C$ , the current will be given by  $i = I_p \cos \omega t$


- Then

$$\begin{aligned}
 p &= vi \\
 &= V_p \sin \omega t \times I_p \cos \omega t \\
 &= V_p I_p (\sin \omega t \times \cos \omega t) \\
 &= V_p I_p \left( \frac{\sin 2\omega t}{2} \right)
 \end{aligned}$$

- The average power is zero

6

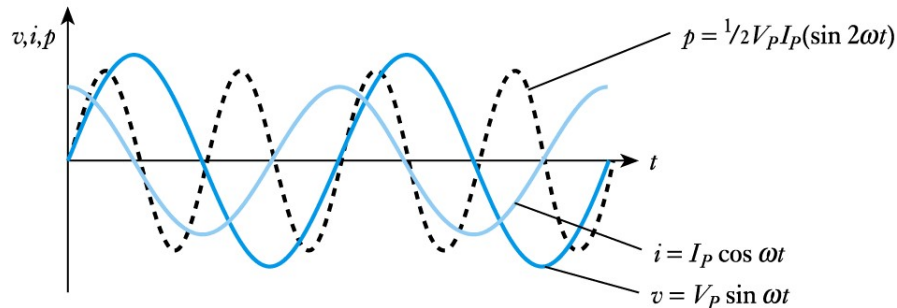- Relationship between  $v$ ,  $i$  and  $p$  in a capacitor



7

## Power in Inductive Circuit


- From our discussion of inductors we know that **the current lags the voltage by  $90^\circ$** . Therefore, if a voltage  $v = V_p \sin \omega t$  is applied across an inductance  $L$ , the current will be given by  $i = -I_p \cos \omega t$
- Therefore

$$\begin{aligned}
 p &= vi \\
 &= V_p \sin \omega t \times -I_p \cos \omega t \\
 &= -V_p I_p (\sin \omega t \times \cos \omega t) \\
 &= -V_p I_p \left( \frac{\sin 2\omega t}{2} \right)
 \end{aligned}$$

- Again the average power is zero

8

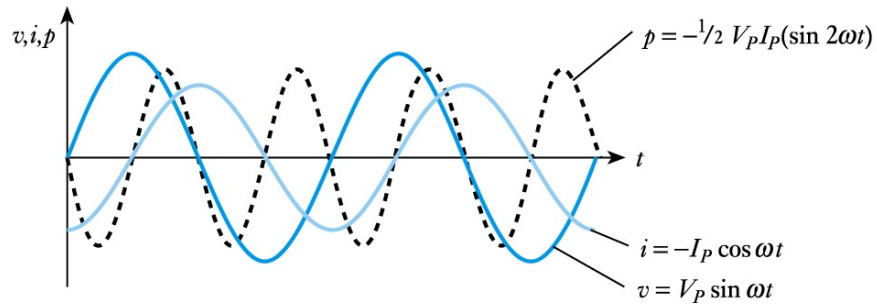• Relationship between  $v$ ,  $i$  and  $p$  in an inductor



9

## Circuit with Resistance and Reactance

- When a sinusoidal voltage  $v = V_p \sin \omega t$  is applied across a circuit with resistance *and* reactance, the current will be of the general form  $i = I_p \sin (\omega t - \phi)$
- Therefore, the instantaneous power,  $p$  is given by

$$\begin{aligned} p &= vi \\ &= V_P \sin \omega t \times I_P \sin(\omega t - \phi) \\ &= \frac{1}{2} V_P I_P \{ \cos \phi - \cos(2\omega t - \phi) \} \end{aligned}$$

$$p = \frac{1}{2} V_P I_P \cos \phi - \frac{1}{2} V_P I_P \cos(2\omega t - \phi)$$

10

$$p = \frac{1}{2} V_P I_P \cos \phi - \frac{1}{2} V_P I_P \cos(2\omega t - \phi)$$

- The expression for  $p$  has two components
- The second part oscillates at  $2\omega$  and has an **average value of zero** over a complete cycle
  - **this is the power that is stored in the reactive elements and then returned to the circuit within each cycle.**
- The first part represents the power dissipated in resistive components. **Average power dissipation** is

$$P = \frac{1}{2} V_P I_P (\cos \phi) = \frac{V_P}{\sqrt{2}} \times \frac{I_P}{\sqrt{2}} \times (\cos \phi) = VI \cos \phi$$

11

- The average power dissipation given by

$$P = \frac{1}{2} V_P I_P (\cos \phi) = VI \cos \phi$$

is termed the **active power** in the circuit and is measured in **watts (W)**

- The product of the r.m.s. voltage and current i.e.  $V \times I$  is termed as the **apparent power**,  $S$ . To avoid confusion this is given the **units of volt amperes (VA)**

12

- From the above discussion it is clear that

$$P = VI \cos \phi$$

$$= S \cos \phi$$

- In other words, the active power is the apparent power times the cosine of the phase angle.
- This cosine is referred to as the **power factor**

$$\frac{\text{Active power (in watts)}}{\text{Apparent power (in volt amperes)}} = \text{Power factor}$$

$$\text{Power factor} = \frac{P}{S} = \cos \phi$$

13

## Active (P) and Reactive Power (Q)

- When a circuit has resistive and reactive parts, the resultant power has 2 parts:
  - The first is *dissipated* in the resistive element. This is the **active power, P**
  - The second is *stored and returned* by the reactive element. This is the **reactive power, Q**, which has units of **volt amperes reactive** or **VAR**
- While reactive power is not dissipated it does have an effect on the system
  - for example, it increases the current that must be supplied and increases losses with cables

14

# What is impedance?

- Electrical impedance is the measure of the opposition that a circuit presents to a current when a voltage is applied.
- Impedance is defined as the ratio of RMS value of Voltage to RMS value of current  $Z=V/I$  or  $V=IZ$
- $Z = R + jX$  (for inductive circuit) or  $Z = R - jX$  (for capacitive circuit)



15


## Impedance Diagram

*For any configuration (series, parallel, series-parallel, etc.), the angle associated with the total impedance is the angle by which the **applied voltage leads the source current**.*

*For Resistive network,  $\theta_T$  will be 0*

*For inductive networks,  $\theta_T$  will be positive,*

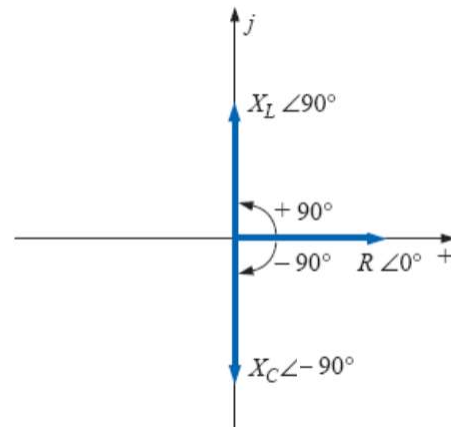
*For capacitive networks,  $\theta_T$  will be negative.*



16



## Phasor Diagram of individual Element

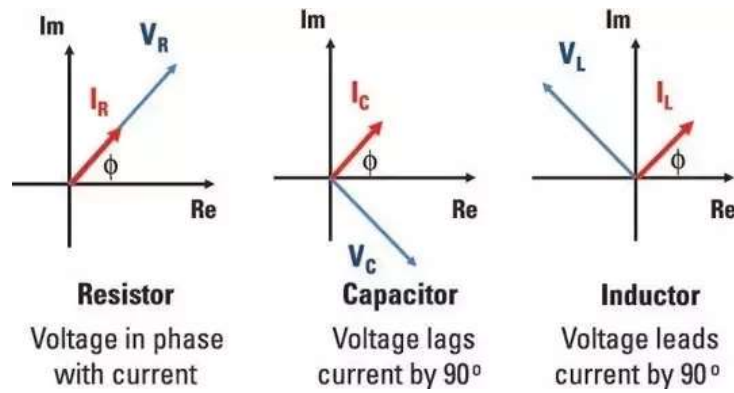


17

## Power Triangle


$$S = P + jQ$$

$$Z = R + j(X_L - X_C)$$

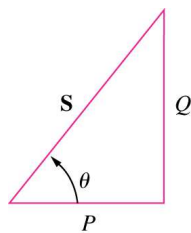


(a)

Power triangle

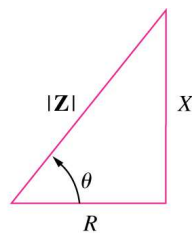

(b)

Impedance triangle

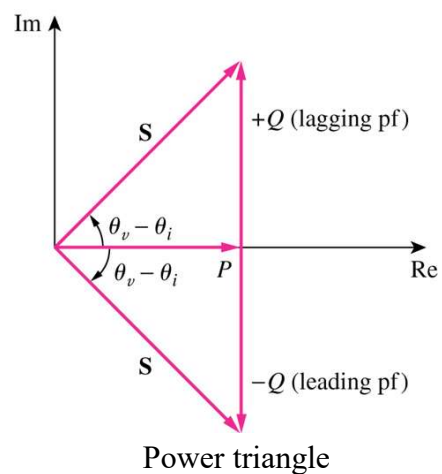

Power triangle


$$\text{Power factor} = \frac{P}{S} = \cos \phi = R / Z$$

$$\text{For inductive (lagging): Power factor} = \frac{P}{S} = \cos \phi = R / (R + jX_L)$$

$$\text{For capacitive (leading): Power factor} = \frac{P}{S} = \cos \phi = R / (R - jX_C)$$

18

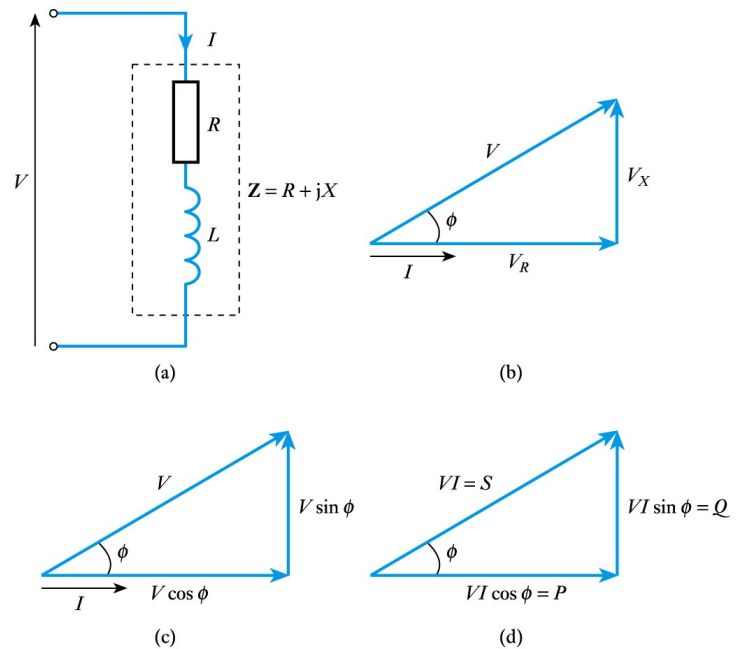- Consider an RL circuit
  - the relationship between the various forms of power can be illustrated using a power triangle



19

- Therefore,  $V$  and  $I$  being rms values

Active Power (Average Power)

$$P = VI \cos \phi \quad \text{watts} \quad \text{or } P = S \cos \phi$$

Reactive Power (Quadrature Power)

$$Q = VI \sin \phi \quad \text{VAR} \quad \text{or } Q = S \sin \phi$$

Apparent Power

$$S = VI \quad \text{VA}$$


Complex Power

$$S = P + jQ = VI \cos \phi + j VI \sin \phi = VI^*$$

with  $S^2 = P^2 + Q^2$

20

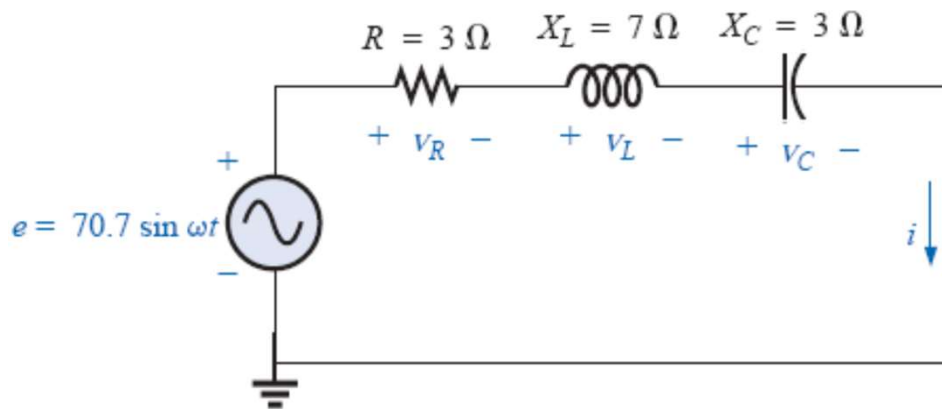Find total Impedance  $Z_T$  ,  
 Draw Impedance diagram (Triangle),  
 Draw Phasor Diagram (Current and  
 Voltage Phasor) ,  
 Power Factor




21

$$\begin{aligned} Z_T &= Z_1 + Z_2 + Z_3 = R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 3 \Omega + j 7 \Omega - j 3 \Omega = 3 \Omega + j 4 \Omega \end{aligned}$$

$$Z_T = 5 \Omega \angle 53.13^\circ$$

Inductive

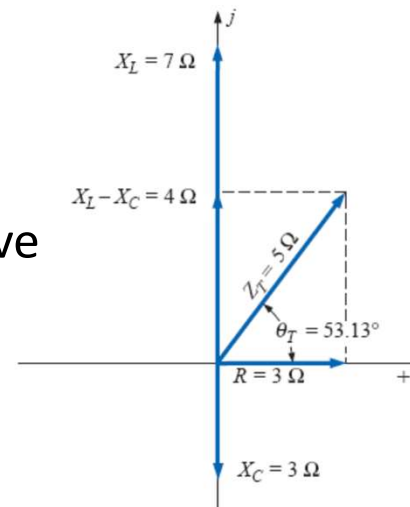

22

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{50 \text{ V } \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 10 \text{ A } \angle -53.13^\circ$$

$\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$

$$\mathbf{V}_R = \mathbf{I}\mathbf{Z}_R = (I \angle \theta)(R \angle 0^\circ) = (10 \text{ A } \angle -53.13^\circ)(3 \Omega \angle 0^\circ) = 30 \text{ V } \angle -53.13^\circ$$

$$\mathbf{V}_L = \mathbf{I}\mathbf{Z}_L = (I \angle \theta)(X_L \angle 90^\circ) = (10 \text{ A } \angle -53.13^\circ)(7 \Omega \angle 90^\circ) = 70 \text{ V } \angle 36.87^\circ$$

$$\mathbf{V}_C = \mathbf{I}\mathbf{Z}_C = (I \angle \theta)(X_C \angle -90^\circ) = (10 \text{ A } \angle -53.13^\circ)(3 \Omega \angle -90^\circ) = 30 \text{ V } \angle -143.13^\circ$$

Kirchhoff's voltage law:

$$\Sigma_C \mathbf{V} = \mathbf{E} - \mathbf{V}_R - \mathbf{V}_L - \mathbf{V}_C = 0$$

$$\mathbf{E} = \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C$$

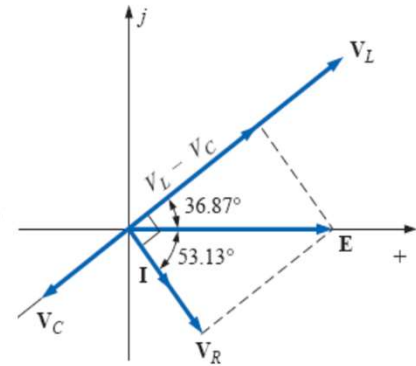


FIG. 15.38

Phasor diagram for the series R-L-C circuit of

For Practicing Complex Algebra calculation: Use Voltage Divider to get Voltage Phasors across R, C, and L

23

## Power Factor:

The total **power factor** ( $\cos \theta_T$ ), determined by the angle between the applied voltage  $\mathbf{E}$  and the resulting current  $\mathbf{I}$ .

$$F_p = \cos \theta_T = \cos 53.13^\circ = 0.6 \text{ lagging}$$


$$F_p = \cos \theta = \frac{R}{Z_T} = \frac{3 \Omega}{5 \Omega} = 0.6 \text{ lagging}$$

Leading means  $\mathbf{I}$  leads  $\mathbf{E}$ : **for Capacitive circuit= leading power factor**

Lagging means  $\mathbf{I}$  Lags  $\mathbf{E}$ : **for inductive circuit= lagging power factor**

24

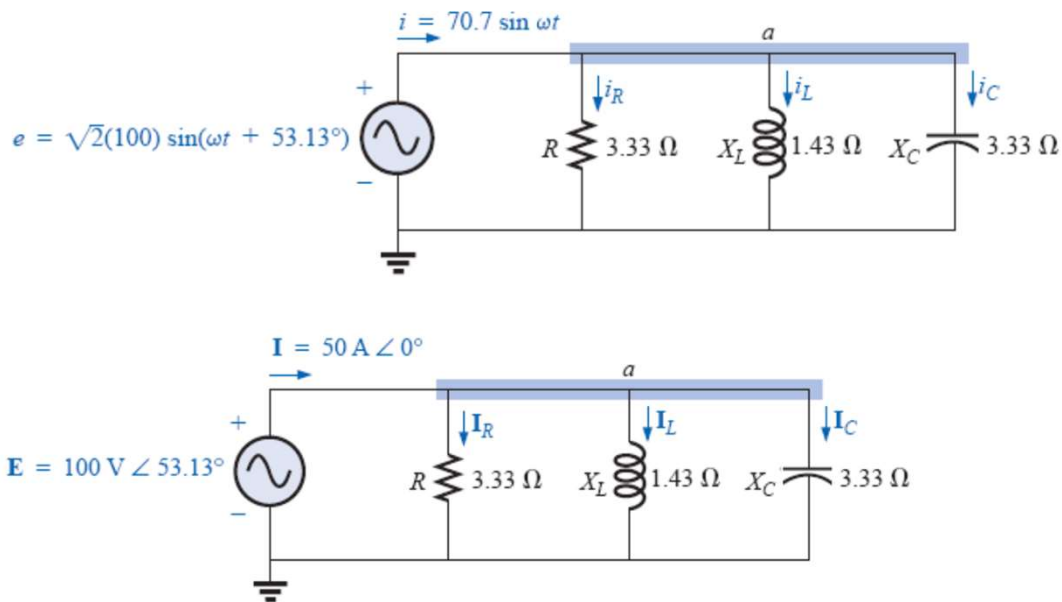Calculate total impedance, currents and draw phasor diagram



25

$$Z_T = \frac{1}{Y_T} = \frac{1}{0.5 \text{ S } \angle -53.13^\circ} = 2 \Omega \angle 53.13^\circ$$

**I**

$$I = \frac{E}{Z_T} = E Y_T = (100 \text{ V } \angle 53.13^\circ)(0.5 \text{ S } \angle -53.13^\circ) = 50 \text{ A } \angle 0^\circ$$

**$I_R$ ,  $I_L$ , and  $I_C$**

$$\begin{aligned} I_R &= (E \angle \theta)(G \angle 0^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle 0^\circ) = 30 \text{ A } \angle 53.13^\circ \end{aligned}$$

$$\begin{aligned} I_L &= (E \angle \theta)(B_L \angle -90^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.7 \text{ S } \angle -90^\circ) = 70 \text{ A } \angle -36.87^\circ \end{aligned}$$


$$\begin{aligned} I_C &= (E \angle \theta)(B_C \angle 90^\circ) \\ &= (100 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle +90^\circ) = 30 \text{ A } \angle 143.13^\circ \end{aligned}$$

26

*Kirchhoff's current law:* At node  $a$ ,

$$\mathbf{I} - \mathbf{I}_R - \mathbf{I}_L - \mathbf{I}_C = 0$$

$$\mathbf{I} = \mathbf{I}_R + \mathbf{I}_L + \mathbf{I}_C$$

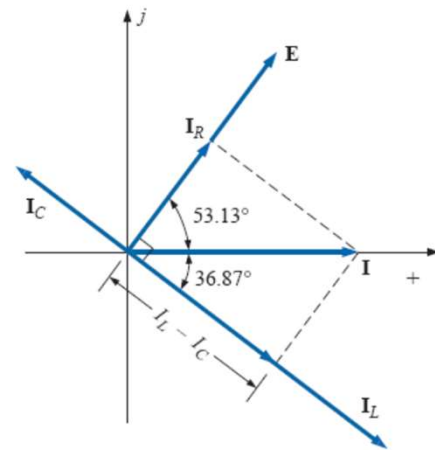

**FIG. 15.74**

*Phasor diagram for the parallel R-L-C*