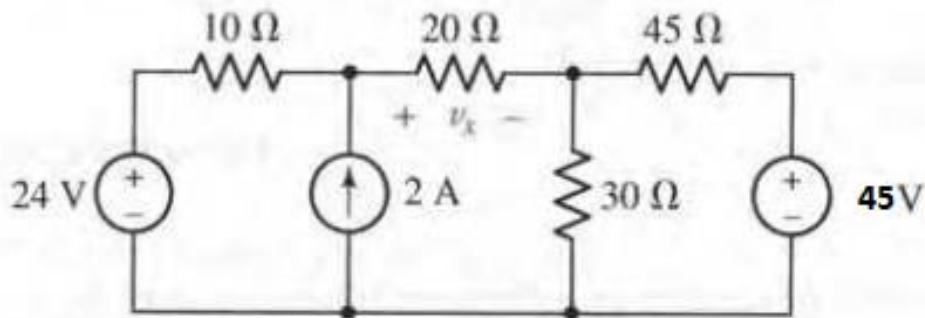


ECE101: Basic Electrical and Electronic Circuits
Tutorial -03

To be discussed in Tutorials during


Feb 02- 07

7. Use superposition to find the value of v_x in the circuit of Fig. 5.52.




■ **FIGURE 5.52**

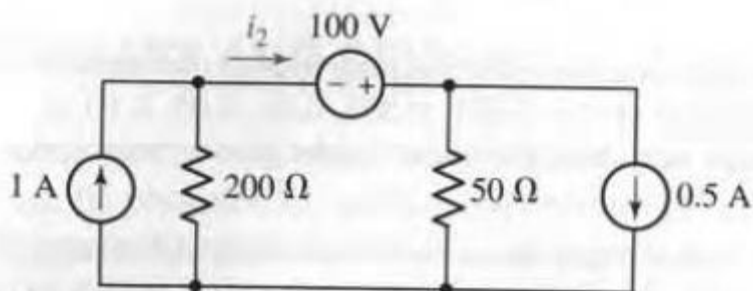9. (a) Use the superposition theorem to find i_2 in the circuit shown in Fig. 5.54.
(b) Calculate the power absorbed by each of the five circuit elements.




■ **FIGURE 5.54**

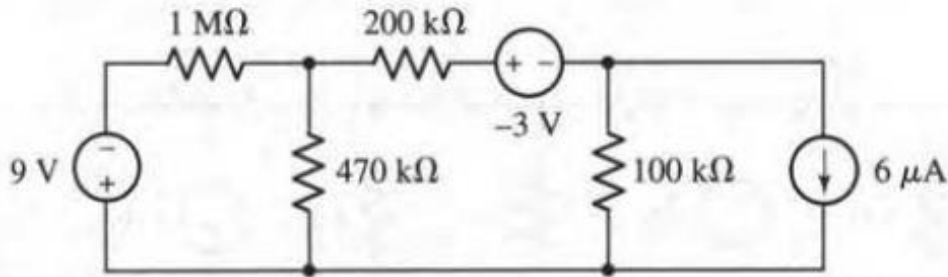25. Determine the power dissipated by the $1\text{ M}\Omega$ resistor using source transformation to first simplify the circuit shown in Fig. 5.70.




■ FIGURE 5.70

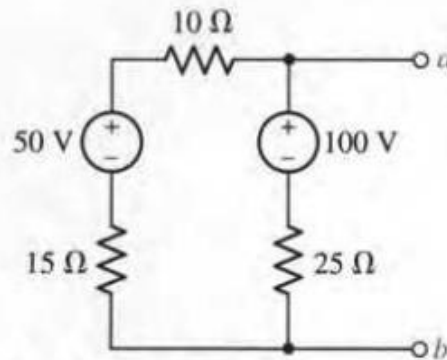40. (a) Find the Thévenin equivalent at terminals a and b for the network shown in Fig. 5.83. How much power would be delivered to a resistor connected to a and b if R_{ab} equals (b) $50\ \Omega$; (c) $12.5\ \Omega$?




■ FIGURE 5.83

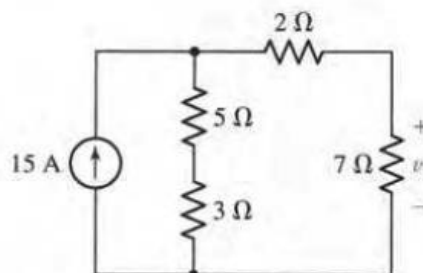42. (a) Find the Thévenin equivalent of the network connected to the $7\ \Omega$ resistor of Fig. 5.85. (b) Find the Norton equivalent of the network connected to the $7\ \Omega$ resistor of Fig. 5.85. (c) Compute the voltage v_1 using both of your equivalent circuits. (d) Replace the $7\ \Omega$ resistor with a $1\ \Omega$ resistor, and recompute v_1 using either circuit.




■ FIGURE 5.85

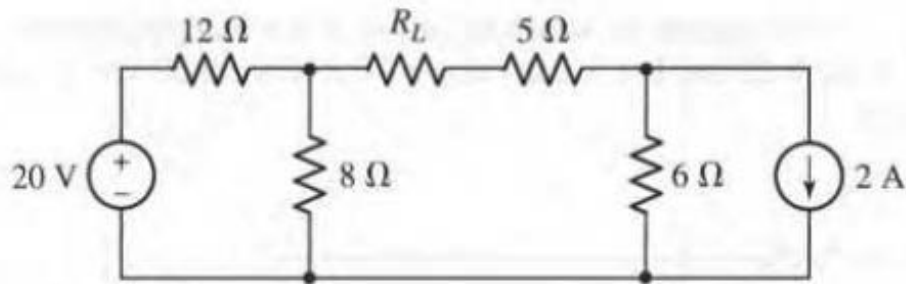61. If any value whatsoever may be selected for R_L in the circuit of Fig. 5.101, what is the maximum power that could be dissipated in R_L ?



■ FIGURE 5.101

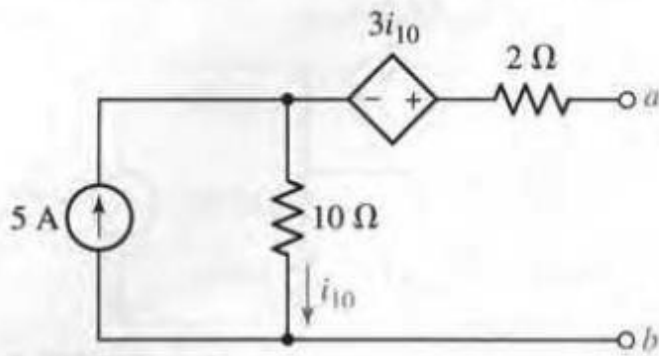63. (a) Determine the Thévenin equivalent of the network shown in Fig. 5.103, and (b) find the maximum power that can be drawn from it.



■ FIGURE 5.103