

## Lec-7


### Network Theorems

- Superposition Theorem
- Thevenin's Theorem and
- Norton's Theorem
- Maximum Power Transfer Theorem

1


### SUPERPOSITION THEOREM

*The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.*

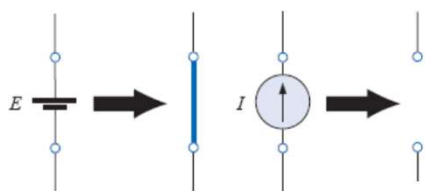

**FIG. 9.1**

*Removing the effects of ideal sources.*

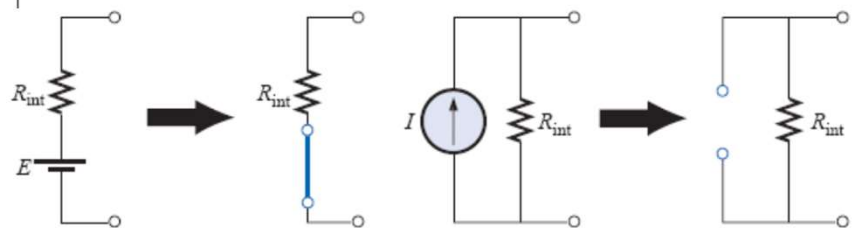

**FIG. 9.2**

*Removing the effects of practical sources.*

2


### *Not Valid for Power Calculation*

*The total power delivered to a resistive element must be determined using the total current through or the total voltage across the element and cannot be determined by a simple sum of the power levels established by each source.*


$$I_T^2 = (I_1 + I_2)^2 = I_1^2 + I_2^2 + 2I_1I_2$$

3

Determine the current through the 4 Ohm?

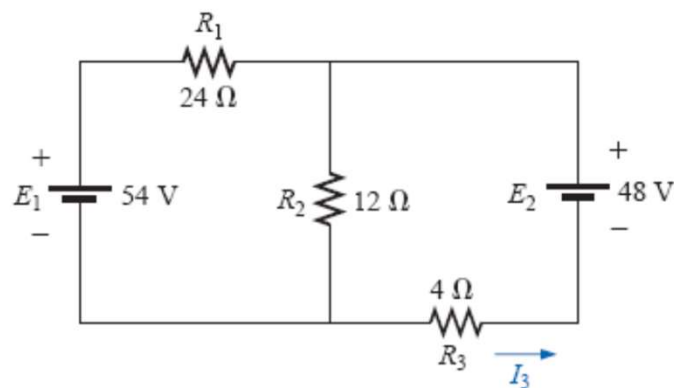

4

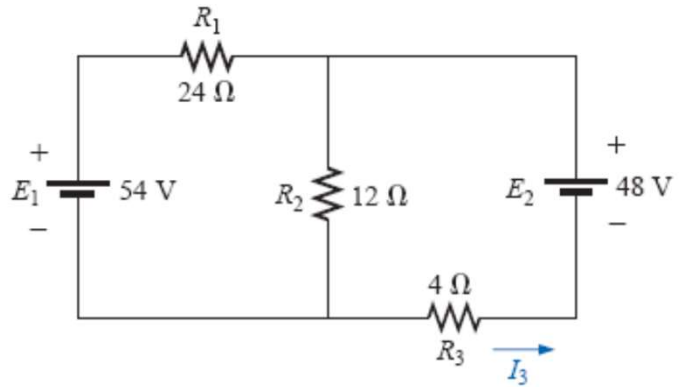


$$I_3 = I''_3 - I'_3 = 4\text{ A} - 1.5\text{ A} = 2.5\text{ A}$$

5
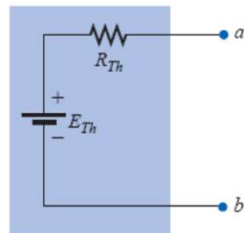
## THEVENIN'S THEOREM


*Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor,*



6


**Draw Thevenin's equivalent ckt taking  $R_4$  as load**

**Calculate:  $I(R_4)$**

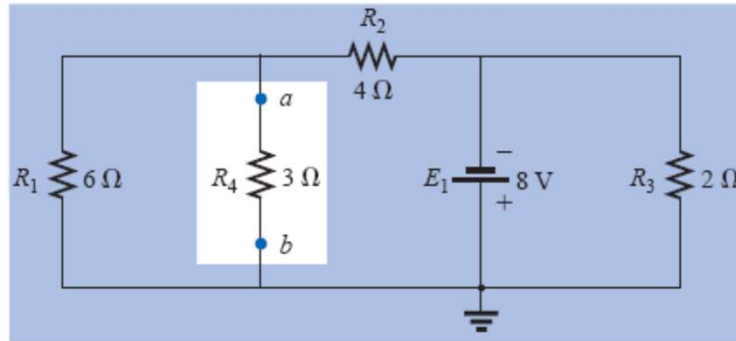


7

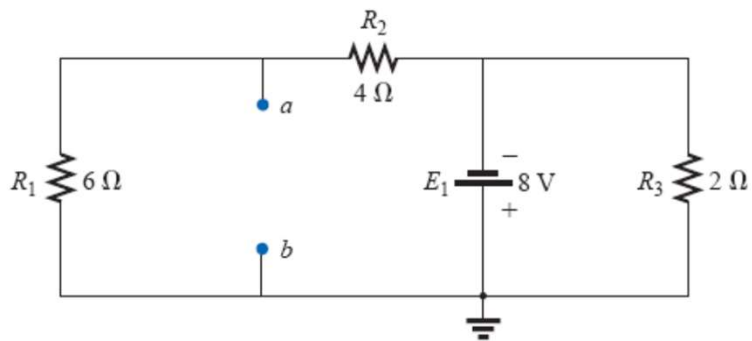*1. Identifying the terminals of particular interest for the network (Removing Load)*



8

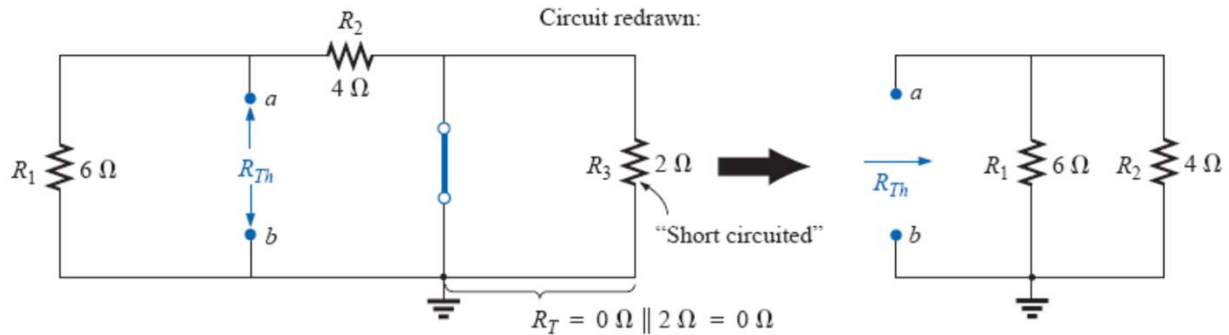**2. Calculate  $R_{Th}$**  by first setting all sources to zero (voltage sources are replaced by short circuits, and current sources by open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.)




9

$$R_{Th} = R_1 \parallel R_2 = \frac{(6\ \Omega)(4\ \Omega)}{6\ \Omega + 4\ \Omega} = \frac{24\ \Omega}{10} = 2.4\ \Omega$$
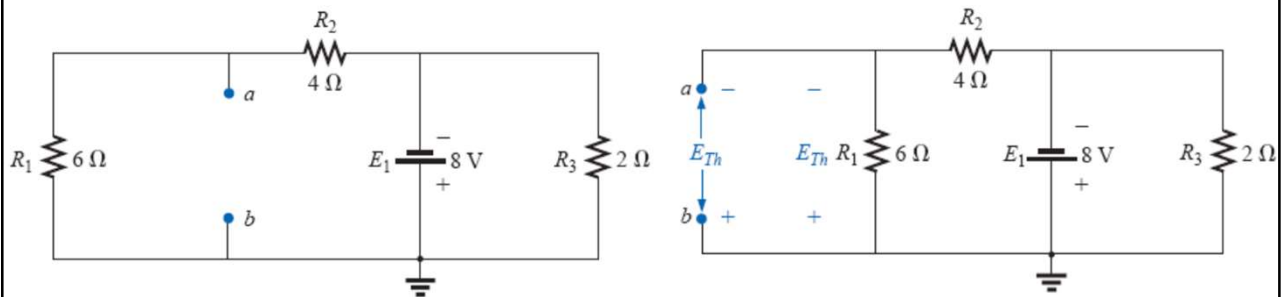
### 3. Determining $E_{Th}$ for the network

Calculate  $E_{Th}$  by first returning all sources to their original position and finding the open-circuit voltage between the marked terminals.




10

Applying the voltage divider rule,

$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$

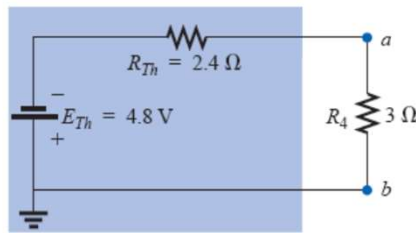**4. Substituting the Thévenin equivalent circuit for the network external to the resistor R4**



**Calculate: I (R4)= 0.88 A**

11

Thevenin's equivalent resistance can also be calculated from:

$$R_{Th} = V_{OC} / I_{SC}$$

Where:


$V_{OC}$  is open ckt voltage

$I_{SC}$  is short ckt current

12

## NORTON'S THEOREM

Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor.

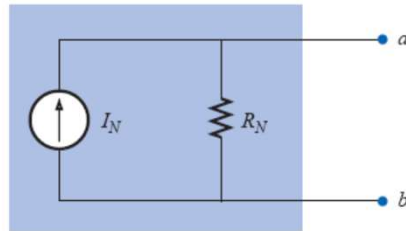


**FIG. 9.58**

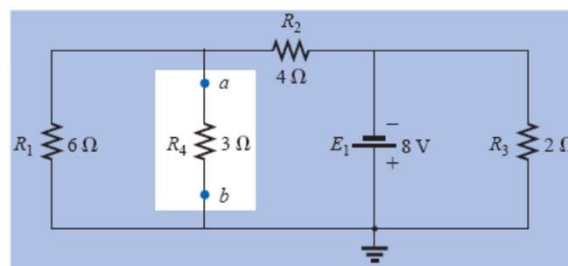*Norton equivalent circuit.*

13

Draw Norton's Equivalent Ckt for given network being  $R_4$  as load



Calculate:  $I(R_4) = ?$ , using Norton's Theorem

14

1. Remove that portion of the network across which the Norton equivalent circuit is to be found.

2. Mark the terminals of the remaining two-terminal network.

$R_N$ :

3. Calculate  $R_N$  by first setting all sources to zero (voltage sources are replaced with short circuits, and current sources with open circuits) and then finding the resultant resistance between the two marked terminals.

$$R_N = R_{Th}$$


$I_N$ :

4. Calculate  $I_N$  by first returning all sources to their original position and then finding the short-circuit current between the marked terminals. It is the same current that would be measured by an ammeter placed between the marked terminals.

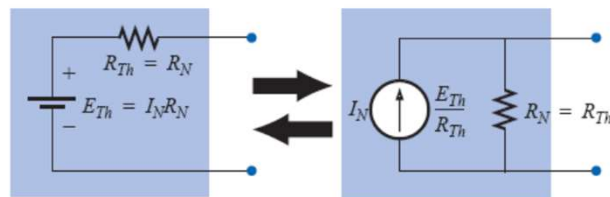5. Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.

15

Converting between Thévenin and Norton equivalent circuits




16



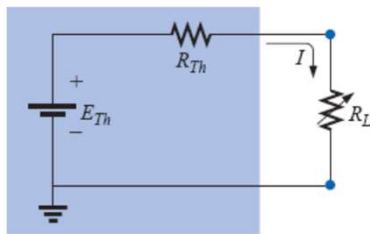
## MAXIMUM POWER TRANSFER THEOREM

A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thévenin resistance of the network as “seen” by the load.




$$R_L = R_{Th}$$

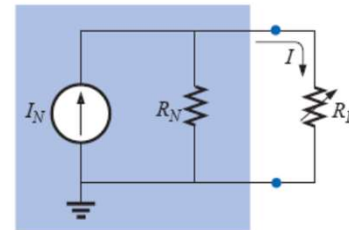


$$R_L = R_N$$

17

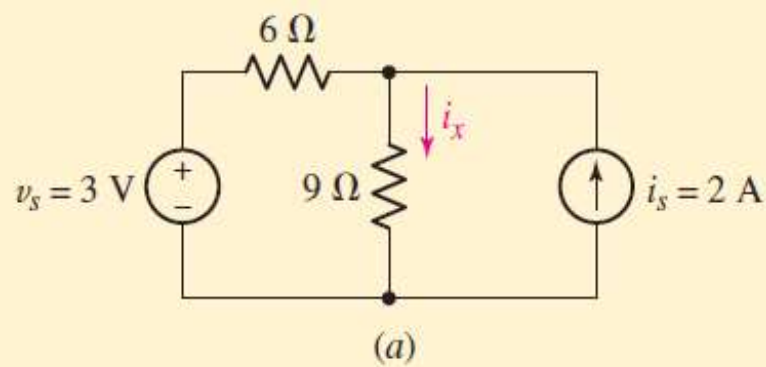


18

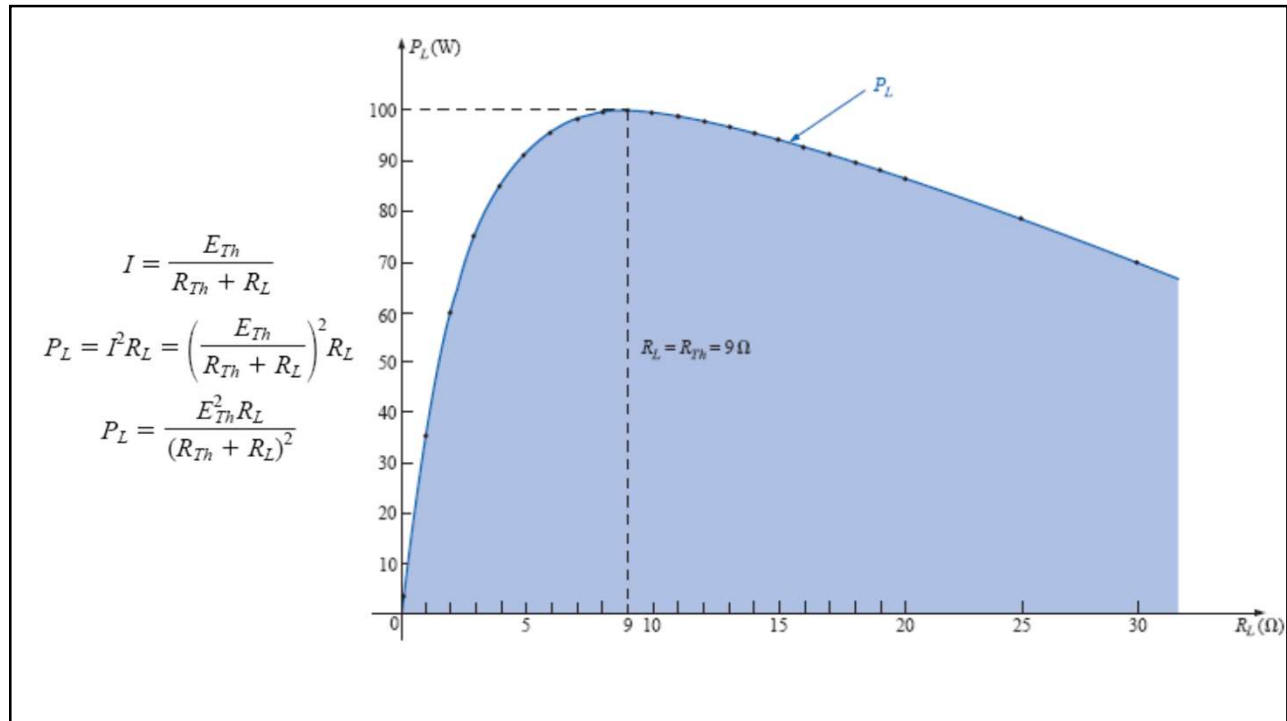

19

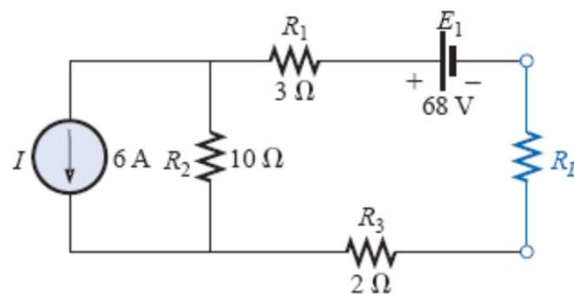
Find the value of  $R_L$  for maximum power to  $R_L$ , and determine the maximum power.



20

$$R_{Th} = R_1 + R_2 + R_3 = 3\ \Omega + 10\ \Omega + 2\ \Omega = 15\ \Omega$$

$$R_L = R_{Th} = 15\ \Omega$$

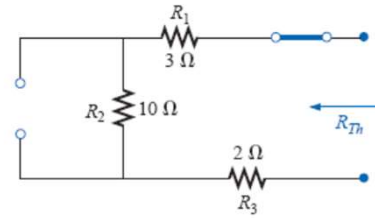

$$V_1 = V_3 = 0\ \text{V}$$


and  $V_2 = I_2 R_2 = I R_2 = (6\ \text{A})(10\ \Omega) = 60\ \text{V}$

Applying Kirchhoff's voltage law,

$$\sum_{\text{C}} V = -V_2 - E_1 + E_{Th} = 0$$

and  $E_{Th} = V_2 + E_1 = 60\ \text{V} + 68\ \text{V} = 128\ \text{V}$

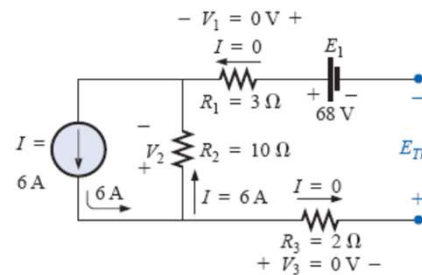Thus,  $P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(128\ \text{V})^2}{4(15\ \Omega)} = 273.07\ \text{W}$



21

Thanks

22